

~~JOB SHEETS~~

JOB SHEETS

ELECTRONICS TECHNICIAN

ASSIGNMENT SHEET

DC Theory

Materials: TM11-661

Introduction: To understand the nature of electricity this study covers the basic theory of the structure of matter. With this knowledge it is possible to determine what makes a electrical charge and the nature of charged bodies, Also that the flow of electricity actually is the movement of electrons from one level of potential energy to another. Included is an introduction to the units of measurement, and Ohm's Law.

Assignment: Study Chapter 2 to 5 of TM-661

Test:

1. Define the following:

- a. element
- b. atom
- c. compound
- d. electron
- e. proton and neutron

2. What effect does distance have when varied on the force of charges?

3. What is meant by the word potential?

4. Define conductors and insulators.

5. What is resistance and its unit of measurement?

6. State Ohm's Law and give three equations for I, E, and R.

7. Describe the effect a rise in temperature has on a copper conductor.

8. What is the definition of an ampere?

9. Describe the difference between a voltmeter and an ammeter and their use in an electrical circuit.

10. Give the color code of a 500,000 ohm resistor.

MEMORANDUM FOR THE RECORD
SUBJECT: [Illegible]

DATE: [Illegible]

1. [Illegible text paragraph]

2. [Illegible text paragraph]

3. [Illegible text paragraph]

4. [Illegible text paragraph]

- a. [Illegible]
- b. [Illegible]
- c. [Illegible]
- d. [Illegible]
- e. [Illegible]

5. [Illegible text paragraph]

6. [Illegible text paragraph]

7. [Illegible text paragraph]

8. [Illegible text paragraph]

9. [Illegible text paragraph]

10. [Illegible text paragraph]

11. [Illegible text paragraph]

12. [Illegible text paragraph]

13. [Illegible text paragraph]

Lucas. A.

ELECTRONICS TECHNICIAN

ASSIGNMENT SHEET

DC Circuits

Materials: TM-661 and Principles of Radio--Henney

Introduction: DC circuits provide the necessary foundation to understand complex electronic circuits. A good knowledge of these circuits will always be important for electronic equipment consists in a great part a DC voltage distribution system, in which the greater majority of troubles occur.

Assignment: Study chapters 6 and 9 in TM-661 and chapter 2 in Henney.

Test: Turn in work for the following problems:

TM-661

a to j on page 63 ✓

1 to 8 on pages 108 to 111 ✓

Henney

problems 46 to 48 in chapter 2

ELECTRONICS TECHNICIAN

LUCAS. A.

JOB SHEET

Multimeter

Objective: How to manipulate and read indications on a multimeter.

Materials: Various sizes of resistors and power supply.

Equipment: Multimeter.

Procedure: Draw the scales of your instrument and show where the following readings are located, giving the settings of the function and range switches:

Ohms: 100, 2K, 50K, and 1 Meg.

Volts DC: 5, 120, and 600.

Volts AC: 250, 400, and 800.

Measure and record the resistance of the resistors

120 OHMS, 2000 OHMS

52 K OHMS - 2 MEG. OHMS

Measure and record all AC and DC voltages found in the power supply.

190 V. D.C. + 350 V D.C. + 295 V D.C. +
4 V. A.C. 6 V A.C.

100 Watt

Calculated

Calculated for 100 Watt and 1000 Watt and 10000 Watt

Calculated for 100 Watt and 1000 Watt and 10000 Watt

Calculated for 100 Watt and 1000 Watt and 10000 Watt

Calculated for 100 Watt and 1000 Watt and 10000 Watt
Calculated for 100 Watt and 1000 Watt and 10000 Watt
Calculated for 100 Watt and 1000 Watt and 10000 Watt

Calculated for 100 Watt and 1000 Watt and 10000 Watt

Calculated for 100 Watt and 1000 Watt and 10000 Watt

Calculated for 100 Watt and 1000 Watt and 10000 Watt

Calculated for 100 Watt and 1000 Watt and 10000 Watt

Calculated for 100 Watt and 1000 Watt and 10000 Watt
Calculated for 100 Watt and 1000 Watt and 10000 Watt

Summary Questions:

1. What precautions must be observed when measuring voltages after a resistance measurement?

MAKE SURE THE FUNCTIONAL SWITCH IS CHANGED FROM THE OHMS POSITION TO VOLTS POSITION

2. How many times greater will the 100X setting be than the 10X?

10 TIMES GREATER

3. What part of the ohmmeter scale is the most accurate?

CENTER $\frac{2}{3}$ OF THE SCALE

4. What precaution must be made when measuring an unknown voltage?

SET THE RANGE SWITCH IN THE HIGHEST POSITION.

The first of these is the fact that the company has been successful in its operations since its inception in 1911.

The second of these is the fact that the company has been successful in its operations since its inception in 1911.

The third of these is the fact that the company has been successful in its operations since its inception in 1911.

The fourth of these is the fact that the company has been successful in its operations since its inception in 1911.

10
 9
 8
 7
 6
 5
 4
 3
 2
 1
 0

100 Ω ON R x 1
2 K Ω " R x 100
50 K Ω " R x 10 K.
1 MEG " R x 100 K

RANGE FACT:	
5V	ON
120V	ON
600V	ON

250 V. 200	500 400	15
400 V. 200	500 400	15
800 V. 200	1500 400	15


ELECTRONICS TECHNICIAN

JOB SHEET

Voltage Divider--Loaded

Objective: How to construct a voltage divider for a given load and to study the effects of load on EMF.

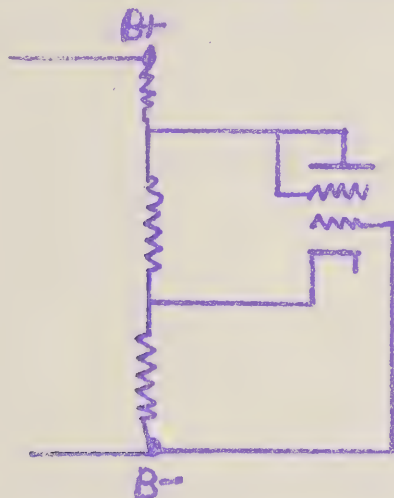Materials: Obtain vacuum tube from instructor.



Equipment: Multimeter, power supply and tube manual.


Procedure: From data in tube manual determine current and voltage requirements for tube.
Measure no load voltage of power supply.
Load power supply with a load equivalent to the tube and measure voltage again. The voltage should still be higher than needed if the power supply is the proper type. Increase the load 10 ma. more than load requirements. Measure voltage again. This voltage and current will be the basis for designing the bleeder.

Construct circuit similar to one shown above.

Draw schematic of your circuit and included values of all resistances and voltages found on tube and across bleeder.

Question: What is the value of the bleeder current?

12 ma.

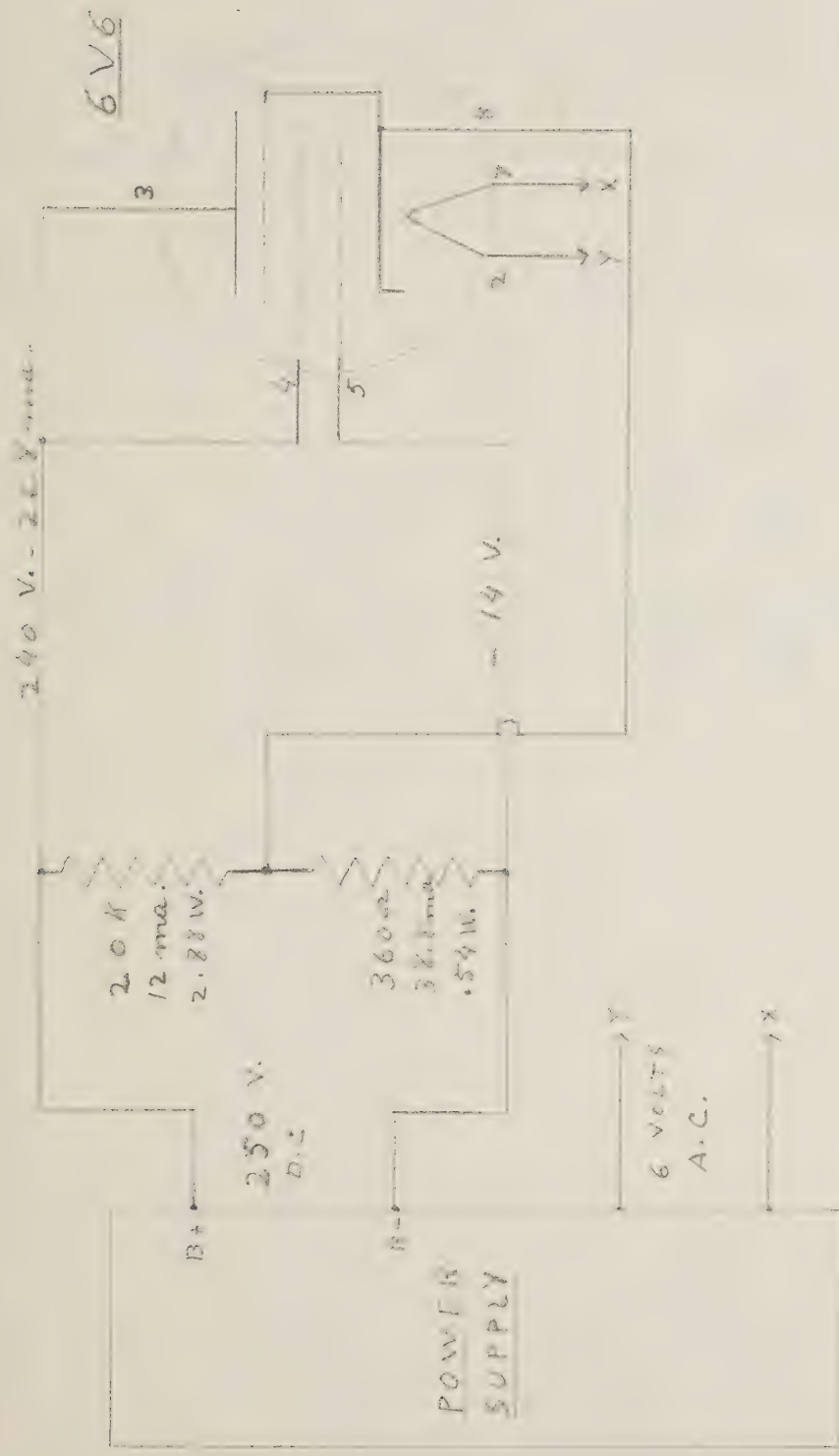

San Jose State College	Los Angeles Tech. School	Los Angeles Tech. School	DATE
Los Angeles, California	Los Angeles, California	Los Angeles, California	SEPT. 21-56
Class: Electronics	Approved By:	Drawn By: LUCAS, AGUSTIN	


ELECTRONICS TECHNICIAN

JOB SHEET

Series Type Ohmmeter



Objective: How to construct and understand the characteristics of the common ohmmeter.

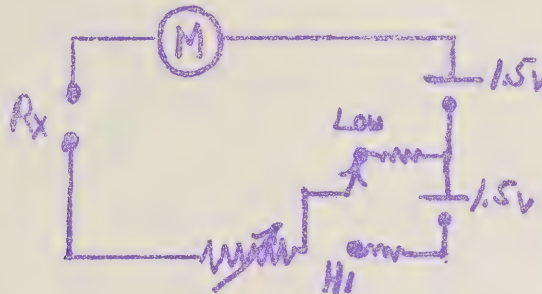Materials: Basic meter, two $1\frac{1}{2}$ volt batteries, decade box (resistance) and components to construct circuit as shown.



Procedure: Construct ohmmeter with two ranges. Use $1\frac{1}{2}$ volt for one range and 3 volts for the higher range. Use decade box to check accuracy of meter and two calibrate.

Draw calibrated scales:

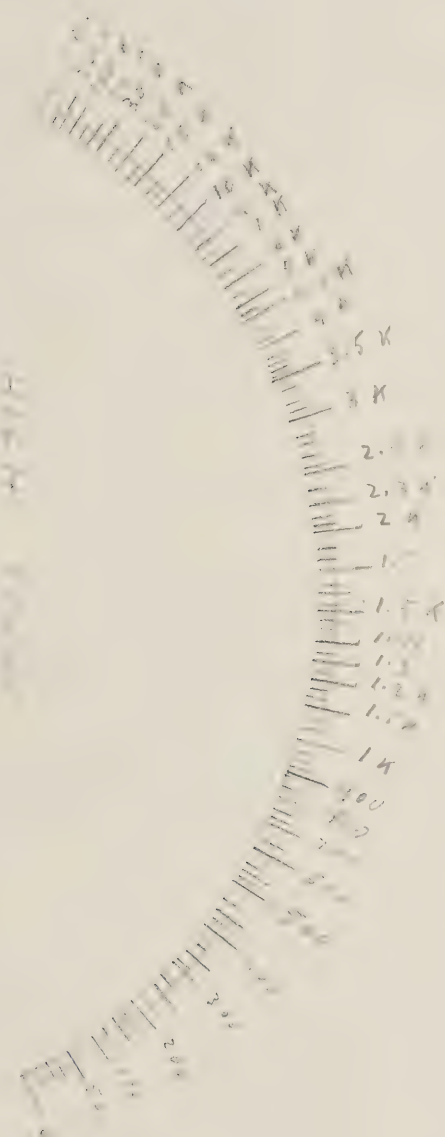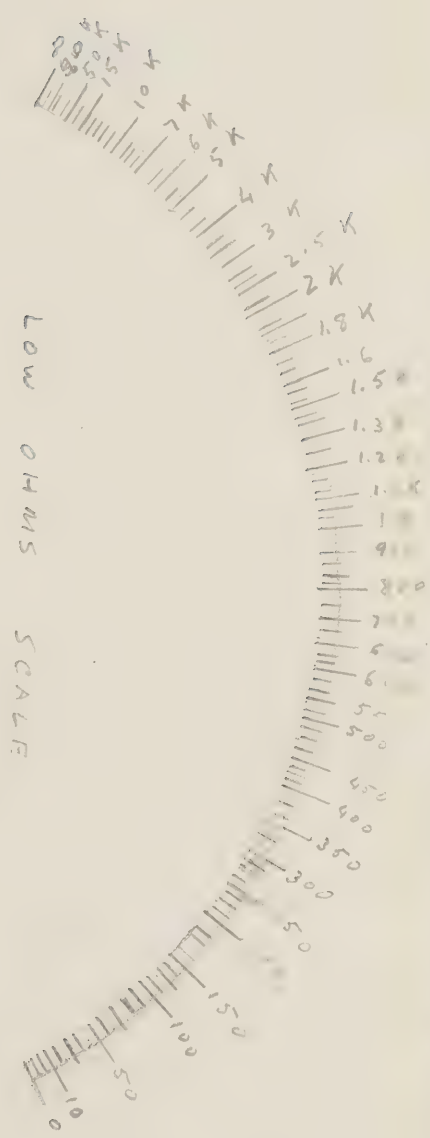

Los Angeles Radio Institute

1111 1/2 SERIES TYPE WINDUP

1111

Los Angeles, California

Brown Bay

Lucas HAWK

Los Angeles Electronics

Approved By

SEPT 27 1950


ELECTRONICS TECHNICIAN

JOB SHEET

Voltmeter

Objective: How to construct, understand limitations, and use of the voltmeter.

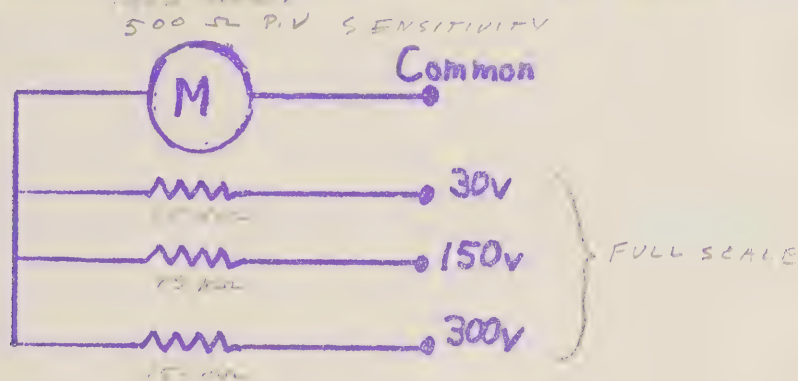Materials: Meter used on job sheet for Meter Sensitivity, and components to construct circuit as shown:



Equipment: VTVM and power supply.

Procedure: Construct a voltmeter having three ranges up to 300 volts.

Measure the voltages obtained from the bleeder resistor of the power supply with the VTVM and the voltmeter you have just constructed. Record each separately:

Bleeder Tap	VTVM	Voltmeter
1. 30 V.	30 V.	29.5 V
2. 100 V	100 V	100 V
3. 300 V	300 V	300 V
4. 300 V	300 V	295 V
5. 300 V	300 V	100 V

Job Sheet

Voltmeter (cont.)

Summary Questions:

1. Why did the voltages measure higher with the VTVM?

THE HIGH RESISTANCE OF THE VTVM DOES NOT LOAD THE CIRCUIT AS THE ANALOG METER WOULD.

2. Describe the importance of meter sensitivity when measuring voltages in electronics circuits.



THE SENSITIVITY OF A METER IS OF HIGH IMPORTANCE. IF A METER OF LOW SENSITIVITY IS CONNECTED TO A CRITICAL CIRCUIT, IT WILL DRAW TOO MUCH CURRENT THERE, FOR GIVE UN-ACCURATE READINGS. THE HIGHER THE RESISTANCE OF THE METER, THE HIGHER THE SENSITIVITY.

ELECTRONICS TECHNICIAN

JOB SHEET
Ammeter and Meter Resistance

Objective: How to measure meter resistance and construct an ammeter.

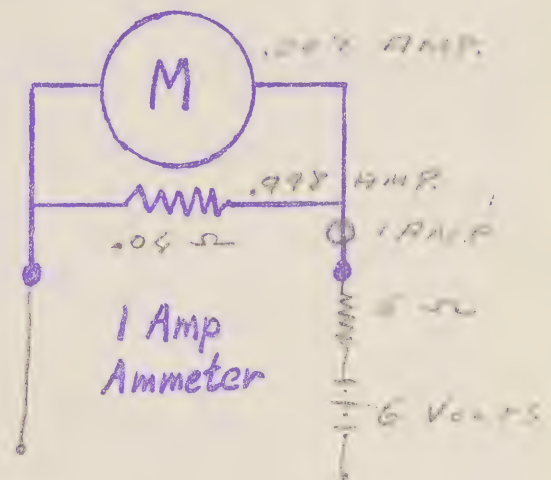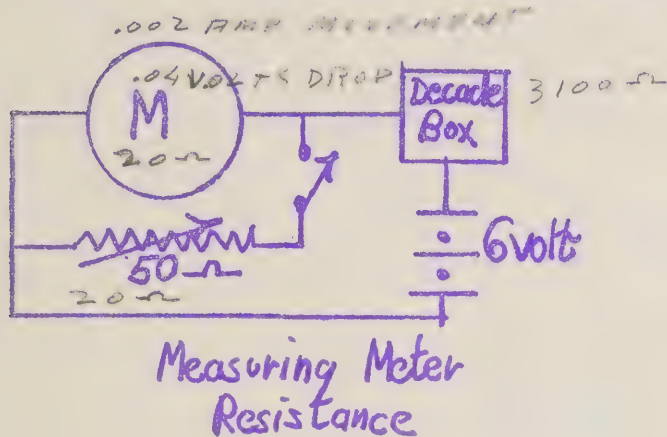Materials: Basic Meter, 6 volt battery, and components to construct circuits as shown:



Equipment: Resistance decade box, and resistance bridge.

Procedure: To measure resistance of meter, adjust decade box with switch open for variable shunt until meter reads full scale. Close switch and adjust shunt until meter reads $\frac{1}{2}$ scale. Measure shunt resistance and record. This the practical value of the meter resistance.

To construct the ammeter, use data obtained above. If your meter has a low value of resistance, use resistance wire for the shunts. The proper length can be measured with the bridge, and wound on $\frac{3}{8}$ or $\frac{1}{2}$ inch tubing.

Summary: Write a technical report on how the procedure used in this job measures the resistance of the meter.

ELECTRONICS TECHNICIAN

JOB SHEET


Voltmeter Sensitivity

Objective: How to measure meter sensitivity.

Materials: Milliampmeter(DC), Resistance Decade Box, 6 volt battery, and hookup wire.

Procedure: Connect circuit as shown:

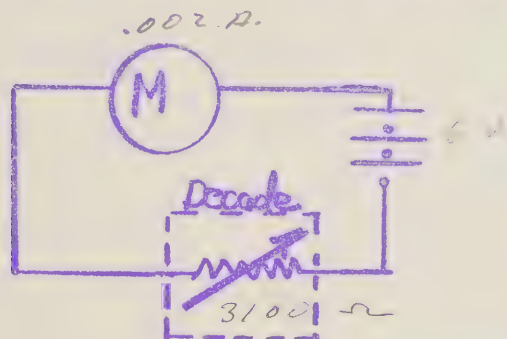CAUTION!!! Check to see that full range of resistance in decade box is in circuit before connecting battery.



Adjust resistance until meter reads full scale.
Record value of resistance.

3100 Ω

Summary Questions:

From the above data calculate the following:

1. Current flow for full scale deflection.

.002 AMPS $\left(\frac{6}{3100} = .002 \right)$
SERIES RESISTANCE - 3100 Ω
VOLTAGE DROP ACROSS METER - .04 VOLTS.
METER INTERNAL RESISTANCE - 20 Ω

2. Ohms per volt.

$$\#1 \quad \frac{20 \Omega \text{ INTERNAL RESISTANCE}}{.04 \text{ METER VOLTAGE DROP}} = 500 \text{ OHMS PER VOLT}$$

$$\#2 \quad \frac{1}{.002 \text{ FULL SCALE CURRENT}} = 500 \text{ OHMS PER VOLT}$$

ELECTRONICS TECHNICIAN

JOB SHEET

R-C Time Constant

Objective: How to construct a R-C time circuit and to understand time with respect to the charge and discharge of R-C constants.

Materials: To perform and construct circuits as illustrated:




Equipment: VTVM and low voltage power supply.

Procedure: With equipment set up as shown in fig. 1, find the firing and deionizing points of the lamp. Record these voltages

85 V 68 V 100 V

Calculate and construct circuit to make neon lamp flash once every second. Draw schematic giving all values:
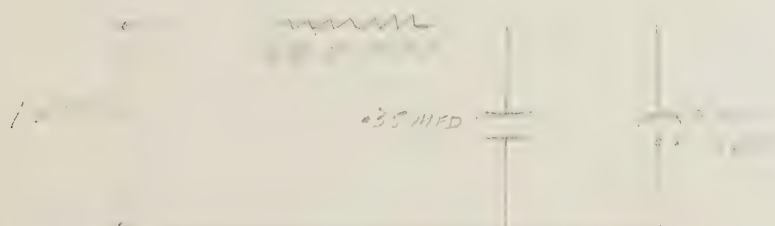
$$85 : 110 = 77\% ; 68 : 110 = 64\% = \frac{1}{T.C.} 5,5 \text{ sec}$$
$$T.C. = 10 \text{ SEC.} \quad 10 = R.C. \quad C = 0.25 \mu F$$
$$R = \frac{10}{0.25} = 28.5 \text{ MEG.}$$



Summary Questions:

1. If resistance is in the megohms and capacitance is in microfarads. What unit of time will the constant be in?

See summary

Job Sheet---R-C Time Constant

2. If resistance is in ohms and capacitance in microfarads, what unit of time will the constant be in?

microseconds

3. What percentage of full charge is two time constants?

70%

4. What percentage of discharge is three time constants?

5%

ELECTRONICS TECHNICIAN

ASSIGNMENT SHEET

R-C Time Constants

Materials: Keith Henney, and Glen Richardson, Principles of Radio, Chapter 6, sections 6.3, 6.4, 6.5, and 6.6.

Army Tech. Manual, TM 11-581, Electrical Fundamentals (Alternating Current), Chapter 3, Section 43

Navships 900,016, T.O. 16-1-195, Radar Electronic Fundamentals, Section III, paragraph 17.

Introduction:

A knowledge of R-C time constants is an electronics technician is important, since all electronic circuits in one form or another contain a combination of resistance and capacitance. A resistor and capacitor provides an accurate and inexpensive method for timing and wave shaping.

Assignment:

Read references given under material.

Test:

1. If a 1k ohm resistor and a .05ufd capacitor are connected in series, what is the time constant of the circuit? $50 \mu s$
2. A capacitor has 500 volts across it when fully charged. If it is connected in a circuit with a resistor in series, what will the voltage be at the end of three time constants if the circuit is shorted? $15 V$
3. How many time constants will it take a capacitor-resistor combination to reach 95% of the applied voltage? 3



ELECTRONICS TECHNICIAN

JOB SHEET

R-C Time Constant

Objective: How to construct a R-C time circuit and to understand time with respect to the charge and discharge of R-C constants.

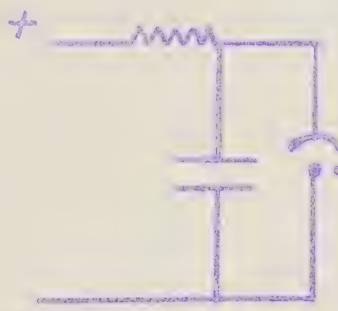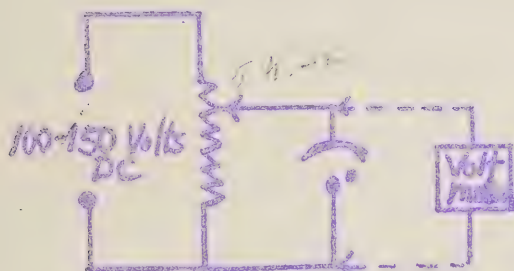Materials: To perform and construct circuits as illustrated:



Equipment: VTVM and low voltage power supply.


Procedure: With equipment set up as shown in fig. 1, find the firing and deionizing points of the lamp. Record these voltages.

FIRE AT 85 V. 110 SUPPLY

Calculate and construct circuit to make neon lamp flash once every seconds. Draw schematic giving all values:

$$85 \div 110 = 77\% ; .5 \div 110 = 64\% ; 5 = \frac{1}{2} T.C.$$
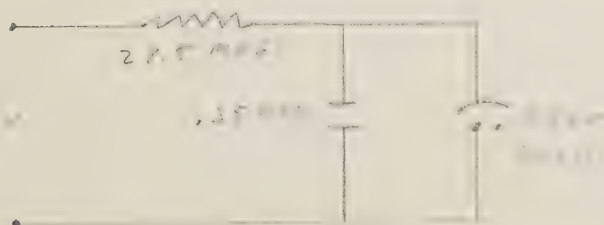
$$10 = R.C \quad R = \frac{10}{35} = 28.5 \text{ MEG.}$$



STIMULATING QUESTIONS:

1. If resistance is in the megohms and capacitance is in microfarads. What unit of time will the constant be in?

SECONDS

Job Sheet--R-C Time Constant

2. If resistance is in ohms and capacitance in microfarads,
what unit of time will the constant be in?

MICRO SECONDS

3. What percentage of full charge is two time constants?

86%

4. What percentage of discharge is three time constants?

95%

ELECTRONICS TECHNICIAN


INFORMATION SHEET

RC Time Constants

R-C Time Constant: The time required to charge a capacitor to 63% or to discharge it to 37% of its final voltage.

The value of the time constant in seconds is equal to the product of the circuit resistance in ohms and capacity in farads.

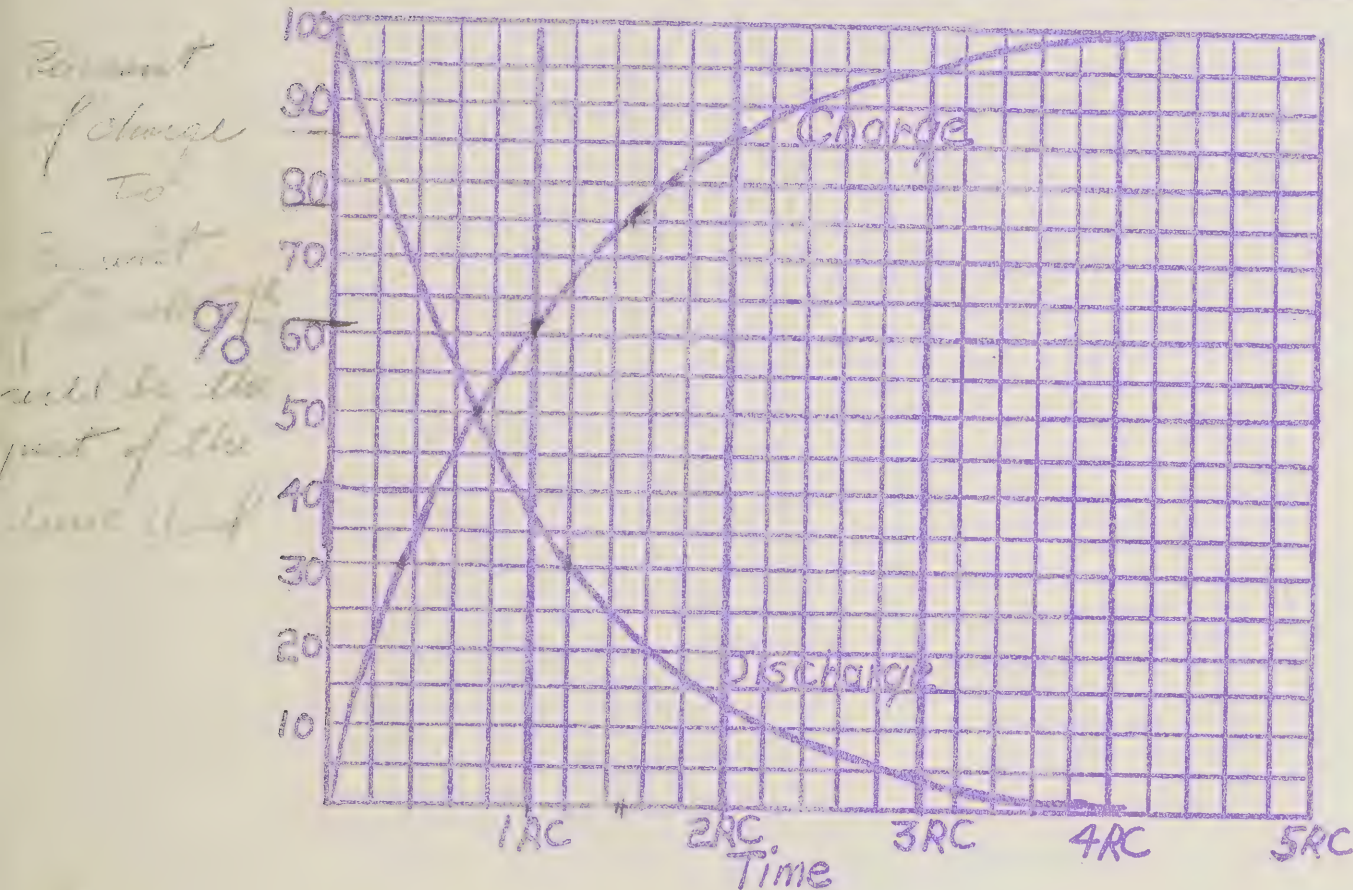110 UNIVERSAL CHARGE AND DISCHARGE CURVES OF R-C CIRCUITS



SHORT TABLE OF UNIVERSAL TIME-CONSTANT VALUES

<u>Time in Seconds</u>	<u>% of Applied-Charge</u>	<u>% of Applied-Discharge</u>
.5RC	39	61
1 RC	63	37
2 RC	86	14
3 RC	95	5
4 RC	98	2
5 RC	99	1

just

ELECTRONICS TECHNICIAN

JOB SHEET

Oscilloscope Fundamentals

Objective: How to manipulate an oscilloscope.

Equipment: Oscilloscope, audio oscillator, and scope calibrator.

Procedure: Draw a diagram of the front panel of the oscilloscope and label all controls and their use:

CONTROLS AND THEIR USE:

VERTICAL AND HORIZONTAL POSITION:
DEFLECTION PLATES TO MOVE THE
AND RIGHT.

VARY THE POSITION OF
THE SPOT ON THE

BRIGHTNESS CONTROL: VARIES THE VOLTAGE TO THE GRID OF THE CATHODE RAY TUBE
AMP. SYNCHRONIZES THE SAW TOOTH WAVE WITH THE INPUT SIGNAL.


LINEARITY: VARIES VOLTAGE BETWEEN FOCUS AND ANODE.
FINE FREQ. SELECT - FOR SIGNAL

BE SEEN ON THE TIME BASE LINE.

VERT. AND HORIZ. AMPL.: USED MAINLY TO ADJUST WAVEFORM TO BE
RUN BETTER ON THE FACE OF THE SCREEN.

IF SCRAM DRAWN ON SEPARATE PAGE

Connect equipment as shown:

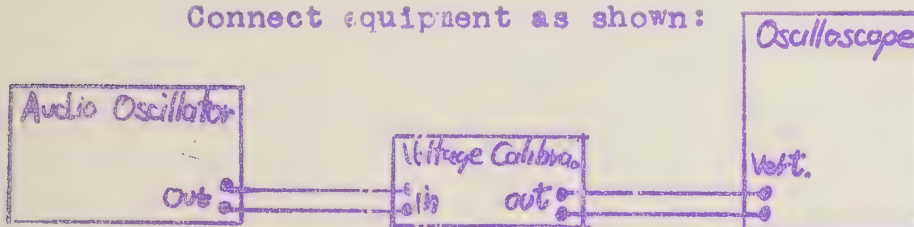

Observe waveforms at 30, 60, 400, and 1500 cycles.
Use voltage calibrator and set the output of the oscil. at 2 volts peak to peak.

Summary Questions:

1. What is the horizontal sweep rate of the scope in case if three full cycles are observed at the different frequencies under procedure?

2. Describe peak to peak, effective, rms, average, and maximum values.

PEAK
IVE VALUE: =
RMS =

MAXIMUM IS THE VALUE

3. Describe your method for using a source of filament voltage to calibrate an oscilloscope.

FILAMENT

4. Give your procedure for using the voltage calibrator in this job sheet.


FIRST SET CALIBRATOR FOR
TO BE
ON

SET CALIBRATOR TO SIGNAL
FOLLOW SIGNAL
VOLTAGE ACROSS
ON SCOPE


School: Los Angeles Trade Tech. C.	Title: OSCILLATIONS	Date:
Los Angeles, California	Drawn By: J. L. S.	
Class: Electronics	Apparatus: By: J. L. S.	



VERB. LUN

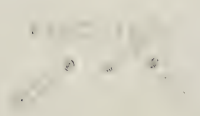

M-DU

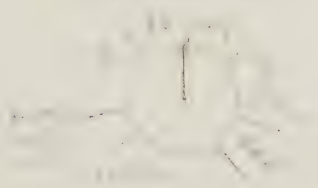

VERB. LUN



VERB. LUN

ORIGINALS TECHNICAL

JOB SHEET


Integrating and Differentiating Circuits

Objective: How to observe the effects of RC circuits.

Materials: Potentiometer and capacitor used for RC circuit.

Equipment: Square wave audio generator and oscilloscope.

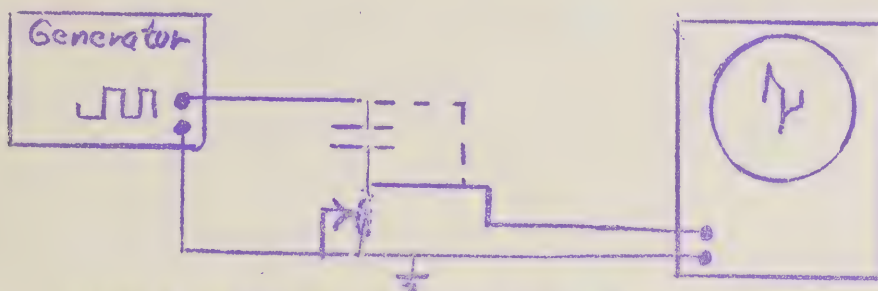Procedure: Connect equipment and materials as shown:



With a fixed frequency show in each case the shape of the wave form across the capacitor and the resistor for time constants of $1/10$ and 10 times one alternation of the input frequency.

(Use form)


Summary Questions:

1. What must the sum of voltages across the resistor and capacitor be equal to? *THE INPUT VOLTAGE*
2. Explain how the peak voltage across the resistor can be twice the input voltage?

AT THE HIGHEST POINT OF THE SQUARE WAVE THE VOLTAGE ACROSS THE CAPACITOR IS ZERO AND THE VOLTAGE ACROSS THE RESISTOR IS TWICE THE INPUT VOLTAGE. THIS IS BECAUSE THE CAPACITOR IS CHARGED TO THE INPUT VOLTAGE AND THE RESISTOR IS DISCHARGED.

WAVE FORMS DRAWN ON SEPARATE SHEET WITH TIME = 1 AND 10 TIMES THE T.C. OF 1/10 OF ONE ALTERNATION OF THE INPUT WAVE. AND 10 TIMES THE T.C. OF 10 TIMES ON AT AN INPUT FREQUENCY OF 1000 CYCLES

143

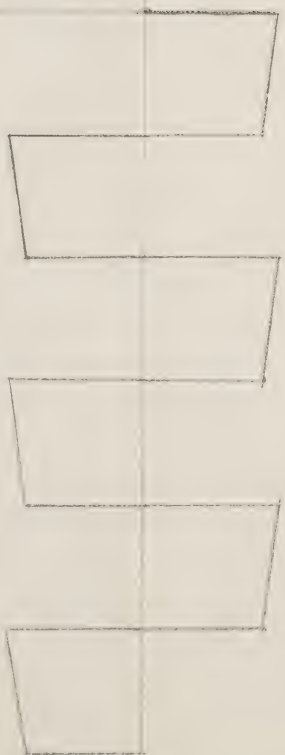

DIFFERENTIATING - 1000 CFS - T.C. - 1/10 ALTERNATION

DIFFERENTIATING - 1000 CFS - T.C. - 10 ALTERNATIONS



INTEGRATING - 1000 CFS - T.C. - 1/10 ALTERNATION

INTEGRATING - 1000 CFS - T.C. - 10 ALTERNATIONS

LOS ANGELES TRADE-TECH. JR. COLLEGE

TITLE: INTEGRATING & DIFFERENTIATING

DATE


LOS ANGELES, CALIF.

DRAWN BY: LUCAS, AGUSTIN

10-15-56

ELECTRONICS CLASS

APPROVED BY:

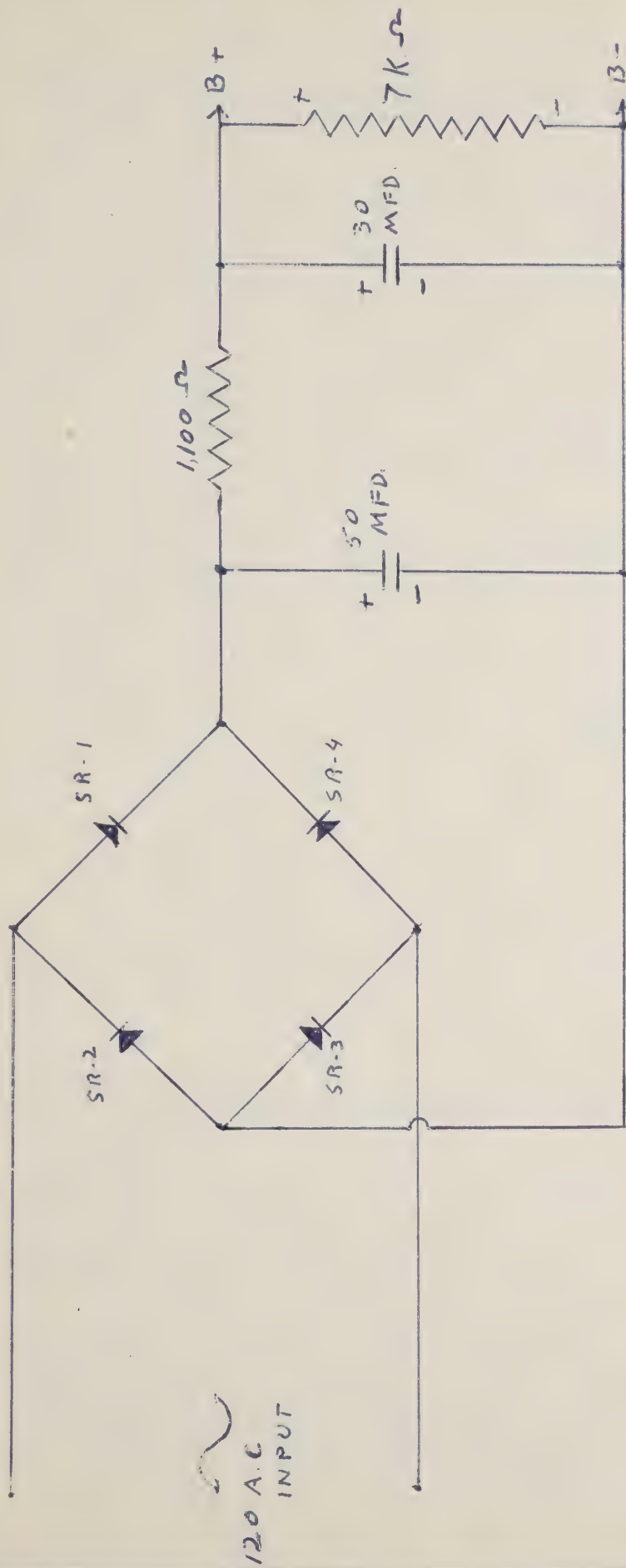

SR's - 150 V
75 MA.

LOS ANGELES TRADE-TECH. JR. COLLEGE	TITLE: SELE. BRIDGE RECTIFIER	DATE
LOS ANGELES, CALIF.	DRAWN BY: A. LUCAS	10-23-56
ELECTRONICS CLASS	APPROVED BY:	

Los Angeles Trade Tech. Jr. College
Instructor: R.H. Oeffinger

JS-

ELECTRONICS TECHNICIAN

JOB SHEET

Full-wave Rectification

Objective: How to test and service full-wave power supplies.

Materials: Obtain full-wave test power supply.

Equipment: Oscilloscope and voltmeter.

Procedure: Draw schematic of power supply --use drawing form.

Show with arrows the current flow for each half cycle of primary source.

Connect scope and voltmeter across output. Record voltage and waveforms for the following:

Connected as full-wave
475 volts

Amplified

Half-wave
450 volts

Summary Questions:

1. What is the ripple frequency at 60 cycles?
120 c.p.s.


2. Which is the easier to filter, a half-wave or full-wave power supply? Why?

Full wave. The ripple frequency is twice the half wave, therefore is easier to filter


3. Describe your method for determining a defective power transformer.

By tacking voltage measurements it could be determine if any of the windings were open. By continuity checks it would show if there were any shorted or open windings, also.

FULL WAVE RECTIFIER

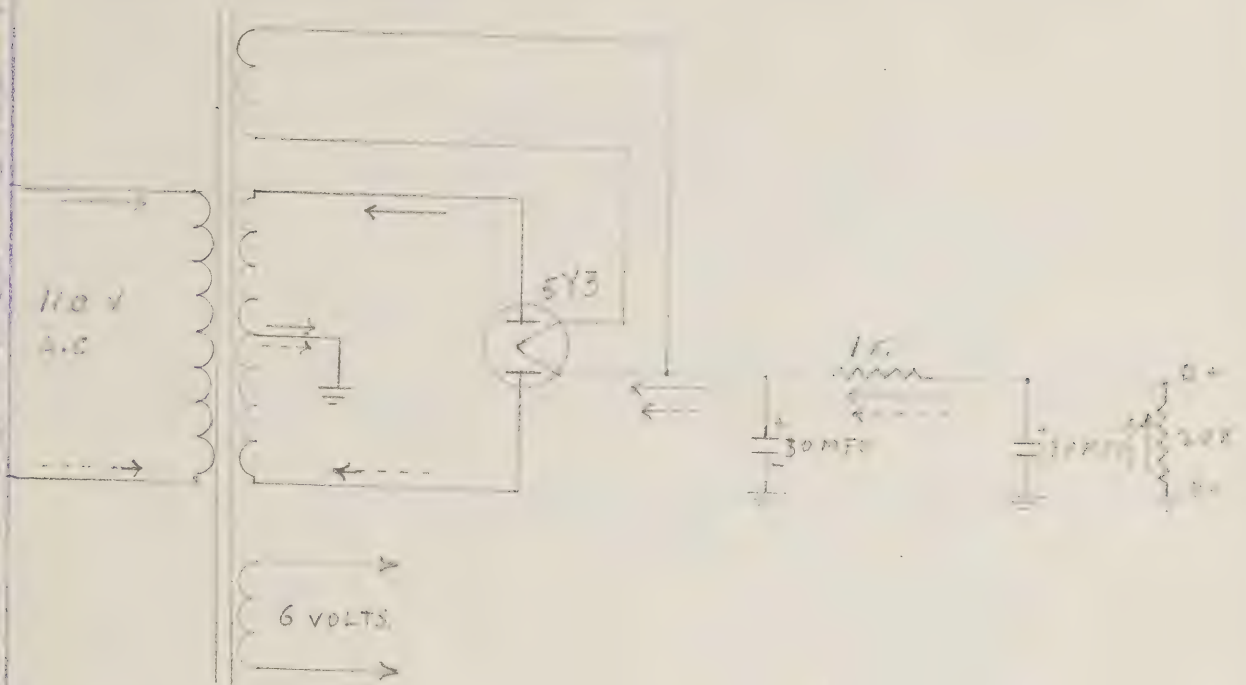

VOLTAGE TRIPLER

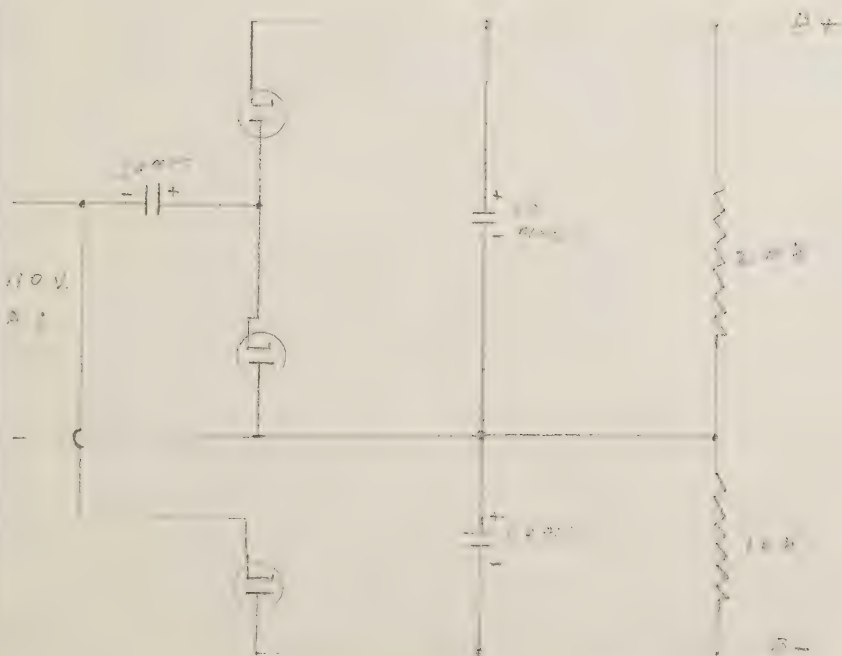

110 V A.C. 110 V A.C. 110 V A.C.

FULL WAVE RECT. AND VOLT. TRIPLER

Los Angeles Trade Tech Jr. College
Instructor: R.H. Oeffinger

JS-

ELECTRONICS TECHNICIAN

JOB SHEET

Voltage Doublers

Objective: How to test and service voltage doublers.

Materials: Obtain half-wave and full-wave voltage doubler power supplies.

Equipment: Oscilloscope and voltmeter.

Procedure: Draw a schematic for each type(use form) and show the following: current flow with arrows, polarity on capacitors, and voltage output.

Connect oscilloscope and voltmeter to output and record voltages and waveforms for the following:

Light Load
275 volts

Heavy Load
120 volts

Half wave

300 volts

250 volts

Full wave

Summary Questions:

1. What component determines the voltage regulation in voltage doublers?

The value of the capacitors

2. What types of electronic equipment are voltage doublers suitable to deliver power to?

Low current-using devices

3. Draw a schematic of a voltage tripler.

Drawn on separate form



LUCAS, AGUSTIN

Los Angeles Trade Tech. Jr. College
Instructor: R.H. Oeffinger

JS-


ELECTRONICS TECHNICIAN

JOB SHEET

Selenium Rectifier Power Supply

Objective: How to construct and study the characteristics of AC-DC half-wave selenium power supplies.

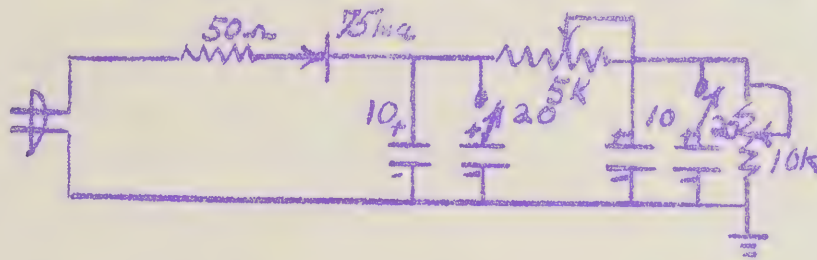Materials: Parts and components to construct circuit as shown:



Equipment: Oscilloscope and voltmeter.

Procedure: Same as previous power supply:

I. Low value of filter resistor: 152 Volts

Medium value 125 Volts

High value 106 Volts

II. Low values of capacitance:

Input 130 Volts

Output 122 Volts

High values of capacitance:

Input 165 Volts

Output 157 Volts

III. Change of load:

Light Load 152 Volts

Heavy Load 140 Volts

Job Sheet--Selenium Rectifier (cnt.)

Summary Questions:

1. Describe the action of a selenium rectifier.

The selenium rectifier will pass current in one direction, but offers a very high resistance in the other direction due to the combination of the selenium coating on one side of the plates and the plates themselves.

2. Calculate the voltage drop across the selenium for light and heavy load.

Values: Light load 20K Heavy load 10K Filter resistor 500 ohms

Voltage measurements across input cap. With load 152 Volts

Without load 170 Volts

Heavy load 140 Volts

$$152 \div 20K = 7.6 \text{ Ma. IN CRT}$$

$$500 \Omega \times 7.6 \text{ Ma} = 3.8 \text{ V. FILT. R.}$$

3. What are the advantages and disadvantages of selenium rectifiers?

Advantages: Do not need filament voltage supply

Disadvantages: Low inverse peak voltage

Low current-carrying ability

Temperature changes affect the backward resistance


4. What is the proper method for checking a selenium rectifier?

Connect another in parallel with the one being checked and measure the output voltage. parallel


$$140 \div 10K = 14 \text{ Ma. IN CRT}$$

$$500 \Omega \times 14 \text{ Ma} = 7 \text{ VOLT. FILT. RES.}$$

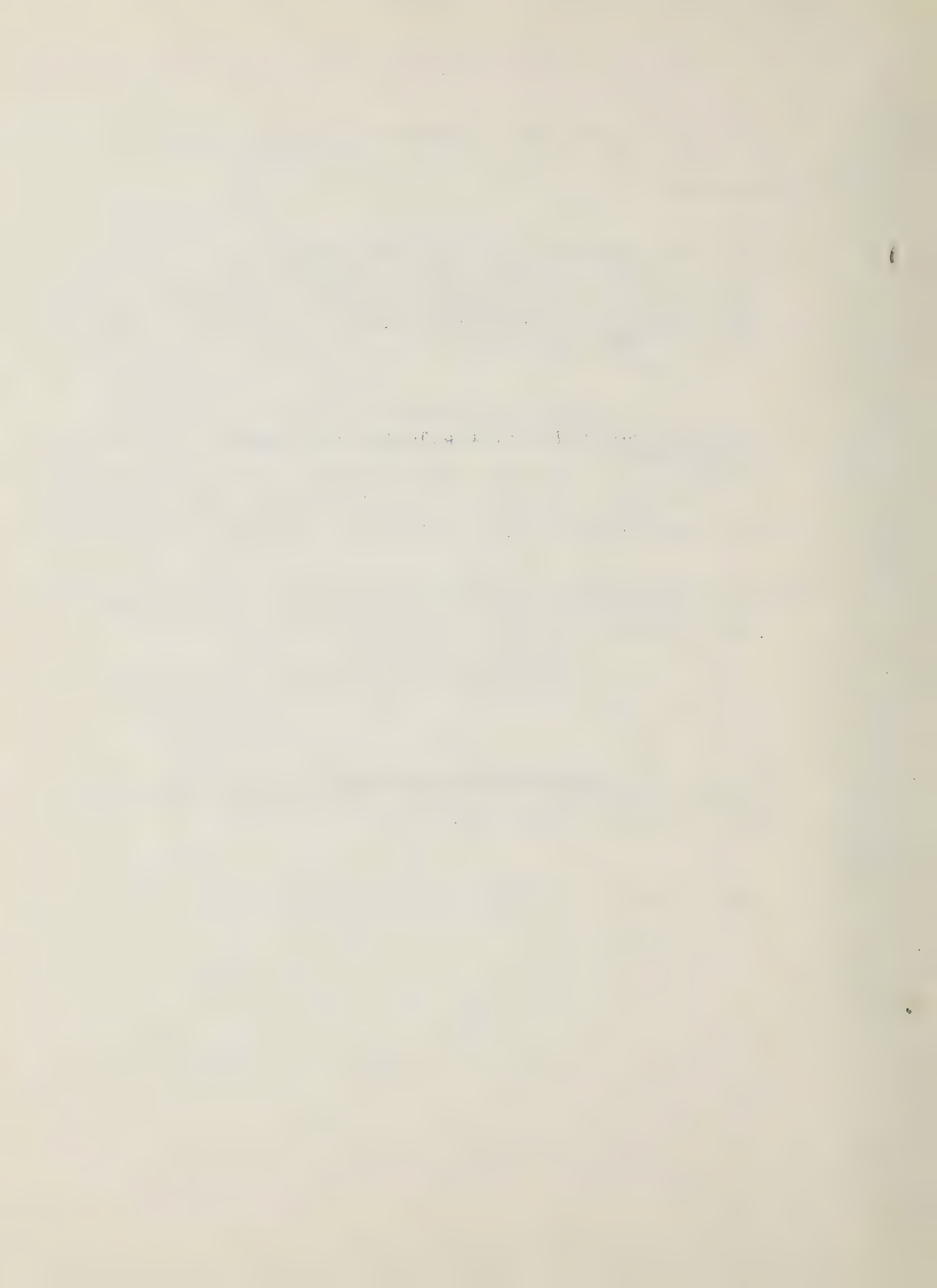
$$170 - \frac{140}{140} = 23 \text{ VOLT. RECT DROP}$$




HALF WAVE RECTIFIER (TUBE)

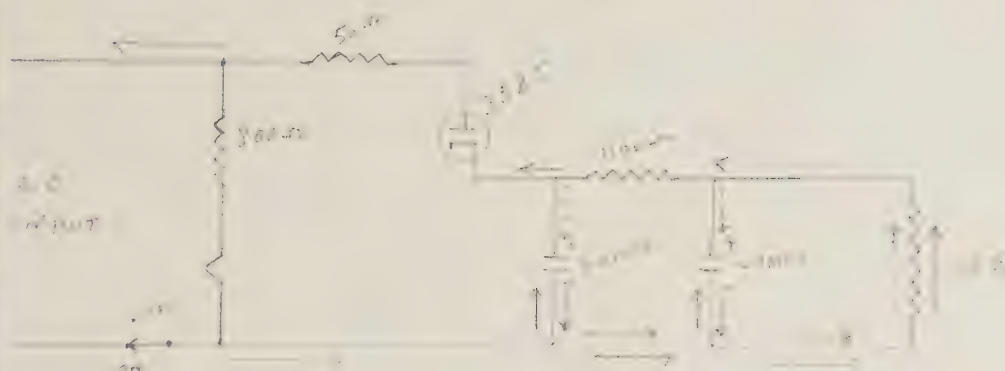

HALF WAVE RECTIFIER (SELENIUM)

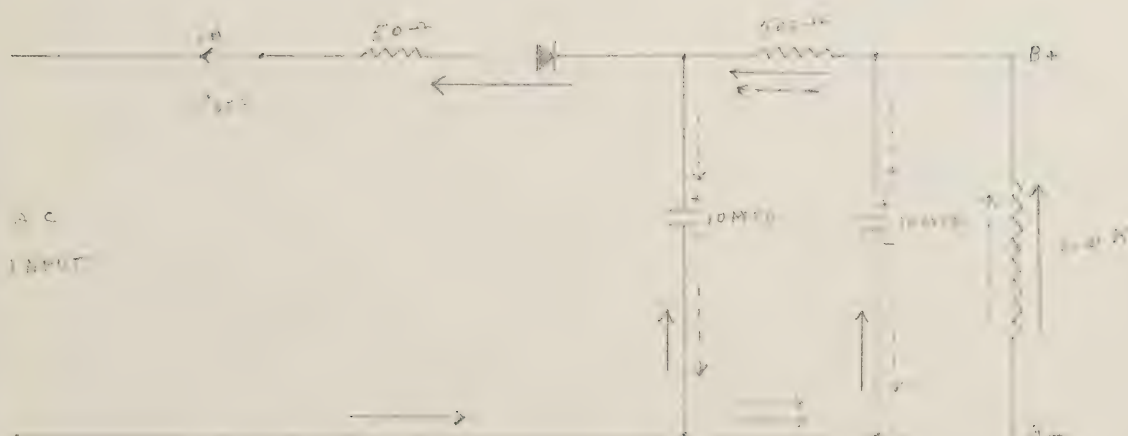

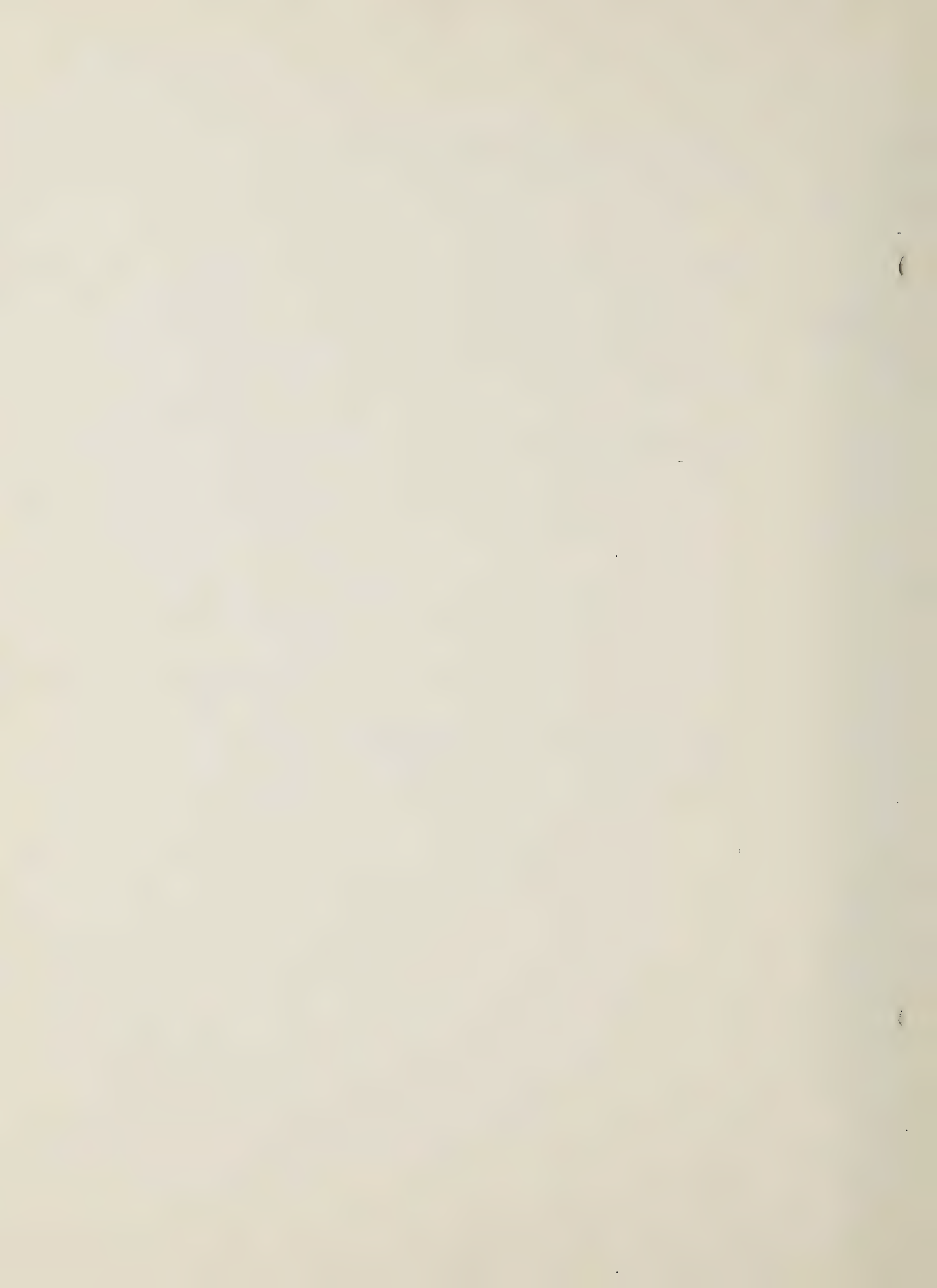

Los Angeles Trade Tech. Jr. College
Instructor: R.H. Oeffinger

JS-


ELECTRONICS TECHNICIAN

JOB SHEET

Half-wave Rectifier--AC-DC Power Supply

Objective: How to construct and test half-wave AC-DC power supplies.

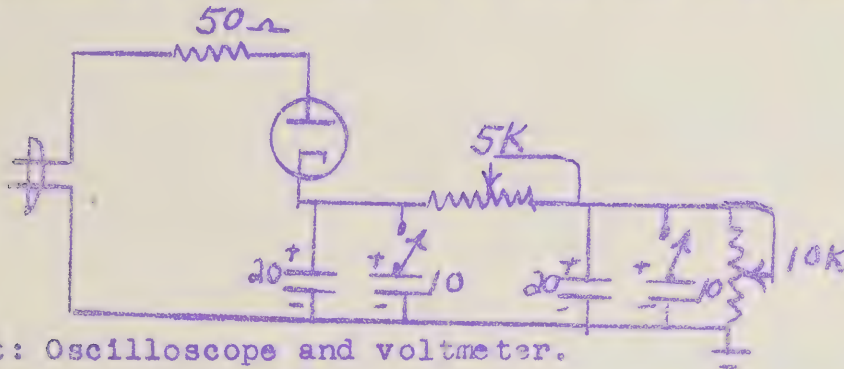Materials::Parts and components to construct the following circuit:



Equipment: Oscilloscope and voltmeter.

Procedure: Set R_L FOR RATED LOAD. Connect scope and voltmeter across load resistor. Record voltage readings and waveforms for the following conditions:

I. Low value of filter resistor R_F .

160 Volts

Medium value.

150 Volts

High value

140 Volts

II. Change values of capacitance and check voltage and waveforms across them:

Low values

Input 165 Volts

Output 145 Volts

High values


Input 165 Volts

Output 140 Volts

III. Connect scope and voltmeter at output and vary load. Record voltage and waveforms.

Light Load 140 Volts

Heavy Load 86 Volts

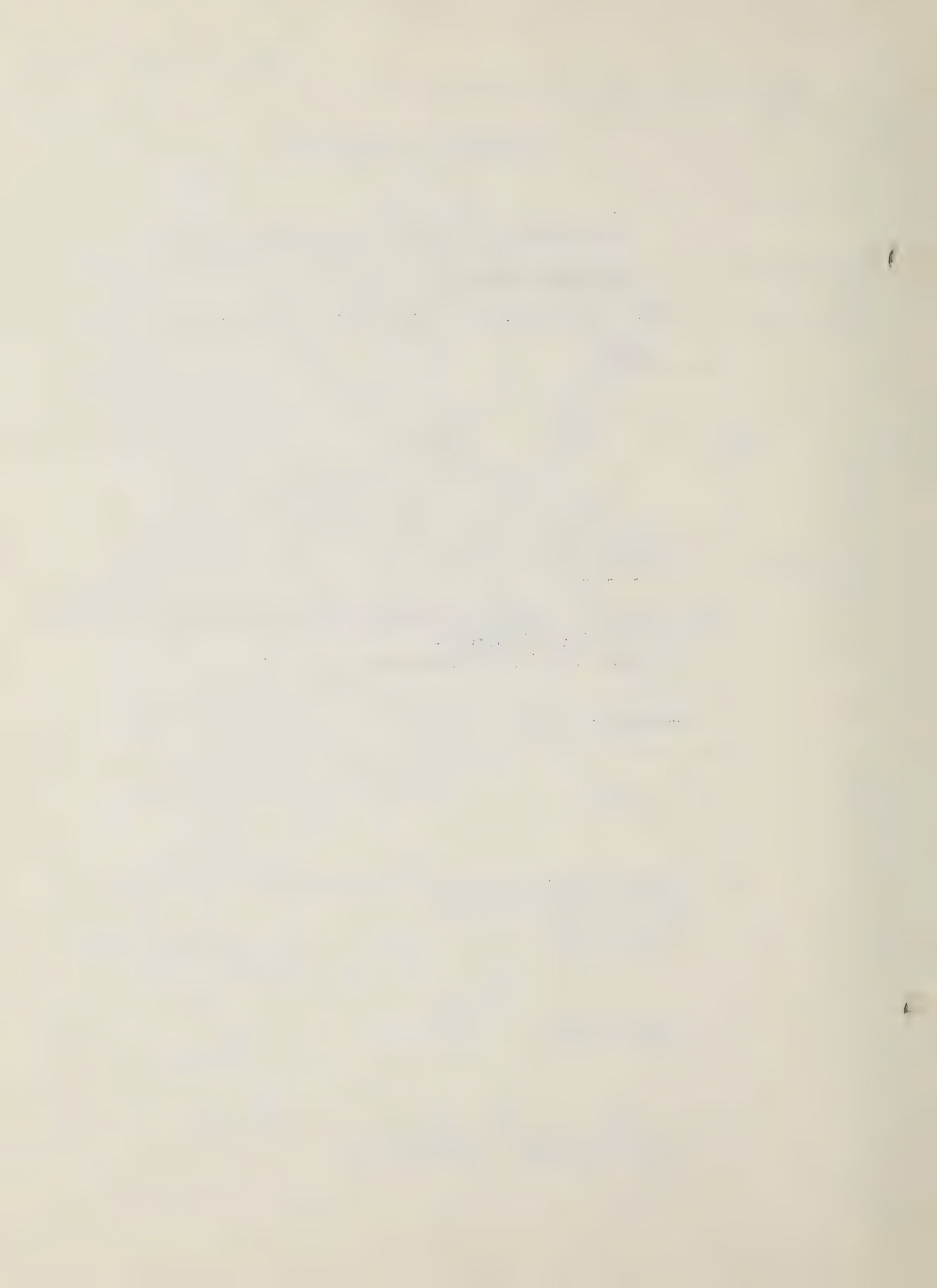

Job Sheet--AC-DC Power Supply (Cont.)


Summary Questions:

1. Why is this type of power supply called AC-DC?
Because it can work either from an A.C. or D.C. source.


2. What is the relation between load and size of filter capacitors?
The size of the load will determine the value of the capacitors
Heavy load-----Large capacitor
Light load-----Small capacitor

3. What is the relation between filter resistor and load?
The size of load will determine the value of the filter resistor
Heavy load----- Small resistor
Light load-----Bigger resistor

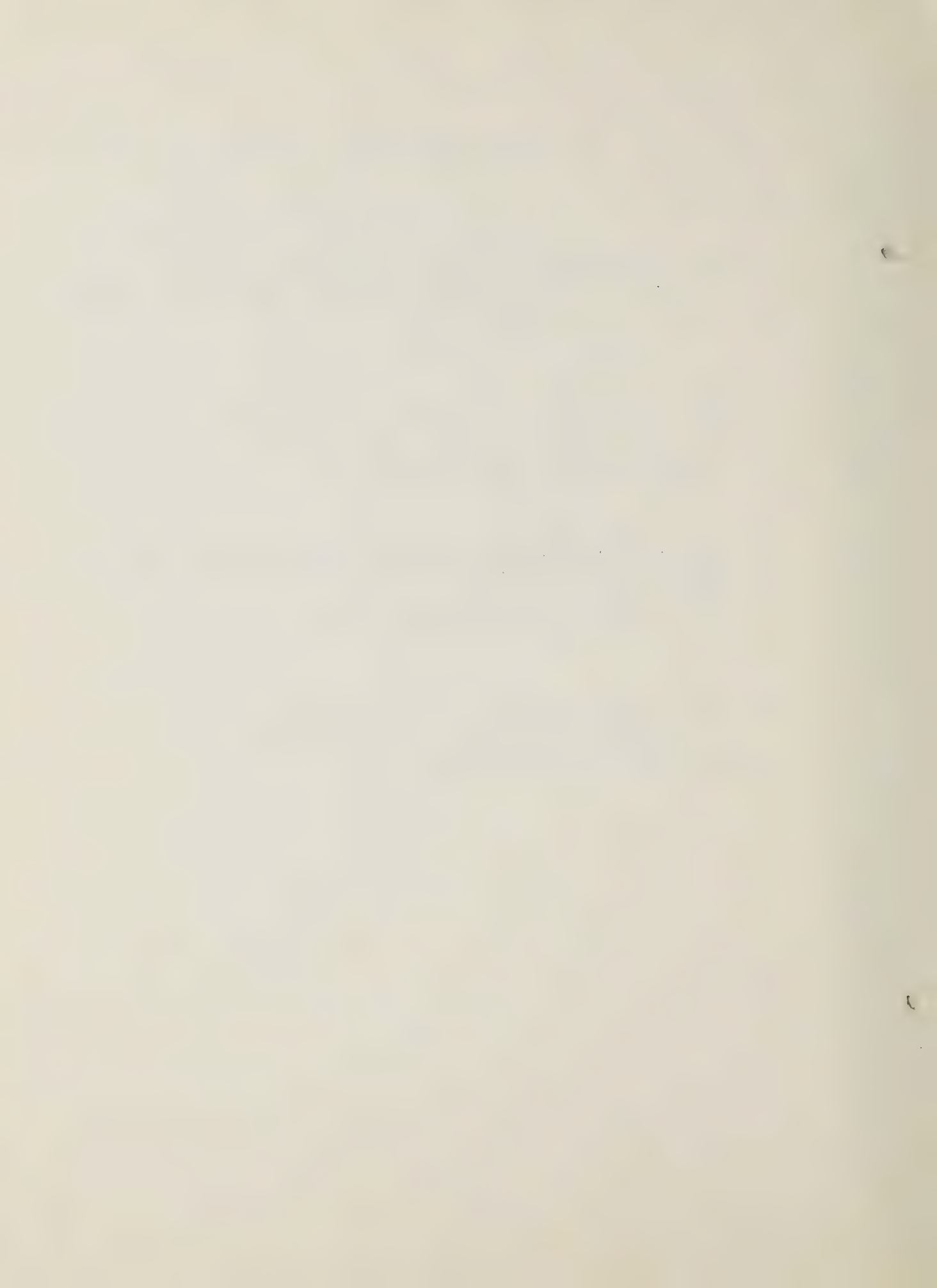
4. What is the purpose of the 50 ohm resistor?
To protect the tube from the surge of current when the filter capacitor starts charging.




NON-SYNCHRONOUS VIBRATOR

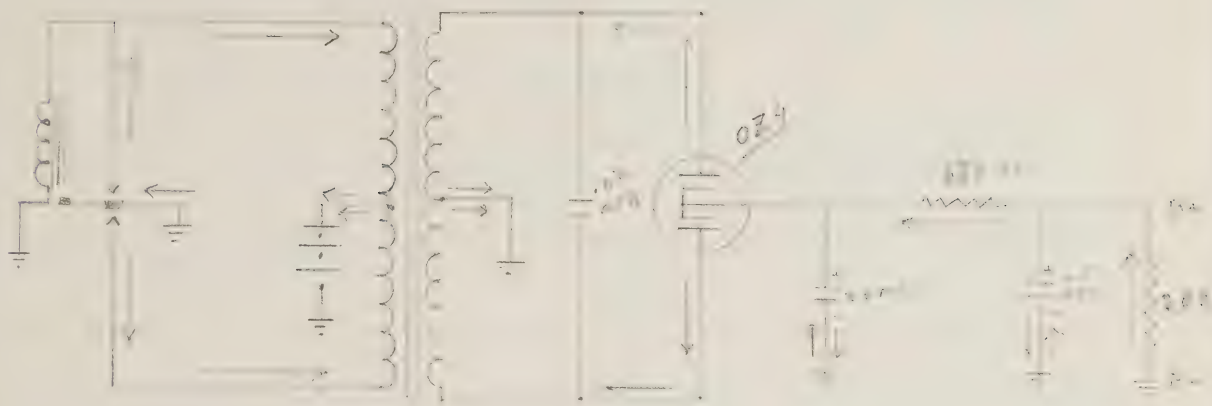

SYNCHRONOUS VIBRATOR

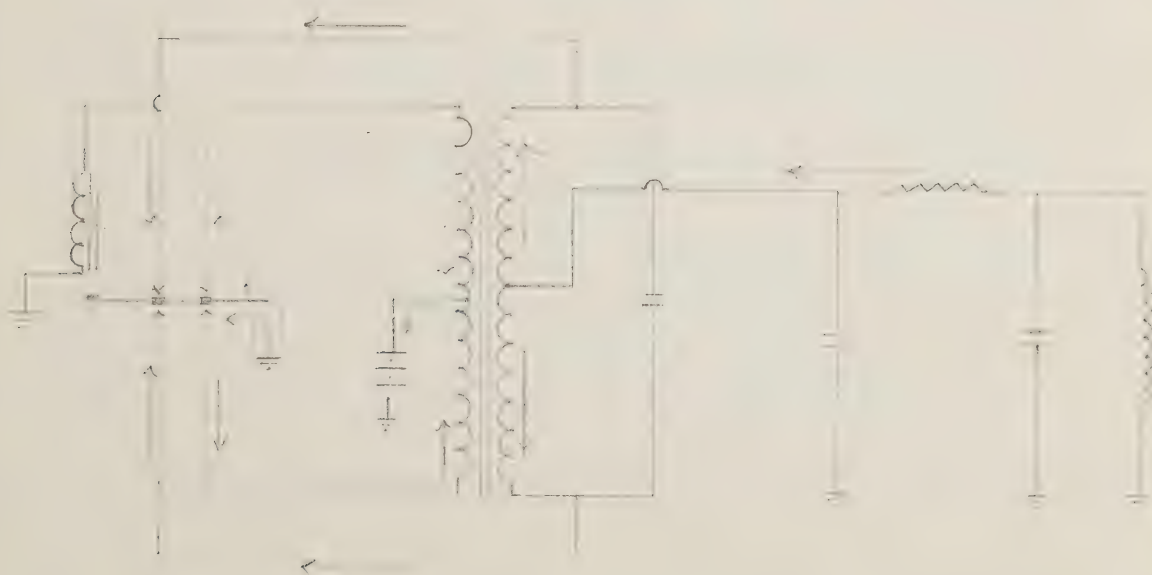

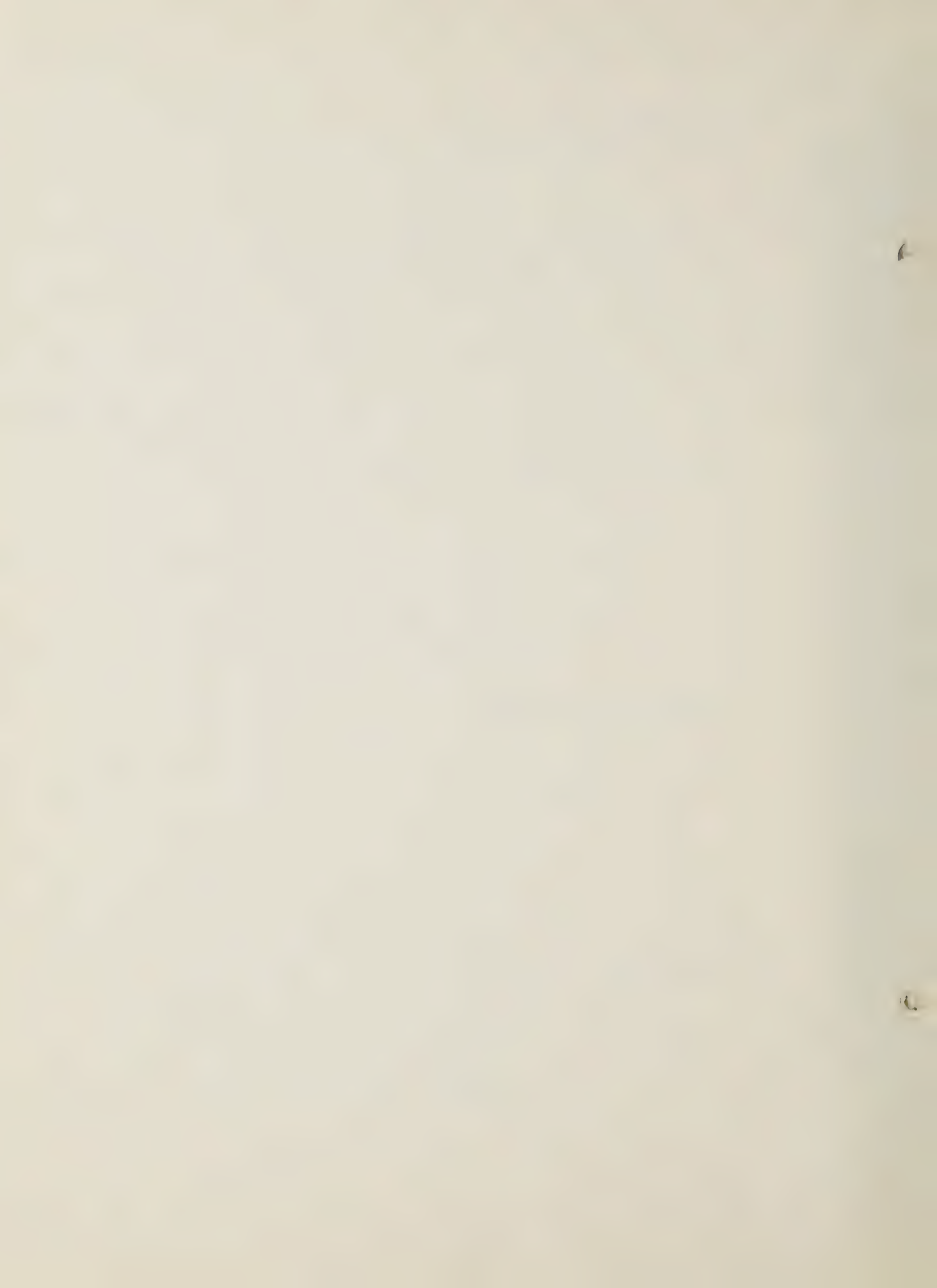

ELECTRONICS TECHNICIAN

JOB SHEET

Vibrator Power Supplies

Objective: How to Test and Service vibrator power supplies.

Materials: Obtain synchronous and non-synchronous vibrator supplies, several sizes of buffer capacitors, and a bad vibrator.

Equipment: Oscilloscope and battery eliminator.


Procedure. Draw schematics of both power supplies (use form).
With arrows show flow of current for each alternation.

Place oscilloscope across primary of the power transformer and observe waveforms.

Replace vibrator with bad one and observe waveform.

Shunt buffer capacitor with additional ones again observe waveforms.

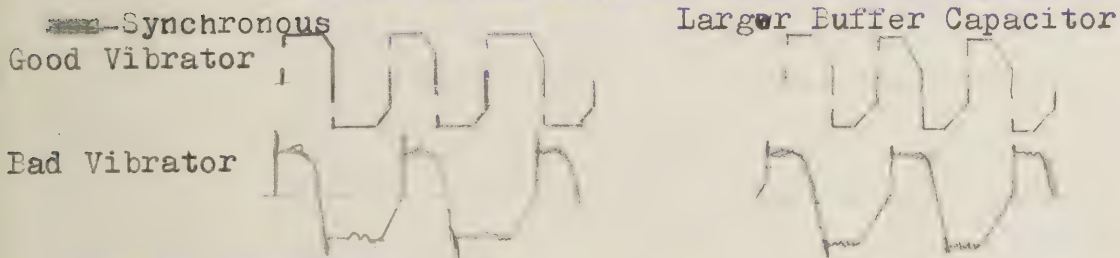Waveforms for vibrator and buffer capacitor checks:





Summary Questions:

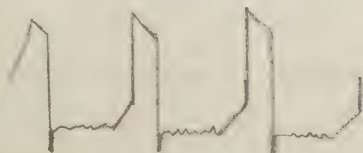1. What is the frequency of most vibrator power supplies?
115 c.p.s.
2. What is the purpose of the buffer capacitor? To prevent the C.M.F. on the secondary from damaging the points of the vibrator
3. Explain your procedure for locating a short in first the the buffer capacitor and second the B+.

First, pull out the rectifier tube. This will isolate the transformer from the B+ line. Next check with ohmmeter for shorts in the B+ components. If the buffer is shorted, after pulling out the tube the short will still show. The next step to disconnect the buffer and see if the short is still in the power supply. Any component can be checked the same way .

On the ^{non}Synchronous Vibrator Supply, due to faulty vibrators this is the only wave form I was able to get.



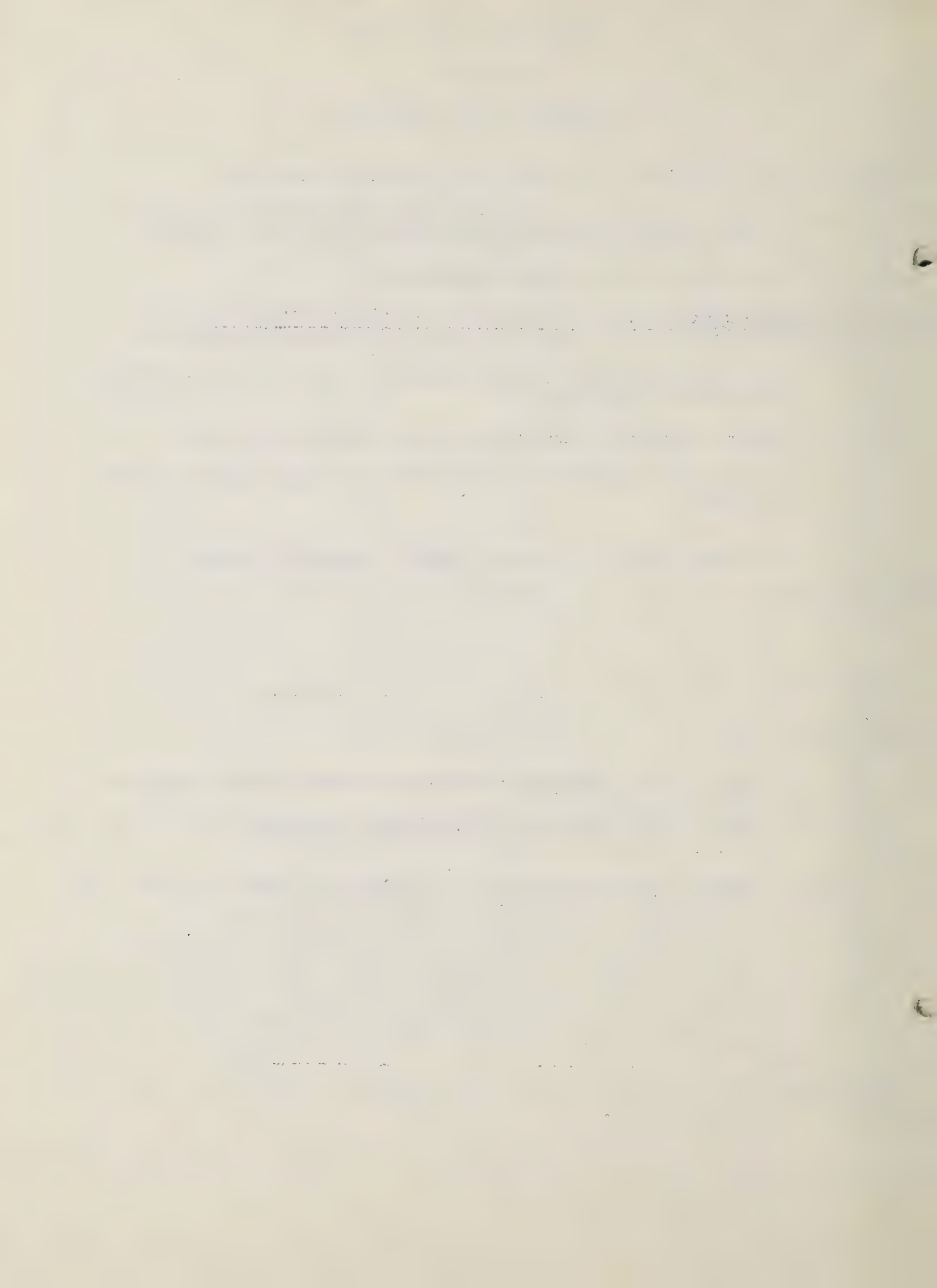

...the buffer mechanism. ...
 ...the power contact period, A1 the inertia swing ...
 ...contact period, and A2 the power swing period. Vibrator ...
 ...across the primary of the power transformer.
 ...contact at point 2 opens an induced voltage set up by the ...
 ...of the transformer would ordinarily create a high peak ...
 ...point and cause a burning arc to occur at the contact points. ...
 ...this peak voltage charges the buffer condenser, which shock ...
 ...circuit formed by the condenser and the effective inductance ...
 ...is started at point ...
 ...continues as shown by the dotted line, except that the inertia ...
 ...close at point 3 completely damping the rest of the oscillations ...
 ...the opening of the inertia contact causes the same effect to take ...
 ...for the other half of the cycle.

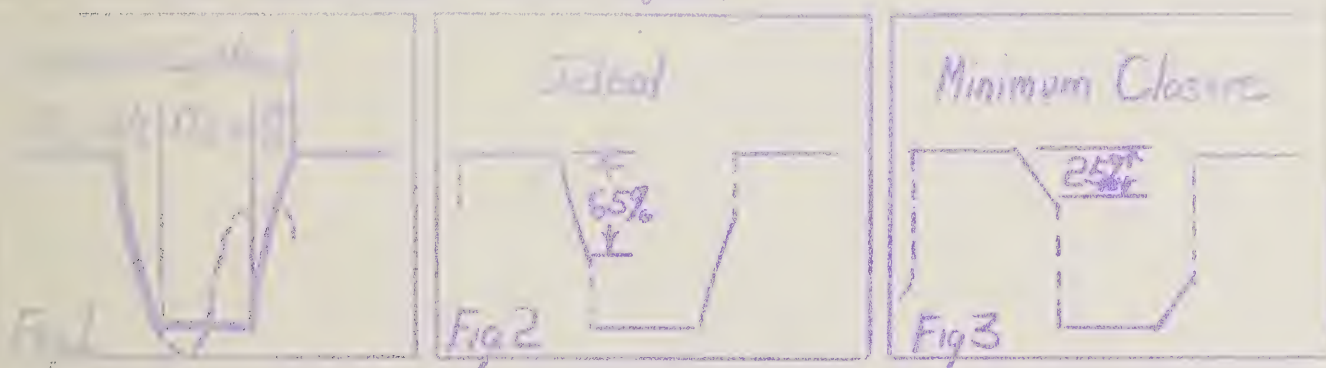




Fig. 2 illustrates the ideal practical value of choosing a buffer ...
 ...to give 65% closure. Increasing the primary voltage also increases ...
 ...of closure (less time on contact period) and since the average ...
 ...circuits vary from 5.5 to 7.5 volts, selecting a primary ...
 ...6.3 volts will compensate for this range. 25% is the ...
 ...as shown in fig. 3.

Fig. 3 and 4 show overclosure caused most likely by worn contacts.
(Worn contacts increase the swing of the reed thus prolonging the off-contact time).


When inertia contacts are entirely worn off the effect is known as "single-footing" and is shown in figs. 5 and 6.

Figs. 7, 8, and 9 are for conditions of vibrator contacts.

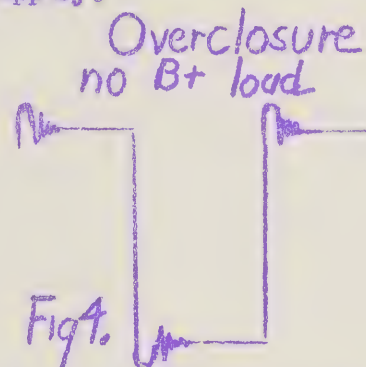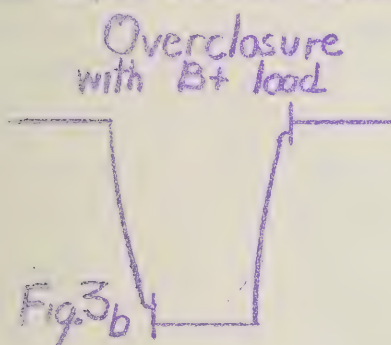For fig. 10 remove the scope from the primary of the power transformer to the input filter condenser of the "B" supply.



Single-Footing-B+ Load

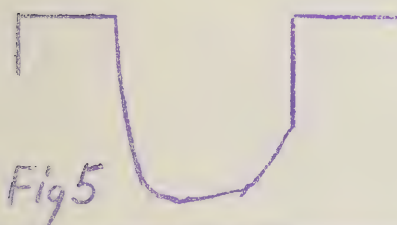

Single-Footing No B+ Load


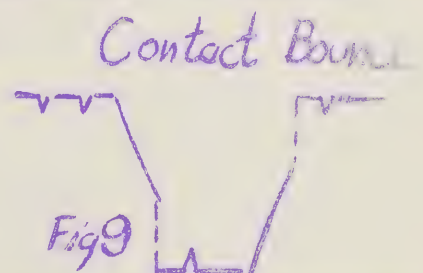
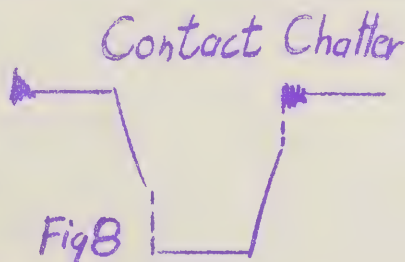
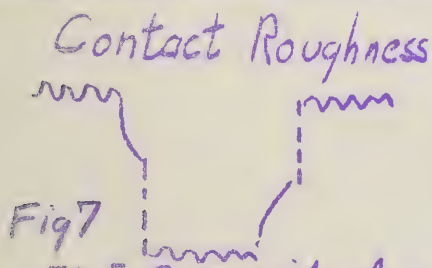
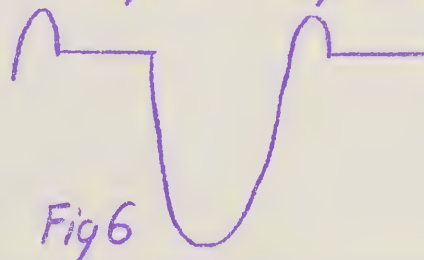


Fig 7+8 considered minor-

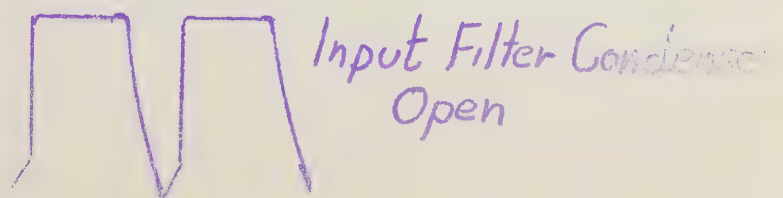


TECHNICAL ASSIGNMENT SHEET

Load Lines

Reference: Principles of Radio-Receivers: Electron Tubes--Army T.O.

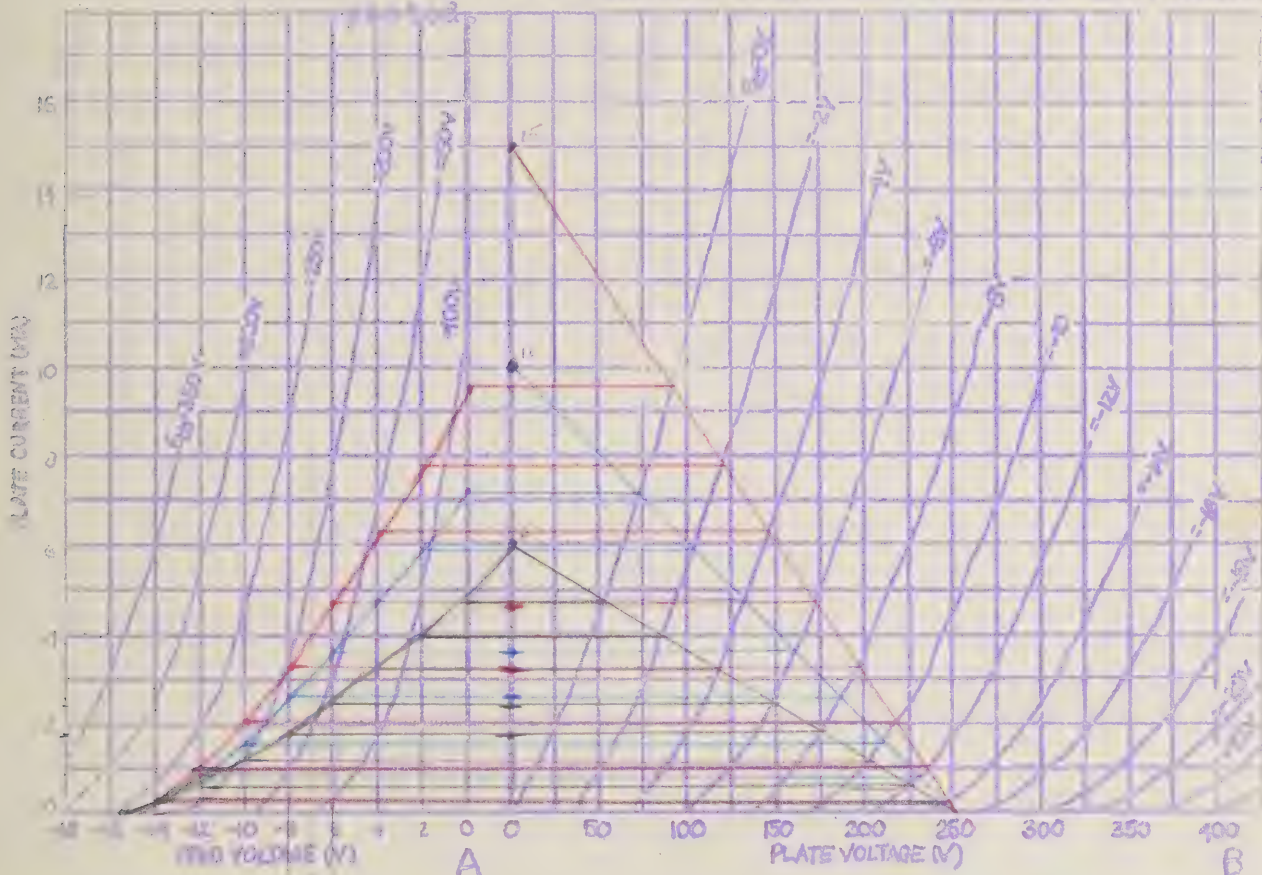Introduction: The electronics technician that becomes employed in the area of design of amplifiers (engineering aide) must understand the dynamic conditions that exist. The use of load lines will determine the results that can be expected.



Assignment: Construct load lines for three different loads using a 250 volt plate supply. Transfer all three to the grid characteristic chart.

A - 6 ma. 41.3 K. B - 10 ma. 25 K. C - 15 ma. 16.7 K.

Tests:

1. What is the output signal for each load with an input signal of 2 volts P.P. ? (choose bias for linear operation)

A = 3.0 P.P.T.

A - .75 ma. $41.3 K \times .75 \text{ ma} = 30.8 \text{ V}$. B = 1 ma. $25 K \times 1 \text{ ma} = 25 \text{ V}$.

B = 2.5 P.P.T.

C = 1.5 ma. $16.7 K \times 1.5 \text{ ma} = 25 \text{ V}$.

C = 3.0 P.P.T.

2. What is the gain in each case?

A = 15.0 dB

B = 12.0 dB

C = 12.0 dB

3. With respect to gain, what is the general rule of the size of the load resistor?

To a certain point, as the value of the load resistor increases, the gain increases.

After a certain point, the gain decreases as the load resistor increases.

At a certain point, the gain is maximum.


ELECTRONICS TECHNICIAN

TOP SECRET

Voltage Amplifiers--Triode

Objective: How to construct and measure performance of voltage amplifier and characteristics of vacuum tubes using the tube manual.

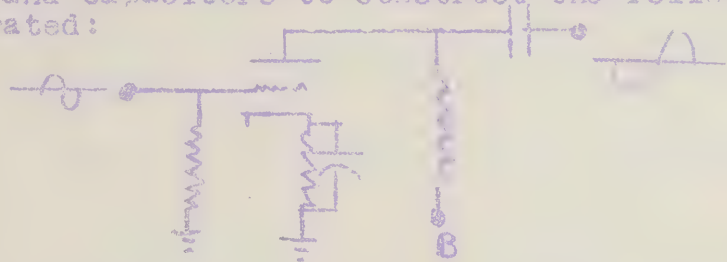Materials: Resistors and capacitors to construct the following amplifier as illustrated:



Equipment: Oscilloscope, VTVM, and audio signal generator, and construction boards.

Procedure: Consult instructor for selection of four triode tubes to be used as voltage amplifiers.

With the aid of the tube manual construct one at a time a circuit for each tube using the circuit construction boards. Design and alter components for each circuit for maximum output with B+ supply available.

List the following characteristics for each tube:

1. Filament voltage.
2. Amplification factor.
3. Transconductance.
4. AC plate resistance.

Draw a schematic for each circuit and label the following:

1. B+
2. Values of components.
3. Plate voltage.
4. Bias voltage.(cathode)

List the following characteristics for each amplifier:

1. Voltage gain. (use 1000 cycles as standard)
2. Maximum undistorted input and output peak to peak voltage.


Summary Questions:

1. What affect on gain does increasing the size of the load resistor have? Why?
2. Describe the action and purpose of the cathode by-pass capacitor.
3. What affect will too small a coupling condenser have on the over all performance of the amplifier?
4. How is phase inversion accomplished in an amplifier?

VOLTAGE AMPLIFIERS JOB SHEET

SUMMARY QUESTIONS :

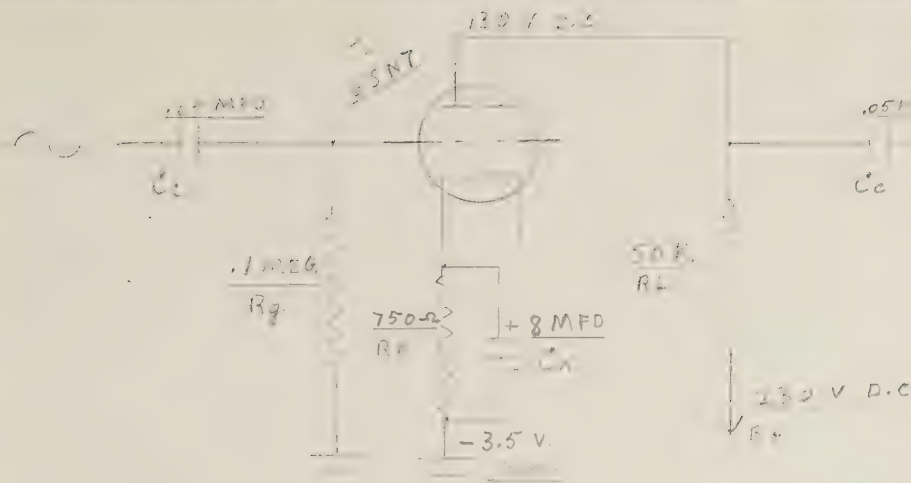1. Increasing the size of the load resistor will increase the gain, because the " $I_p R_L$ " drop will be greater, therefore a greater change will be developed across R_L .
2. The purpose of the cathode capacitor is to keep the voltage across the resistor (R_k) constant. To do this, the capacitor charges on the positive swing of the plate current change and discharges through the resistor on the negative swing.
3. Too small coupling capacitor will discriminate against the low frequencies.
4. The plate voltage is 180 degrees out of phase with the signal voltage. When the signal voltage goes positive more current flows in the plate circuit, therefore the plate voltage goes down and vice-versa. Giving 180 degrees phase inversion.




TUBE CHARACTERISTICS:

Filament Voltage: 6.3
 Amplification factor: 20
 Transconductance: 2600 umhos
 A.C. Plate resistance: 7.7 K.

AMPLIFIER CHARACTERISTICS:

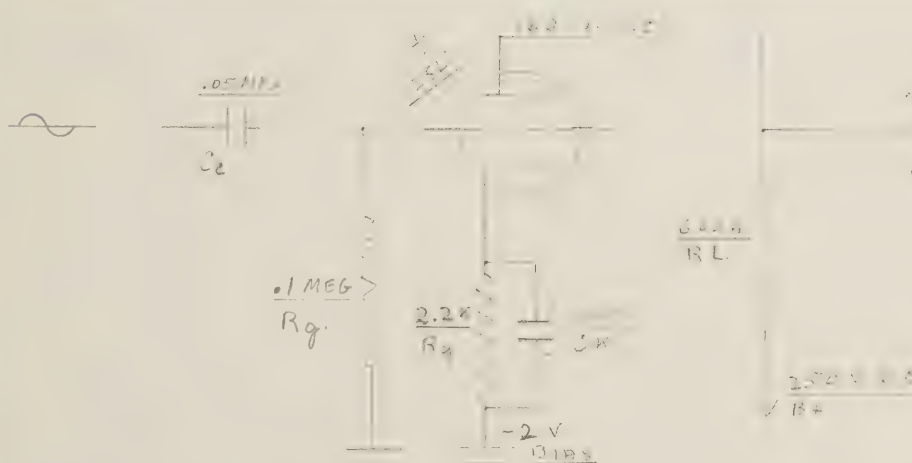Input Signal: 5.5 Volts A.C. P. to P.
 Output Signal: 77 Volts A.C. P. to P.
 Gain: 14
 Maximum undistorted input: 12 Volts A.C. P. to P.
 " " output: 165 Volts A.C. P. to P.



TUBE CHARACTERISTICS:

Filament Voltage: 12.6 Volts
 Amplification factor: 70
 Transconductance: 1600 umhos
 A.C. Plate resistance: 44 K.

AMPLIFIER CHARACTERISTICS:

Input Signal: 3 Volts A.C. P. to P.
 Output Signal: 113 Volts A.C. P. to P.
 Gain: 37.6
 Maximum undistorted input: 4 Volts A.C. P. to P.
 " " output: 140 Volts A.C. P. to P.

LOS ANGELES TRAFFIC CONTROL COLLECTOR

LOS ANGELES, CALIF.


ELECTRONIC CUBES

AVP

AGUSTIN LUCAS

DEC-1-1956

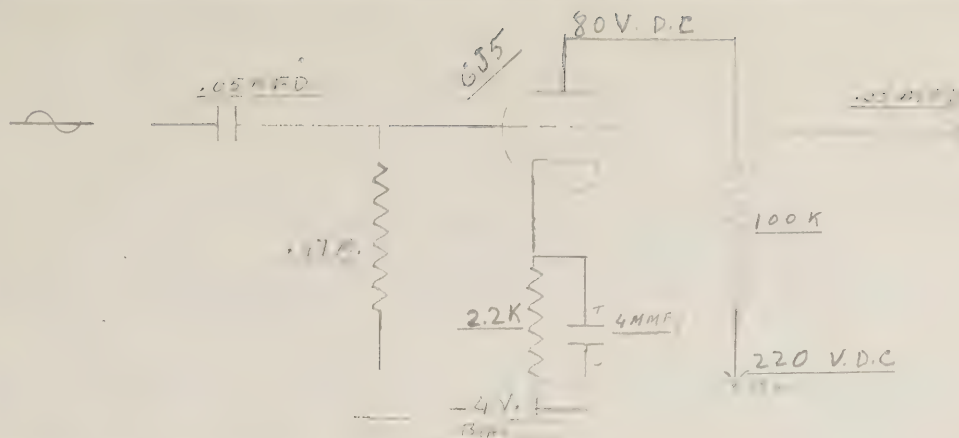School of Los Angeles Radio Institute
 Los Angeles, California
 Class: Electronics
 Approved By: AUGUSTIN LUCAS
 DATE: DEC-1-1956




TUBE CHARACTERISTICS:

Filament Voltage: 6.3
 Amplification Factor: 20
 Transconductance: 2600 umhos
 A.C. Plate resistance: 7.7 K.

AMPLIFIER CHARACTERISTICS:

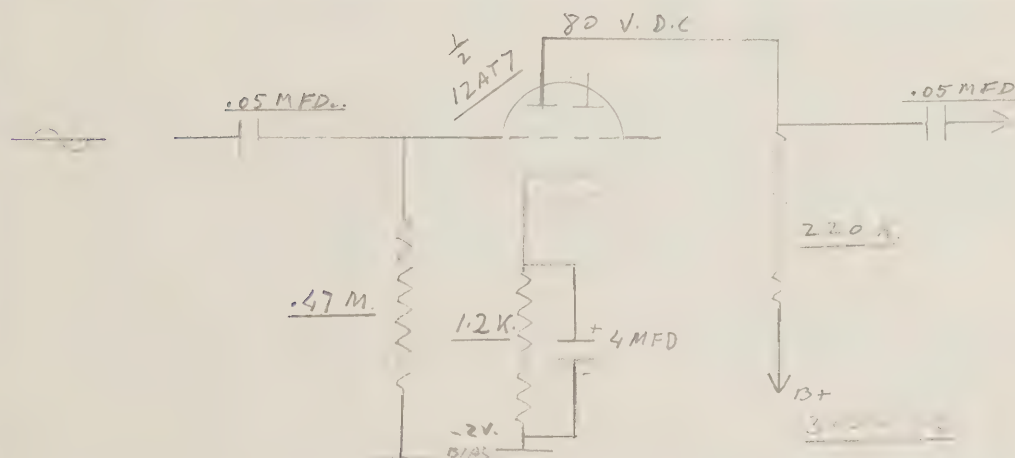Input Signal: 5.5 Volts A.C. P. to P.
 Output Signal: 85 Volts A.C. P. to P.
 Gain: 15.6
 Maximum undistorted input: 15.5 Volts A.C. P. to P.
 " " output: 198 Volts A.C. P. to P.



TUBE CHARACTERISTICS:

Filament voltage: 12.6
 Amplification factor: 60
 Transconductance: 5500 umhos
 A.C. Plate resistance: 10.9 K.

AMPLIFIER CHARACTERISTICS:

Input signal: 3 Volts A.C. P. to P.
 Output signal: 85 Volts A.C. P. to P.
 Gain: 28.3
 Maximum undistorted input: 9 Volts A.C. P. to P.
 " " output: 240 Volts A.C. P. to P.


ELECTRONICS TECHNICIAN

JOB SHEET

Vacuum Tube Characteristics

Objective: How to determine the characteristics of a vacuum tube and voltage amplifiers.

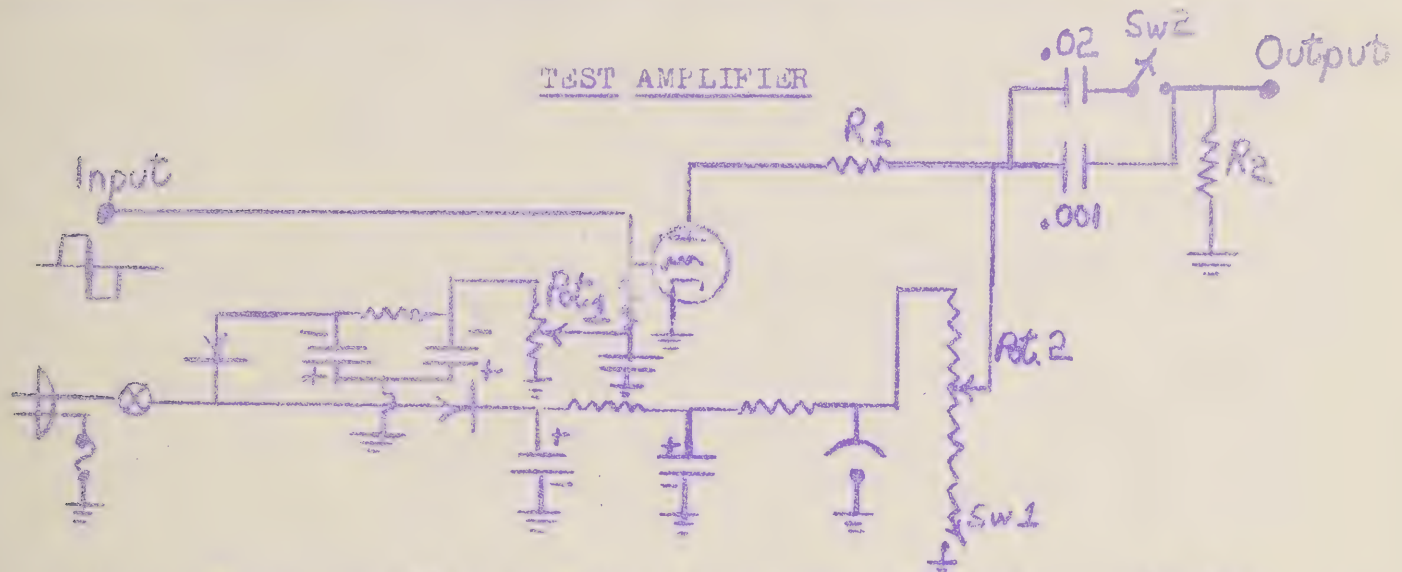Equipment: Oscilloscope, voltmeter, square and sine-wave audio generator, and test amplifier.



Procedure: Study amplifier and its above circuit, and consult the instructor before going further. Instructor's OK JS (initial)
For the following use graph paper--log for freq. response.

- ✓ 1. Close Sw. 1, turn pot. 2 to B+ side, put voltmeter across R-1, and vary grid bias with pot. 1. With this information draw a grid characteristic curve.

- ✓ 2. From information obtained from above pick a grid bias voltage and vary pot. 2. From this draw a plate characteristic curve.

- ✓ 3. Open Sw 1, connect generator to input and oscilloscope to output. Vary grid bias, plate load, and the sine-wave output from generator at 1000 cycles. Draw waveforms for class A, B, and C. What effect is noticed by varying the plate load?

THE OUTPUT IS ALSO VARIED AND DISTORTED

- ✓ 4. Run a frequency response and draw the curve. Use sine-wave output. Close Sw 2 and draw another response curve.

3. Change generator from sine-wave to square-wave at 500 cycles. Draw waveforms with Sw 2 open and closed.

Summary questions:

1. What is the phase relation between input signal and output plate voltage and plate current?

THE PLATE VOLTAGE IS 180° OUT OF PHASE WITH THE INPUT SIGNAL.


2. If an amplifier has poor high frequency response, what should a square-wave in the output look on the scope? Poor low frequency response?

CURVES DRAWN ON SEPARATE SHEET.

3. What effect did the increase in the size of the coupling capacitor have on the frequency response?

IT INCREASED THE RANGE OF THE FREQUENCY RESPONSE, ESPECIALLY AT THE LOW END.

INPUT - 1000 CYCLES

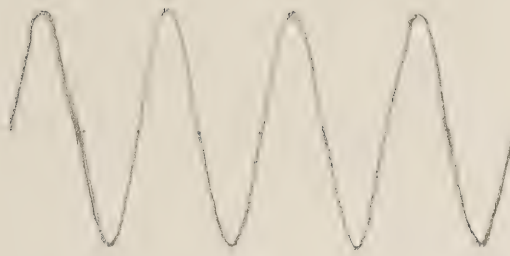

CLASS A WAVE FORM



CLASS B WAVE FORM




CLASS C WAVE FORM

SQUARE WAVE INPUT - 500 CYCLES



SW-2 OPEN - SMALL C_2

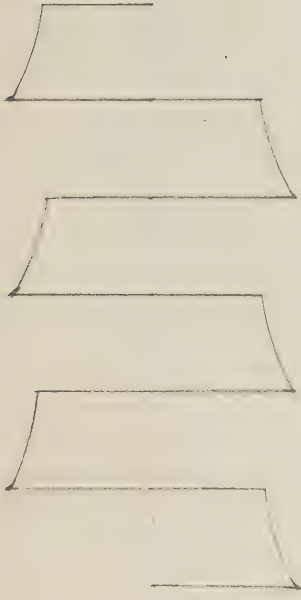

SW-2 CLOSED - LARGE C_2

FREQUENCY RESPONSE CURVES



POOR LOW FREQUENCY RESPONSE





POOR HIGH FREQUENCY RESPONSE

U.S. AIR FORCE COLLEGE OF ENGINEERING, WAVE FORMS

AGUSTIN LUCAS

JAN-3-1957

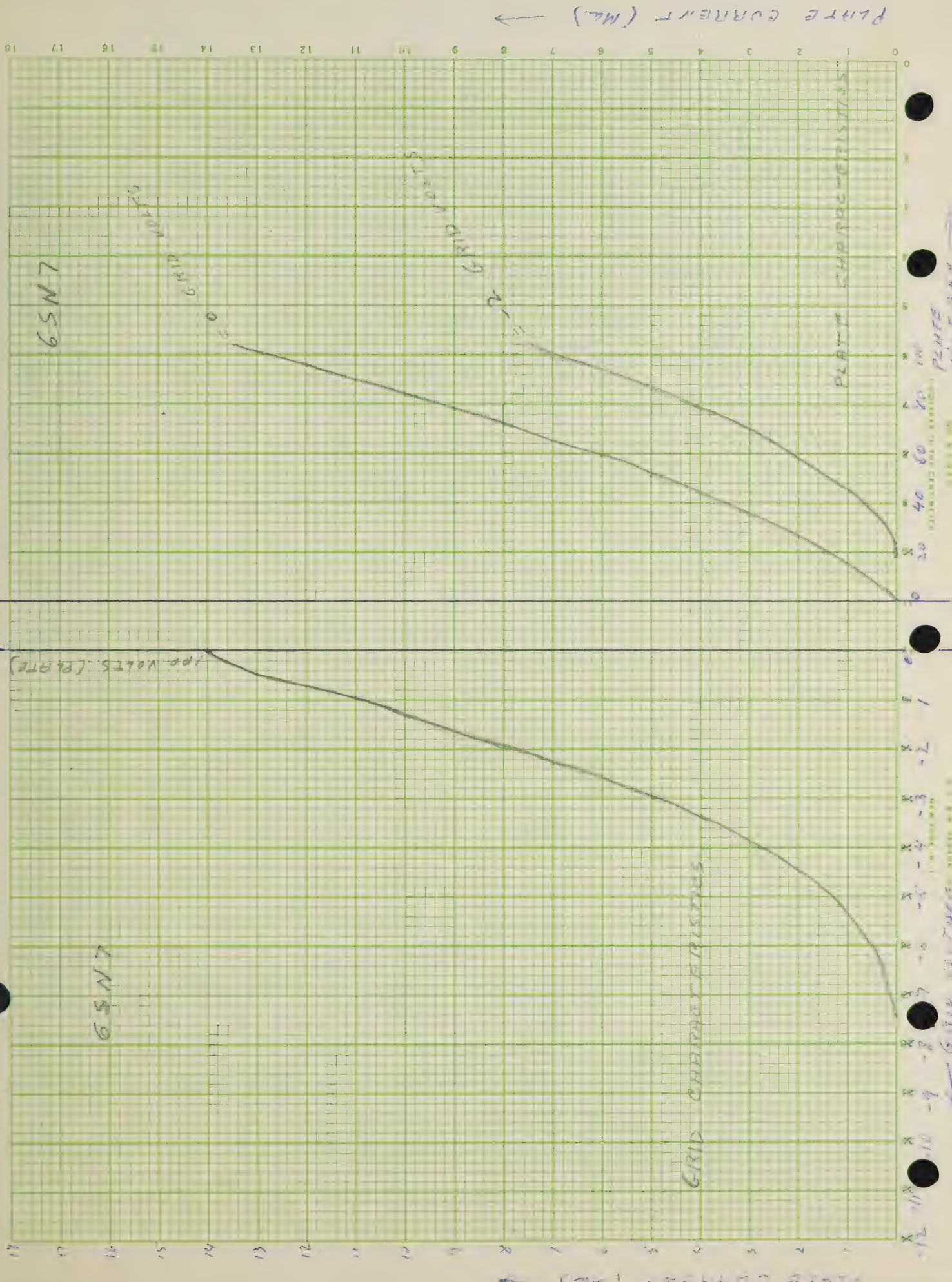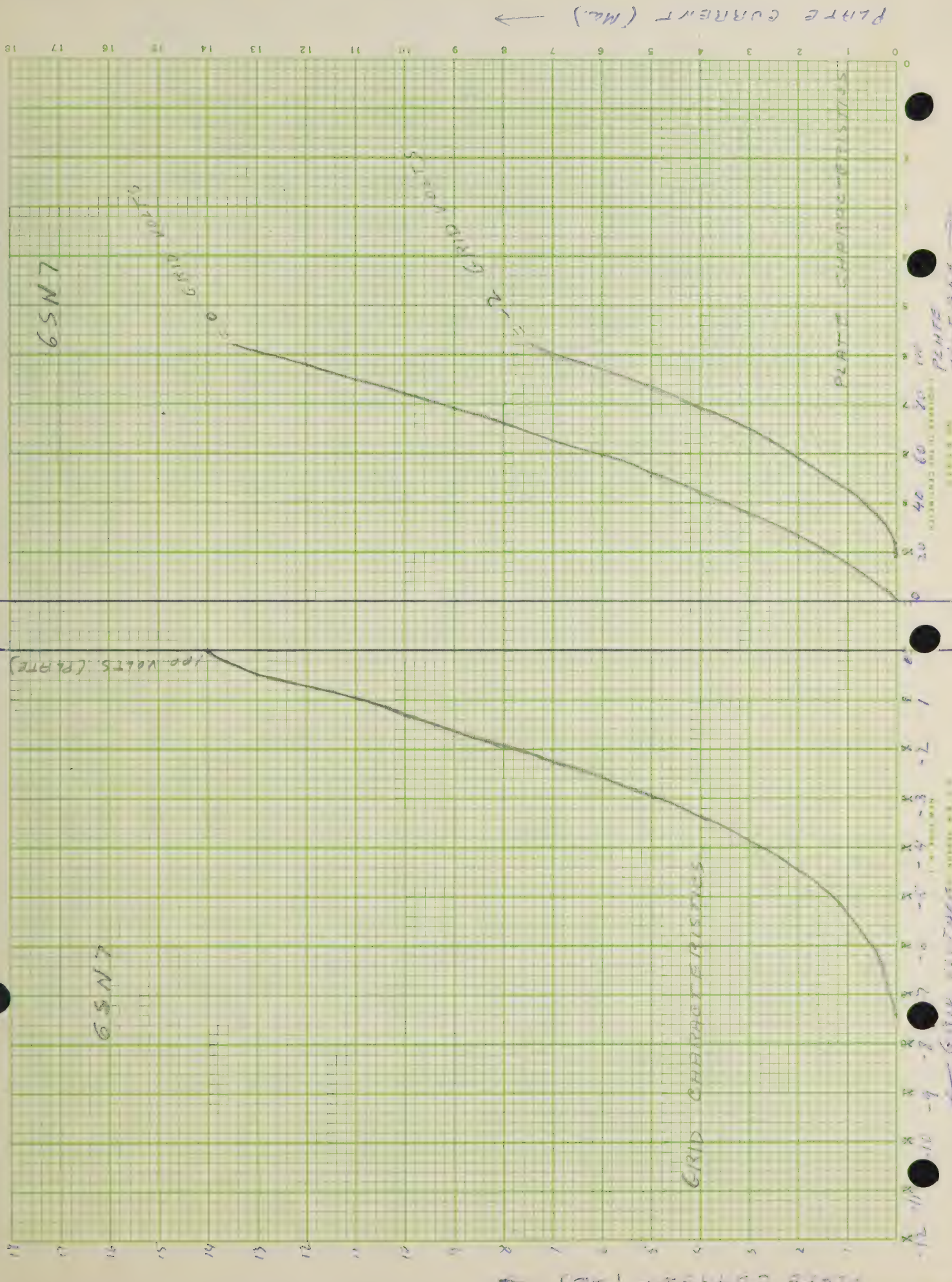


JOB SHEET

Phase Inverters

Abstract: How to recognize, test and measure the performance of standard phase inverter circuits.

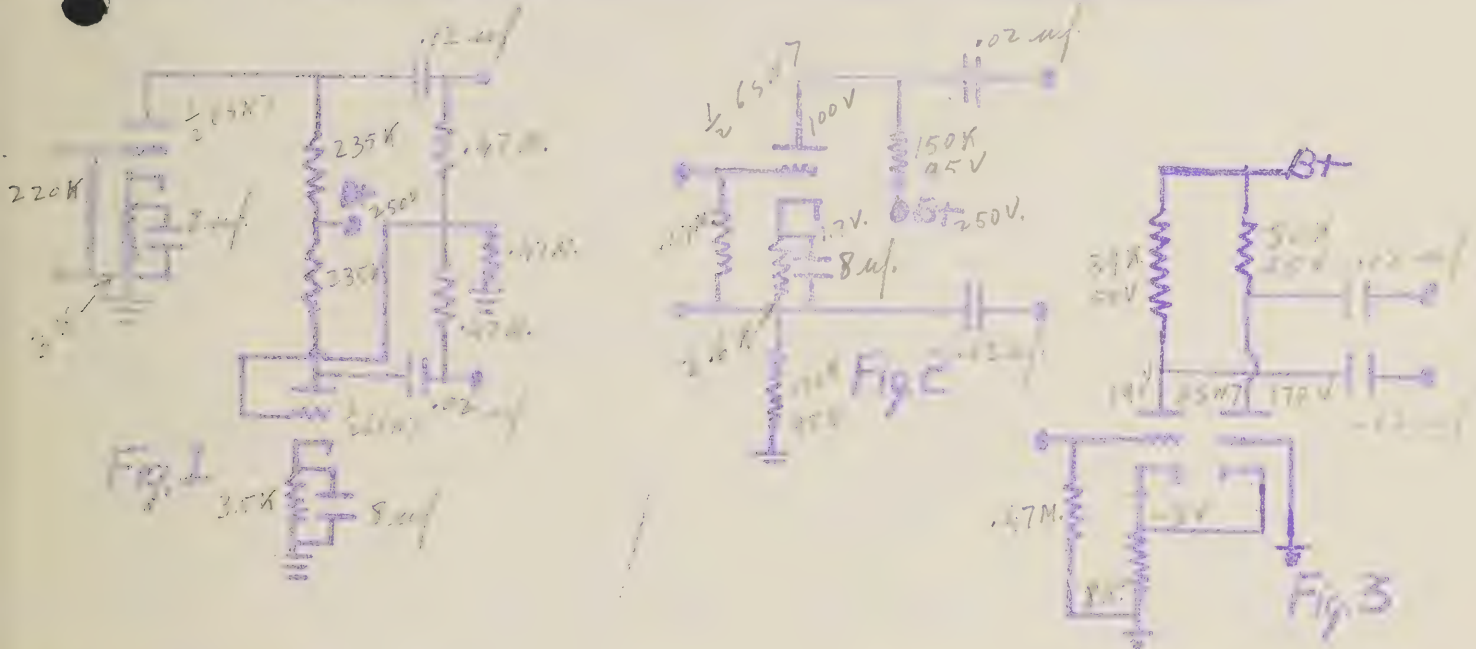Materials: Components and parts to build the following circuits:



Equipment: Audio generator, Oscilloscope and VTVM.

Procedure: With the aid of tube manuals, references, notes and calculations determine the value of each component. Label each circuit and value of each component. Insert signal of proper value from generator. With oscilloscope determine the amplitudes of both outputs for each type. Check to see that they are equal.

Summary Questions:

1. What is the chief purpose of phase inversion?

To obtain two signals of equal amplitude and 180° out of phase so they can be fed to a push-pull stage.

2. If there is no signal from one of the outputs of a phase inverter, what would the signal look like in the output stage?

A wave of smaller amplitude


3. Explain in detail how phase inversion is accomplished in each type used in this job sheet.

Fig. 1 Self balancing: On this type, phase inversion is accomplished by using two tubes, one acts as an amplifier and the other as the phase inverter. The output of both tubes flows through a voltage divider composed of the grid resistors of the push-pull stage connected to ground through a common resistor. The voltage drop across this resistor is the algebraic sum of both outputs and it is the input signal to the phase inverter. If the output of the amplifier varies, this voltage will vary in proportion, changing the output of the phase inverter to the same amplitude but 180 degrees out of phase.


Fig. 2 Split load: On this type, phase inversion is accomplished by splitting the load of the tube. One output is taken off like from a straight amplifier, the other is taken from the second half of the load, which is in series with the R_k . Since the plate current flows through both equal RL in series both outputs are equal, and 180° out of phase because, one is taken from the negative side of the load and the other from the positive side.

Fig. 3 Grounded grid: Phase inversion is done by a duo triode or two triodes. Both cathodes are connected to ground by a common unbypassed resistor. The grid of the phase inverter is grounded placing it at a more negative potential than the cathode. The voltage across the R_k is developed by the algebraic sum of both plate currents and it is the signal applied to the inverter. Since the cathode potential will be changing at the same time that the amplifier grid, the action of the tube will be reversed giving an output which is 180° out of phase. If the R_k is the proper size it should give a voltage with an amplitude which is half the amplitude of the voltage applied to the amplifier grid.

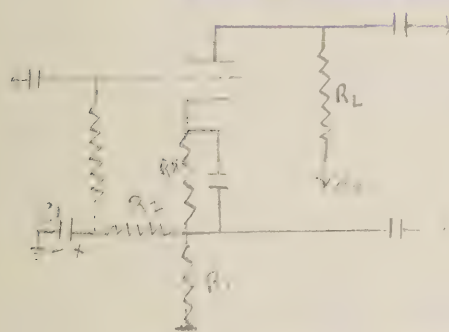4. Describe and draw the schematics for two other methods of phase inversion:



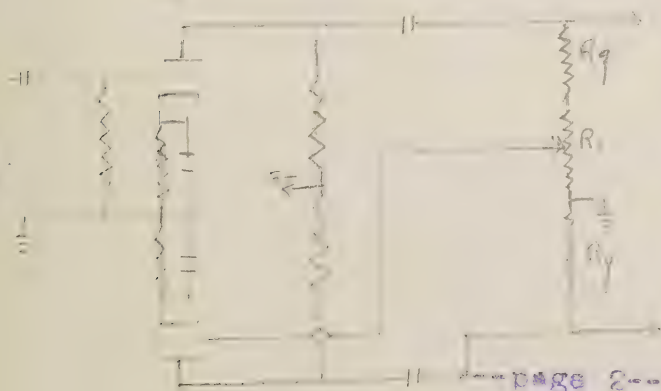4. This is a variation of the split load inverter to permit a grounded input. R_1 , R_2 and C_1 form a parallel circuit as far as the signal is concerned therefore R_1 and R_2 must be equal and double the size of R_L . C_1 must be fairly large to pass all the audio frequencies.



5. This is a variation of the self balancing inverter. This inverter must be balanced manually. The signal input for the inverter is taken off the "pot" R_1 , which is part of a voltage divider. The amount of voltage tapped must be adjusted so that the output of the inverter is of equal amplitude that the output of the amplifier.

JOB SHEET


Pentode Voltage Amplifier

Objective: To calculate practical values of components for pentode voltage amplifiers, and be able to construct and test.

Materials: To construct amplifier as shown.

Equipment: Audio generator and oscilloscope.

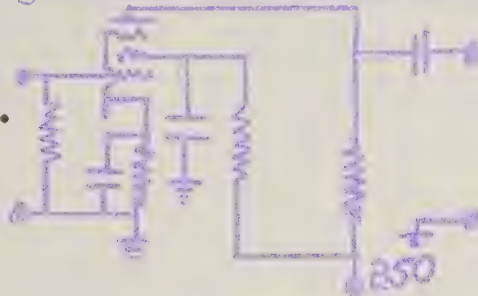Input .4 Pto P.
Output 100 P. to P.
Gain 250



Rg---.47 Meg.
Rk---560 Ohms
Rsc---.4 Meg.
RL---125 K.
Ck---8 ufd.
Csc---.22 ufd.
Cc---.05 ufd

Procedure: Select one of the following tubes to construct the above amplifier: 6BN7, 6SK7, 6AU6, and 6AG5.

With aid of tube manual design circuit to give the maximum output with a supply of 250 volts.

Connect audio generator to input and oscilloscope to output. Determine maximum V.G. --undistorted.

Raise voltage on screen by parallel resistor across screen resistor--check V.G. Increased

Summary Questions:

1. Why do pentodes have a high plate resistance? Because a greater change in plate voltage is needed to produce a small change in plate current.

2. What is the range of amplification factor of pentodes?
Up to 1500

3. Compare Triodes And Pentodes as follows: advantages, disadvantages, and characteristics.

The main advantage of the pentode over a triode is the lower interelectrode capacitance and greater amplification. Also in a pentode amplifier a smaller input signal can be used, due to the fact that the control grid has more control on the plate current. The pentode has more distortion than a triode because of a smaller linear portion in the characteristics curve. (Eg I_p)

ELECTRONICS TECHNICIAN
JOB SHEET

The Decibel

Objective: How to use decibels.

Materials: Load resistor for amplifier.

Equipment: Audio amplifier, audio oscillator, and AC voltmeter.

Procedure: Insert $\frac{1}{2}$ volt signal into amplifier and calculate power input and output. Use 1000 cycles as standard.
Repeat above for 1 and $1\frac{1}{2}$ volt input.

$R = 1M$

$\frac{1}{2}$ V. INPUT - $P = \frac{E^2}{R} = \frac{.5^2}{10^6} = .25 \mu W$; OUTPUT $5.8V$; $\frac{5.8^2}{8} = 4.205 W$
 $R = 8 \Omega$

1 V INPUT - $\frac{1^2}{10^6} = 1 \mu W$; OUTPUT $7.7V$; $\frac{7.7^2}{8} = 7.41 W$
 $R = 8 \Omega$

$1\frac{1}{2}$ V. INPUT $\frac{1.5^2}{10^6} = 2.25 \mu W$; OUTPUT $8.5V$; $\frac{8.5^2}{8} = 9.03 W$
 $R = 8 \Omega$

Calculate the db gain for each case.

GAIN.

1 - $DB = 10 \log \frac{4.2}{2.5 \times 10^{-7}} = \log 1.68 \times 10^7 = 7.2253 \times 10 = \underline{72.22 DB}$

2 - $DB = 10 \log \frac{7.41}{10^{-6}} = \log 7.41 \times 10^6 = 6.8698 \times 10 = \underline{68.7 DB}$

3 - $DB = 10 \log \frac{9.03}{2.25 \times 10^{-6}} = \log 4.01 \times 10^6 = 6.6031 \times 10 = \underline{66.03 DB}$

Summary Questions:

1. What is the difference between db and dbm?

DB is used with a reference level. DBM is used with a reference level of 1 milliwatt.

2. An amplifier has a rated output of 80 watts, what is the db gain with a 6 milliwatt zero reference?

$DB = 10 \log \frac{80}{.006} = \log 13333.33 = 4.1249 \times 10 = \underline{41.22 DB}$

3. What is the wattage output of a device with a gain of -15dbm?

$-15 DBM = 10 \log \frac{X}{.001} = -1.5 = \log \frac{X}{.001}$ ANTILOG 1.5 = .316

$\frac{X}{.001} = .316$; THEN $X = .001 \times .316 = \underline{.316 \mu W}$

$\frac{.316}{1000} = .000316$

Los Angeles Trade Tech. Jr. College
Instructor: H.H. Geffinger

JS-


ELECTRONICS TECHNICIAN

3 - SHEET

Voltage Regulation--Glow Discharge

Objective: How to test, measure and construct voltage regulators.

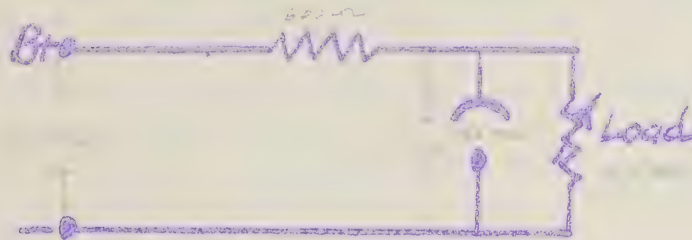Materials: To construct a voltage regulator as shown:



Equipment: Power supply, VTVM, and oscilloscope.

Procedure: Construct voltage regulator for a load within the range of the power supply and regulator tube.

Vary load and measure voltages:

$$3K = 90V - VR \text{ TUBE } 5VT$$

Vary AC input to power supply and record voltage output:

100 V	IN	VR TUBE OUT	100 V	OUT
110 V	IN	VR TUBE OUT	110 V	OUT
120 V	IN	VR TUBE OUT	120 V	OUT
130 V	IN	VR TUBE OUT	130 V	OUT

Connect oscilloscope to output of regulator. Vary filtering by removing a filter capacitor. Record waveforms of the effect that a regulator has on a DC ripple:

WITHOUT JS

WITH JS

Job Sheet--Voltage Regulation-Glow Discharge

Summary Questions:

1. Give your explanation of the characteristics of a glow discharge tube.

The amount of ionization of the gas in the tube varies with the amount of current that the tube conducts. If a high current is passed, the gas is highly ionized and the resistance of the tube is low, and vice-versa, therefore keeping the voltage across the tube fairly constant over a wide range of current.

2. How is the value of the series dropping resistor determined?

$R = \frac{E}{I}$. The voltage dropped across the resistor must be the difference between the input voltage and the rated voltage across the tube. The current used in the calculations is the maximum rated current of the tube.

3. To what type of circuits for regulation are the discharge tubes limited?

The VR tube is limited to low current circuits, since they are rated at a maximum of 30 Ma.

ELECTRONICS TECHNICIAN


JOB SHEET

TRANSFORMER LOADING

Objective: How to understand the effects produced when a transformer is loaded.

Equipment: Power transformer demonstration unit and battery eliminator.

Procedure: Connect equipment as shown:

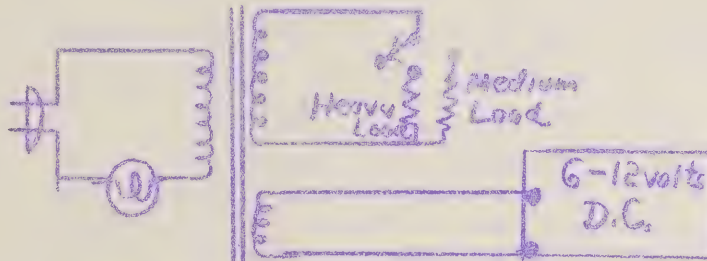

Plug in unit and observe lamp. Load up secondary with light and medium loads. Insert a DC current into one of the low voltage secondary windings. Increase current flow from DC supply until there is no effect noticed between a loaded or unloaded secondary winding.

Summary Questions:

1. Why is lamp dim with no loaded secondary?
(The power in the primary must equal the power in the secondary). If the secondary is open (no load) there is no current flowing, therefore no power is being consumed in either winding, so the lamp on the primary is dim.

2. Why does lamp increase with a loaded secondary?

With a loaded secondary there is current flowing and power is being consumed. The lamp lights brightly in the primary. If the load is increased, more current will flow and the light will also increase.

3. Why did the load have no effect on the lamp when a DC current was sent through one of the other windings?

The D.C. current sets up a stationary magnetic field, which saturates the iron core and eliminates the induction effect of the primary. In this case the only impedance to the source is the low D.C. resistance of the primary, producing a heavy current flow. Changing the load on the secondary has no effect on the lamp since there is no mutual induction between the two windings.

ELECTRONICS TECHNICIAN

JOB SHEET

Impedance

Objective: How to measure and calculate the effects of reactive circuits when resistance has been included.

Materials: Obtain test board for circuits illustrated.

Equipment: AC voltmeter.

Procedure: Apply 60 cycle line voltage to each circuit. Measure the voltage across each component and the line voltage. Measure the value of the resistor. Record all measurements for future use.

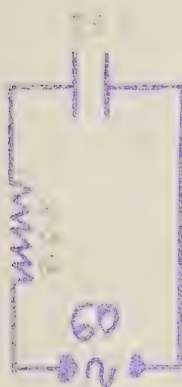


Fig. 1



Fig. 2

SHOW ALL WORK

Summary Questions:

1. From the voltage readings obtained show with vectors and calculations the resultant line or applied voltage.

$$E_T = 1.333$$

Fig. 1

$$E_R = 65 + 70 \text{ V}$$

$$E_L = 0 + 780 \text{ V}$$

2. What is the current value for each circuit?

3. What is the Z of each circuit?

$$Z = \frac{V}{I} = \frac{100}{10} = 10 \Omega$$

$$Z = \frac{V}{I} = \frac{100}{10} = 10 \Omega$$

$$Z = \frac{V}{I} = \frac{100}{10} = 10 \Omega$$

$$Z = \frac{V}{I} = \frac{100}{10} = 10 \Omega$$

4. What is the value of L and C ?

$$X_C = \frac{1}{\omega C} = C = \frac{1}{\omega X_C} = \frac{1}{376.9 \times 9.77} = .27 \text{ MFD.} = C$$

$$X_L = \omega L = L = \frac{X_L}{\omega} = \frac{10}{376.9} = 26.6 \text{ HENRYS} = L$$

5. What is the value of the capacitive reactance?


$$X_C = 9.77 \Omega$$

ELECTRONICS TECHNICIAN
JOB SHEET

Series Resonance

Objective: To demonstrate the effects of inductance and capacitance in resonant circuit.

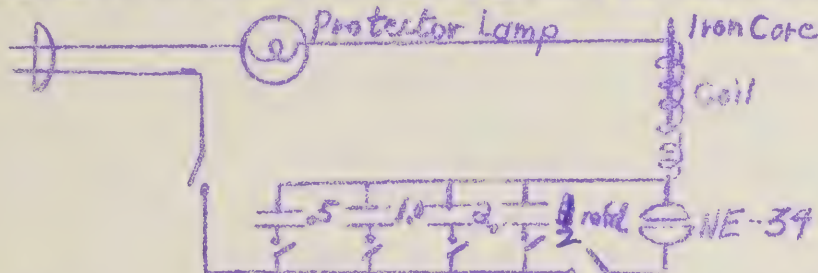Materials: Prepared series resonant circuit as illustrated:



Procedure:

Caution: Open line switch each time when adding capacitance on capacitor bank. Coil should be kept 1.25 inches above base.

1. a. Connect a 2 mfd capacitor and close line switch.
b. Repeat with NE 34 lamp connected across capacitor bank. Note intensity of lamp.
c. With NE 34 connected remove core from coil observing the effect on the lamp.
2. Repeat 1 with 3mfd capacitance connected.
3. Repeat 1 with 5mfd capacitance connected.

Report:

- (Prepare separate technical report)
1. Explain action of the oscillating iron core.
 2. Explain action of the core coming to rest.
 3. Give your reason for the change of light intensity for each case.
 4. What effect did removing the core from the coil have on its inductance? From the reaction on the light, what effect did it have on the circuit?

Date: April 11 1957

ELECTRONICS TECHNICIAN

TECHNICAL REPORT

Title: Series resonance

This report contains the information gathered with the demonstrator board on series resonant circuits.

The circuit was found to be nearest resonance with a 2 mfd. capacitor and the core out of the coil. The voltage across both reactances was almost equal. The current in the circuit is at maximum.

When the core was inserted in the coil the intensity of the lamp NE-34 across the capacitor, decreased slightly, indicating a decrease of the current in the circuit. With the core inserted in the coil, the inductance and reactance were increased, therefore detuning the circuit and decreasing the current.

With the circuit set at resonance and the core outside the coil resting on the board, the line switch was closed. At that instant, a strong magnetic field was set up by the coil, since maximum current is flowing. This magnetic field attracted the core into the coil with great force. As the core entered the coil, its inductance increased, the circuit is detuned and the current decreased. Now, when the core was attracted to the coil its momentum carried it to the other side, so that as it was moving out the inductance of the coil was decreasing bringing the circuit back towards resonance and again increasing the current which in turn increased the attraction by the coil to the core. This increased attraction plus the core's own weight, sent it back down through the coil bringing the circuit back to the original position. This process of oscillations continued on a dampening motion until the core came to a complete stop inside the coil. Since the core never comes out of the coil completely, the circuit never reaches the resonance point. On each oscillation the current decreases more and more until the core loses all its momentum and the changing magnetic field, changing at the line frequency, is able to hold it steady in the coil.

The lamp NE-34 across the capacitor varied in intensity as the core moved in and out of the coil, being brighter at the top and bottom of each oscillation, indicating the changing current in the circuit as it approached resonance.

Removing the core from the inductance decreases its inductance since the iron offers less reluctance to the flux lines than air. The lamp indicated an increase in current by being brighter, proving that the circuit was at resonance with the core out.

Increasing the capacitance, also detunes the circuit since the X_C is decreased. Closing the line switch with the capacitance increased, the core is attracted to the coil like in the first case, but now the current is much less, and the magnetizing force is not enough to hold the core in the coil due to the gravitational force in the core, so it keeps oscillating

Los Angeles Trade Tech. Jr. College
Instructor: R.H. Oeffinger

JS--


Agustin Lucas
April 15 1957

ELECTRONICS TECHNICIAN

Job Sheet Parallel Resonance

Objective: To understand the characteristics of parallel resonance circuits.

Materials: Prepared demonstration unit.

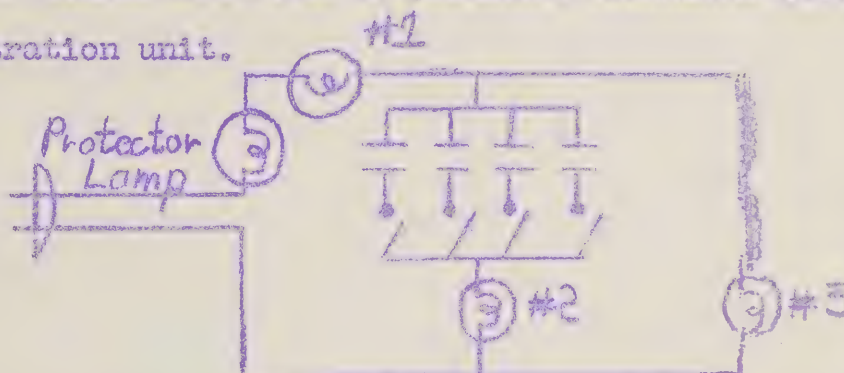

Procedure: CAUTION: Switch 1 should always be opened before adding capacitance. Make certain that iron cores are in the coils before applying voltage.

1. With the capacitance branch out of the circuit, close sw-1, observe the current indicating lamps.
2. Repeat #1 with 4.5 mfd, observe the intensity of lamps 1, 2, and 3.
3. Repeat #1 with 5.5 mfd, observe the intensity of lamps 1, 2, and 3.

Report: 1. Write a technical report explaining the results observed in steps 1, 2, and 3.

2. What would happen if the line voltage was applied without the iron cores in the coils?---Why?

3. At resonance, why does lamp #1 remain lighted a small amount?

TECHNICAL REPORT

Title: Parallel resonance

This report contains information gathered with the demonstrator board on parallel resonant circuits.

Having the capacitor branch out of the circuit both lamps, #1 & #3, light with the same intensity. Since the circuit is a series inductive-resistive circuit the current through all components is the same.

When 4.5 mfd, were connected in parallel with the inductance, lamp #1 becomes dimmer, indicating less line current. Lamp #2 in capacitor branch is dimmer than lamp #3 in inductor branch. This indicates that the circuit is inductive since the X_c is greater than the X_l and the inductive branch current is greater than the capacitive branch current.

When the capacitance was increased to 5.5 mfd. the circuit approached resonance condition. Lamp #1 intensity dropped again, indicating a decrease on line current. No appreciable change was noted on lamp #3 in the inductive branch, while lamp #2 in the capacitive branch increased in intensity to equal lamp #3, indicating that the tank current was equal in both branches.

If the cores of the coils were to be removed with the line voltage applied, the coils will probably burn up. Without the cores the reactance of the coils will decrease considerably, leaving as the only opposition to current the D.C. resistance of the wire plus a very small reactance.

With the circuit at the resonance condition, lamp #1 in the line remained lighted a small amount, because, the line current does not drop to zero since the tank circuit must be supply with energy from the line to keep going.

Voltages readings taken in all three steps.

#1 Lamp #1----- 3.4 volts
 " #3----- 3.45 volts
 Across the coils ----- 106 volts

#2 Lamp #1 -----1.8 volts
 " #2 -----2.5 "
 " #3 -----4 "
 Across the inductor----110 volts
 " " Capacitor---114 "

#3 Lamp #1-----1.6 volts
 " #2-----3.5 "
 " #3-----3.5 "
 Across the inductor----111 volts
 " " capacitor---112.5 volts


ELECTRONICS TECHNICIAN

JOB SHEET

Loading the Resonate Circuit

Objective: to note the effects of loading by removing power from a series resonate circuit.

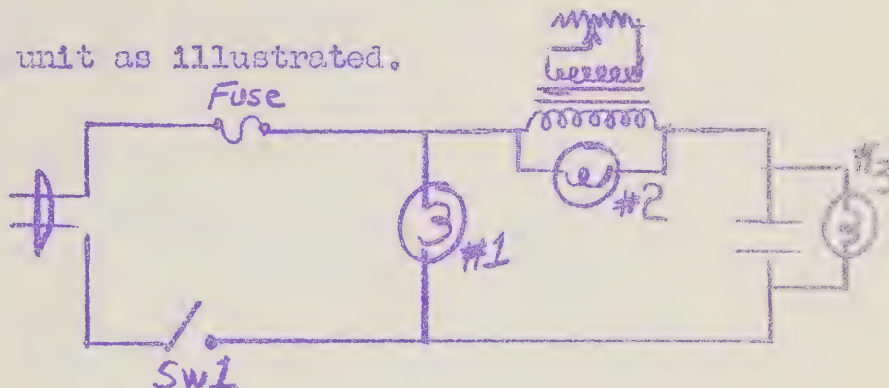Materials & Equipment: Prepared unit as illustrated.



Procedure: Answer questions and give results on a technical report form.

1. Disconnect one lead to the resistor for a no load condition. Close sw/#1 and observe the rise of voltage as the circuit nears resonance.
2. Open sw/#1 and connect the 25 ohm resistor to the secondary. Explain why the intensity of the lamps are different.
3. Slide arm of resistor to maximum position. Lift arm without moving to a new position. Note result and explain.
4. Increase the load upon the secondary to 5 ohms. Explain the difference of intensity between the lamps.
5. Short out the secondary. Observe the intensity of lamps #2 and #3. Give your explanation of the results

TECHNICAL REPORT

LOADING OF THE RESONANT CIRCUIT

This report contains information gathered with the demonstrator board.

With the load disconnected, lamp #3 across the capacitor was brighter than lamp #2 across the transformer with both being brighter than lamp #1 across the line. Since the circuit is a series circuit the lamps indicate that the X_C is greater than the X_L and that the voltage drops across the reactances were greater than the line voltage.

Actual voltage readings:

Line-----120 X_C -----200 X_L -----150

As the secondary of the transformer was loaded with 25 ohms, both lamps decreased in intensity, lamp #2 being slightly brighter. By connecting a resistive load in the secondary the total impedance of the primary is increased. The secondary current sets up a magnetic field which opposes the field set up by the primary and the net effect is a reflected resistance back to the primary which is equal to the load resistance times the square of the turns ratio of the transformer. This increase in impedance in the circuit decreases the current flowing, therefore there is a decrease on the voltage drop across the reactance.

Actual voltage readings:

X_C -----147 X_L -----183

With maximum resistance of 25 ohms in the load, lamp #2 has slightly more intensity than lamp #3 showing a larger IR drop across the transformer due to the reflected impedance.

When the load is disconnected the circuit returns to the original position both lamps being considerably brighter. (* Note)

By increasing the load in the secondary, the reflected impedance is decreased, the total impedance of the circuit is decreased and the current increased. Therefore since the impedance of the transformer decreased lamp #2 dims, showing a decrease in the IR drop. Lamp #3 increased in intensity, showing an increase in the current in the circuit and a greater IR drop across the capacitor.

Actual voltage readings:

X_C -----112 X_L -----78

With the secondary shorted out, lamp #2 is out. This indicates that the IR drop across the transformer is very low. The strong magnetic field set up by the secondary current cancels much of the magnetic field set up by the primary, decreasing the reactance considerably, increasing the current in the circuit. Therefore lamp #3 shows more intensity.

Actual voltage readings:

X_C -----123 X_L -----7

*-SATURATION OF THE CORE.

ELECTRONICS TECHNICIAN



JOB SHEET

Power Amplifiers-Audio

Objective: How to construct and test audio power amplifiers.

Materials: Components and parts to build the following circuits:

Single-Ended

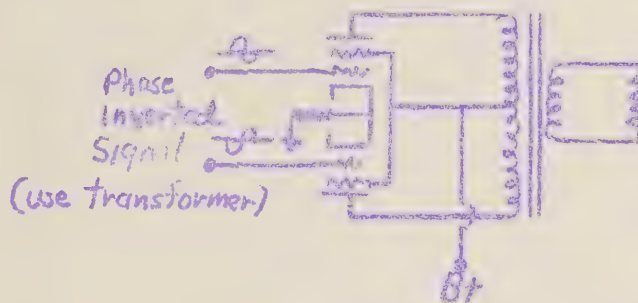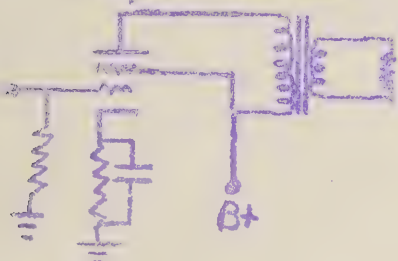

Push-Pull

Equipment: Audio generator, oscilloscope, AC voltmeter, and load resistors.

Procedure: Use tube manual to determine value of components.


Construct first the single-ended amplifier.

Determine the following for the amplifier:

1. Max. undistorted output and required input signal.
Power sensitivity
2. Plate dissipation
3. Plate efficiency
4. Db. Gain

Construct the push pull amplifier

Repeat 1, 2, 3, & 4.

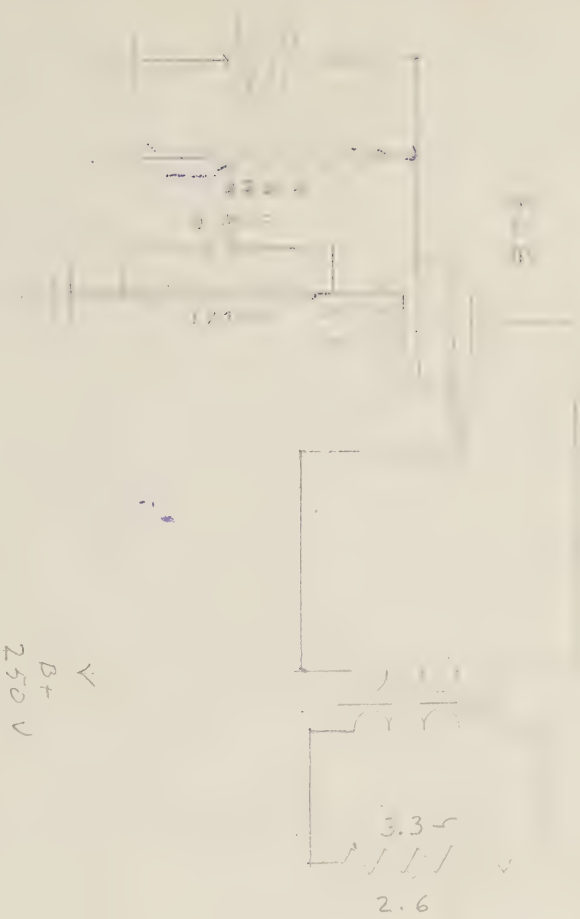

1. MAXIMUM UNDISTORTED OUTPUT = 2.6 V RMS
 RMS OUTPUT = 2.6 V RMS

2. POWER SENSITIVITY = $\frac{P_{OUT}}{I_q^2} \times 10^5 \text{ MILLIWATTS}$

$$P_{OUT} = \frac{E^2}{R} = \frac{2.6^2}{3.3} = 2.3 \text{ WATTS}$$

$$\frac{E_q^2}{I_q^2} = \frac{49}{1}$$

3. PLATE DISSIPATION = $P_{IN}(E_{PI}) - P_{OUT} =$

$$= 250 \times 0.71 - 2.3 = 15.4 \text{ WATTS}$$

4. PLATE EFFICIENCY = $\frac{P_{OUT}}{P_{IN}(E_{PI})} \times 100 =$

$$= \frac{2.3}{17.7} \times 100 = 13\%$$

5. DB. GAIN = $NDB = 10 \log \left(\frac{P_{OUT}}{P_{IN} \left(\frac{E_q^2}{R_q} \right)} \right)$

$$= 10 \log \frac{2.3}{2.23 \times 10^{-2}} = 4. \times 10 = 40 \text{ DB}$$

Los Angeles Trade-Tech. Jr. College	Title:	Date:
Los Angeles, Calif.	Drawn by:	
Electronics	Approved by:	

Los Angeles Trade Tech. Jr. College
Instructor: R.H. Oeffinger

JS-

ELECTRONICS TECHNICIAN

JOB SHEET

Reactance Measurements

Objective: How to determine values of unknown components.






Materials: $7\frac{1}{2}$ watt lamp and various sizes of resistors, capacitors and inductances as needed.

Equipment: AC voltmeter and the 6 boxes with concealed components.

Procedure: Determine what component is in each box, giving its value in ohms, inductance or reactance.

Use the 60 cycle source as the AC EMP. CAUTION--have lamp in series with line source.

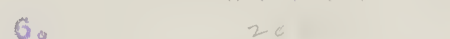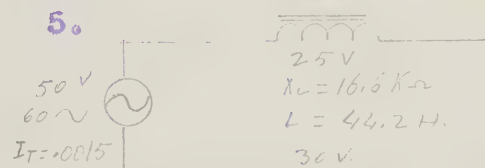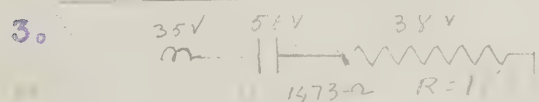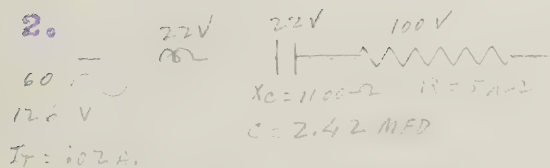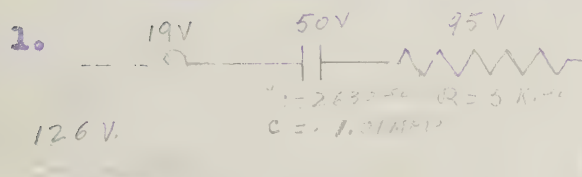Draw schematic of method and components used for solving each one.



Method used: First it was determined which box contained a capacitor by checking with the ohm-meter. Then each individual box was connected to a signal generator with an output of 50 volts, observing the voltage drops across each element as the fr. was varied. Once it was determined what was in the box, the values of each component were found by using ohms law and the formulas for reactances, after they were connected to the 60 cycle A.C. line in the manner shown.

Agustin Lucas
March 26 1957

Los Angeles Trade Tech. Jr. College
Instructor: R.H. Goffinger

JS-

ELECTRONICS TECHNICIAN


JOB SHEET

Resonance

Objective: How to construct a circuit with inductive and capacitive reactive components equal and to study the effects of resonance.

Materials: .5 mfd and .01 mfd capacitors.

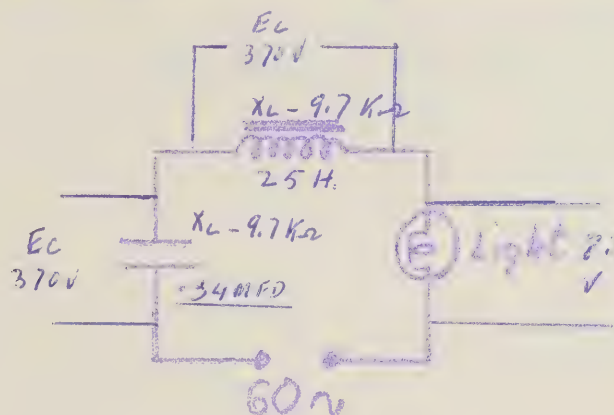Equipment: Series resonance board (as illustrated) and AC voltmeter.



Procedure: Connect circuit to 60 cycle source and record the following:
Short out one at a time the capacitance and inductance and make a note on the intensity of the light; measure voltage across the inductance and capacitance; place in parallel one at a time first the .5 mfd and then the .01 mfd capacitor with the existing capacitance, recording both the voltages existing across the reactances and the intensity of the light.

Summary Questions:

1. What happened to the light when shorting out either the capacitor or inductance?

When one of the reactive components was shorted out, the light dimmed considerably. This effect was caused by the increase of reactance as the circuit went off resonance, decreasing the current flow.

2. At Resonance what should the voltage drops be across the reactances? Explain.

Resonance (cont.)

Summary Questions (cont.)

2. (cont.) The voltage drops across the reactances should be equal since the value of both reactances is the same and the current being equal in all the parts of the circuit.

$$X_L = X_C$$

3. When resonance occurs what limits the flow of current? What is "Q"?

At resonance both reactances are equal and opposite, so they effectibly cancel out, leaving the resistance of the circuit as the only opposition to current.

Q is the merit of the circuit. (How selective). Also it is an indication of how much resistance is in the circuit.

$$Q = \frac{X_L \text{ or } X_C}{R}$$

4. In each case what happened to the light and the voltage across the reactances when the capacitors were paralleled? Give your own explanation.

When the .5 Mfd. capacitor was placed in paralell with the capacitor in the circuit the lighth went out. The voltage across the capacitor dropped by 300 volts, while the voltage across the inductance dropped by 200 volts. As the capacitance was increased, the X_C was decreased, making the X_L more predominant. The circuit is no more at resonance. The current was decreased as the total impedance was increased. Paralelling the .01 Mfd. had hardly no effect since the original capacitance of .34 Mfd is quite large compared with .01 Mfd.

5. What is the formula for the resonant frequency? What does a series circuit represent above and below resonance? Explain. $F_o = \frac{1}{2\pi\sqrt{LC}}$

A series circuit, above resonance acts inductive or represents an inductor. An increas in frequency will make the X_L more predominant.

Below resonance the circuit acts capacitive, since a capacitor presents more reactance to the lower frequency.

Los Angeles Trade Tech. Jr. College
Instructor: R.H. Jeffinger

JS-

ELECTRONICS TECHNICIAN

JOB SHEET

Transformer Characteristics

Objective: How to measure the characteristics of transformers.

Material: Power transformer with all windings removed except primary, 5 ohm 20 watt or more resistor, 5 ohm 10 watt resistor, #30 and #20 enamel covered wire, and insulating tape.


Equipment: Voltmeter and ~~low range AC~~ ammeter.

Procedure: I. On top of primary wind ~~20~~⁸⁰ turns of #30 wire.
Measure voltage across primary and secondary.
How many turns are in the primary? 760

II. Connect equipment as shown:

$$E_p = 114 \text{ v.}$$

$$E_s = 12 \text{ v.}$$

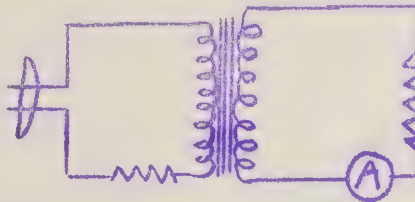

$$\frac{N_p}{N_s} = \frac{E_p}{E_s} \therefore \frac{N_p}{80} = \frac{114}{12} \quad N_p = 760 \text{ turns}$$

Measure voltage across load resistor and series resistor in the primary. Record reading of ammeter in the secondary.

From data recorded to this point, solve the following:

a. Turns ratio. $\frac{760}{80} = \frac{9.5}{1}$ Step down.

b. Wattage in primary and secondary.

c. % of efficiency.

III. Wind ~~20~~⁸⁰ turns on top of last winding with ~~#20~~^{#21} wire.
Measure resistance of both secondary windings. #1 = 6 Ω #2 = .8 Ω

Repeat all instructions and steps as in II.

Secondary with #30 wire:

Ep----- 100 volts.

Es-----4.7 volts.

Voltage across 5 ohms resistor in primary----1.8 volts.

Ip----- $\frac{1.8}{5} = .36$ amps.

Is----- $\frac{4.7}{5} = .94$ amps

Primary watts----- $100 \times .36 = 36$ w.

Secondary watts----- $4.7 \times .94 = 4.42$ w.

Efficiency----- $\frac{4.42}{36} = 12.3 \%$

Secondary with #21 wire:

Ep----- 96 volts.

Es-----8.6 volts.

Voltage across 5 ohms resistor in primary---1.6 volts.

Ip----- $\frac{1.6}{5} = .32$ amps.

Is----- $\frac{8.6}{5} = 1.72$ amps.

Primary watts----- $96 \times .32 = 30.72$ W.

Secondary watts----- $8.6 \times 1.72 = 14.8$ W.

Efficiency----- $\frac{14.8}{30.72} = 48.2 \%$

Job Sheet--Transformer Characteristics (cont.)

Summary Questions:

1. Give your reason for the difference of potential found across the load resistor in the two secondary windings: Since the size of the conductor is one of the factors that determine the amount of EMF induced in a coil, the amount of induced EMF in the #21 wire coil was therefore greater.

2. Why is it impossible to reach 100% efficiency?

To reach 100% efficiency, the phase angle between the voltage and the current must be zero. A point impossible to reach since all the inductive effect can not be eliminated. Also there is a certain amount of flux leakage and core losses.

3. From the wire table calculate how many feet in each secondary winding, and the circular mills of each size of wire

#30 wire-----100 circular mils.

#30 wire-----105 ohms per 1000 feet.

$$\frac{105}{1000} = .105 \text{ ohms per foot.}$$

#30 coil = 6 ohms D.C. resistance.

$$\frac{6}{.105} = 57.14 \text{ Feet in coil}$$

#21 wire-----810 circular mils.

#21 wire-----13.1 ohms per 1000 feet.

$$\frac{13.1}{1000} = .0131 \text{ ohms per foot.}$$

#21 coil = .8 ohms D.C. resistance.

$$\frac{.8}{.0131} = 61 \text{ Feet in coil.}$$

Los Angeles Trade Tech. Jr. College
Instructor: R.H. Oeffinger

JS--

ELECTRONICS TECHNICIAN


JOB SHEET

Transformer Impedances

Objective: How to measure the impedance of a transformer winding.

Equipment: Audio output or interstage transformer, oscilloscope, and audio generator.

Procedure: Connect equipment as shown:

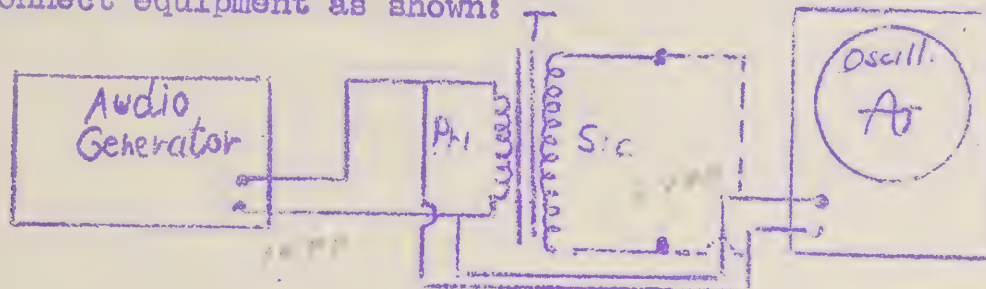

Set audio generator frequency at appx. 1000 cycles. Increase output from generator until a readable waveform is present on the oscilloscope at the output terminals of the generator. With the oscilloscope measure the voltage on the secondary of the transformer.

Use the voltage readings of the primary and secondary to determine the impedance of the two windings.

SHOW ALL WORK OR STEPS HERE:

TRANSFORMER USED - STANCOR - A-3956 OUTPUT

INPUT VOLTAGE 30 V P.P.

OUTPUT " 3 " "

$$\text{RATIO} = \frac{E_P}{E_S} = \frac{N_P}{N_S} = \frac{30}{3} = 10$$

$$\text{SECONDARY IMPEDANCE} = 61 \Omega$$

$$\text{IMPEDANCE RATIO} = \frac{Z_P}{Z_S} = \left(\frac{N_P}{N_S} \right)^2 = \left(\frac{10}{1} \right)^2 = 10^2 = 100$$
$$Z_P = Z_S \left(\frac{N_P}{N_S} \right)^2$$

$$\frac{Z_P}{61} = 100$$

$$Z_P = 61 \times 100 = 6100 \Omega$$

ELECTRONICS TECHNICIAN


JOB SHEET

Germanium Diode Characteristics

Objective: To study the forward and reverse characteristics of germanium diodes with respect to voltage, current, and temperature.

Materials: Seven diodes mounted on board.

Equipment: As shown below:

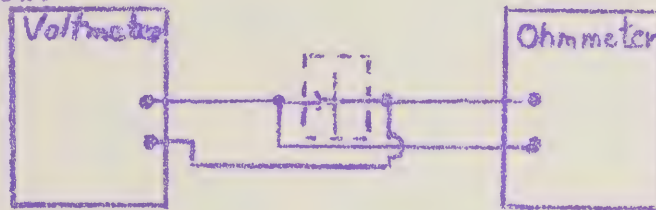

Procedure: Check each diode as follows:

Set one VTVM on the $1\frac{1}{2}$ volt scale and connect across the diode. Place the function switch on ohms for the other meter and also place across the diode.

Check voltage from ohmmeter for forward conduction. Start with Xi range reading both the resistance and voltage. From this calculate the current. Repeat with the balance of the resistance ranges.

Connect ohmmeter for the reverse polarity and repeat all steps as in the forward conduction.

Record all information as in the example below:

Type	FORWARD			REVERSE		
	Resistance	Voltage	Current	Resistance	Voltage	Current
1N34	500 ohms	1.44	2.88ma	Inf.	1.5	0
	600 ohms	1.28	2.13	Inf.	1.5	0
	1.18K	.82	.697	Inf.	1.5	0
	2.8K	.33	.118	1 Meg	1.48	1480mc
	8.0K	.11	.01375	1.1 Meg	1.37	1.245
	20K	.03	.0015	.54 Meg	.54	1.00
	∞	0	—	10K	.02	2.00

Summary Questions

1. Which diode was defective? Give your reasons according to reading taken.
2. For the reverse condition, why does the resistance increase with an increase in applied voltage?
3. In the forward condition, why does the resistance decrease with an increase in applied voltage?

GERMANIUM DIODE READINGS

FORWARD

REVERSE

Resistance	Voltage	Current	Resistance	Voltage	Current
<u>1N48</u>					
150 ohms	1.43 volts	9.54 ma.	Inf.	1.54	---
210 "	1.03 "	4.92 "	"	1.54	---
470 "	.47 "	1. "	"	1.54	----
1.5 K	.18 "	.12 "	500 K	1.5	3 ua.
6 K	.065 "	.108 "	310 K	1.16	3.74 ua.
10 K	.005 "	.5 ua.	20 K	.04	2. ua.
0	0	0	0	0	0
<u>1N51</u>					
220 ohms	1.48	6.74 ma.	Inf.	1.55	-----
290 "	1.13	3.9 "	"	1.55	-----
500 "	.52	1.04 "	20 K	1.46	73 ua.
1.5 K	.19	.169 "	16 K	.98	61.5 ua.
5 K	.06	.012 "	14 K	.18	18.5 ua.
8 K	.006	.75 ua	10 K	.04	4. ua.
0	0	0	0	0	0
<u>1N52</u>					
110 ohms	1.4	12.8 ma.	Inf.	1.54	-----
170 "	.94	5.52 "	"	1.54	-----
420 "	.43	1.025 "	"	1.54	-----
1.6 K	.19	.1088 "	200 K	1.47	7.35 ua.
6K	.07	.01168 "	160 K	.94	5.87 "
0	0	0	30 K	.04	4. "
0	0	0	0	0	0
<u>1N60</u>					
90 ohms	1.38	15.35 ma.	Inf.	1.54	-----
130 "	.86	6.62 "	"	1.54	-----
320 "	.36	1.125 "	"	1.54	-----
1.23 K	.16	.15 "	175 K	1.48	8.45 ua.
5.9 K	.07	.1189 "	150 K	.92	6.14 "
8 K	.015	.00175 "	40 K	.05	1.25 "
0	0	0	0	0	0
<u>1N65</u>					
110 ohms	1.41	12.8 ma.	Inf.	1.55	-----
151 "	.92	6.09 "	"	1.55	-----
360 "	.39	1.075 "	"	1.75	-----
1.32 K	.17	.129 "	500 K	1.52	3.2 ua.
6 K	.08	.0133 "	275 K	1.13	4.11 "
19 K	.02	1.05 ua.	90 K	.12	1.33 "
0	0	0	10 K	.005	.5 "
<u>CK707</u>					
98 ohms	1.4	14.3 ma.	Inf.	1.55	-----
140 "	.89	6.35 "	"	1.55	-----
340 "	.38	1.12 "	"	1.55	-----
1.2 K	.15	.125 "	500 K	1.54	3.4 ua.
4.8 K	.06	.0125 "	440 K	1.25	2.74 "
10 K	.01	1. ua.	44 K	.06	1.363 "
0	0	0	0	0	0

SUMMARY QUESTIONS ON DIODE JOB SHEET:

- #1. By comparing the readings of all diodes, there seems to be an indication that diode 1N51 may be defective. The current on the reverse direction is extremely high compared with the other diodes readings and the reverse resistance many times lower. These facts would indicate that this particular diode will not be to effective as a rectifier.
- #2 In the reverse condition, the diode is biased with a positive potential on the N material and a negative potential on the P material, exerting an attraction on the electrons and holes away from the junction towards the terminals. Increasing the potential between the terminals, will increase the attraction, which in effect is like increasing the resistance of the junction to current flow.
- #3 In the forward condition, the diode is biased with a negative potential on the N material and a positive potential on the P material, with the effect of a driving force pushing the electrons and holes towards the junction where they combine. Increasing the voltage at the terminals increases the driving force, which moves more electrons and holes. The net effect is like decreasing the resistance of the junction to the carriers, since the combination of holes and electrons constitutes the current flow.

Los Angeles Trade Tech. Jr. College
Instructor: R.H. Oeffinger

Agustin Lucas
May 8 1957
JS--

ELECTRONICS TECHNICIAN

JOB SHEET


Transistor Characteristics

Objective: To observe the effect of a change in emitter and base current on output or collector current.

Materials: Prepared transistor circuit and two different types of PNP junction transistors.

Equipment: Two 10 ma meters and a microamp meter.

Procedure: Connect equipment as shown:

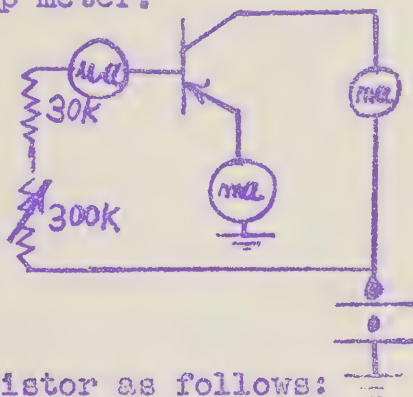

Plot two curves for each transistor as follows:

A. Y axis= Collector Current.
X axis= Emitter Current.

B. Y axis= Collector Current.
X axis= Base Current.

Summary Questions:

1. What is Beta?---What value from the curves plotted was the value of beta for each transistor?

2. What is Alpha?--Using the curves what was the value of alpha for each transistor?

1. Beta is the ratio of collector current to base current, used only on the grounded emitter transistor circuit.


Beta of 2N170 ----18.75
" " 2N229-----30

2. Alpha is the ratio of collector to emitter current.


Alpha of 2N170 ----.94
" " 2N229 ----.85

ALPHA

(2/1/75 2nd)

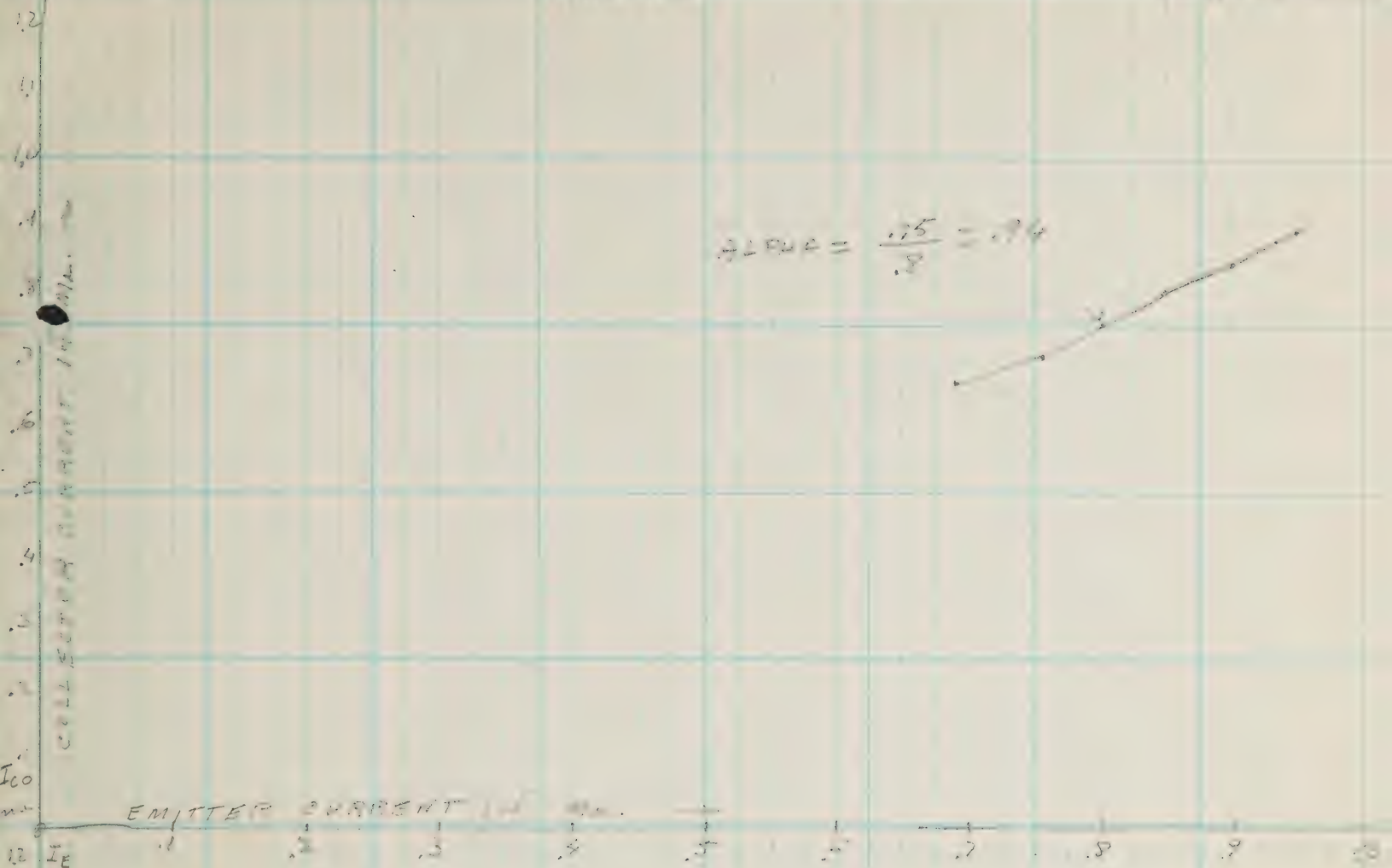



$$\text{ALPHA} = \frac{.75}{.8} = .94$$

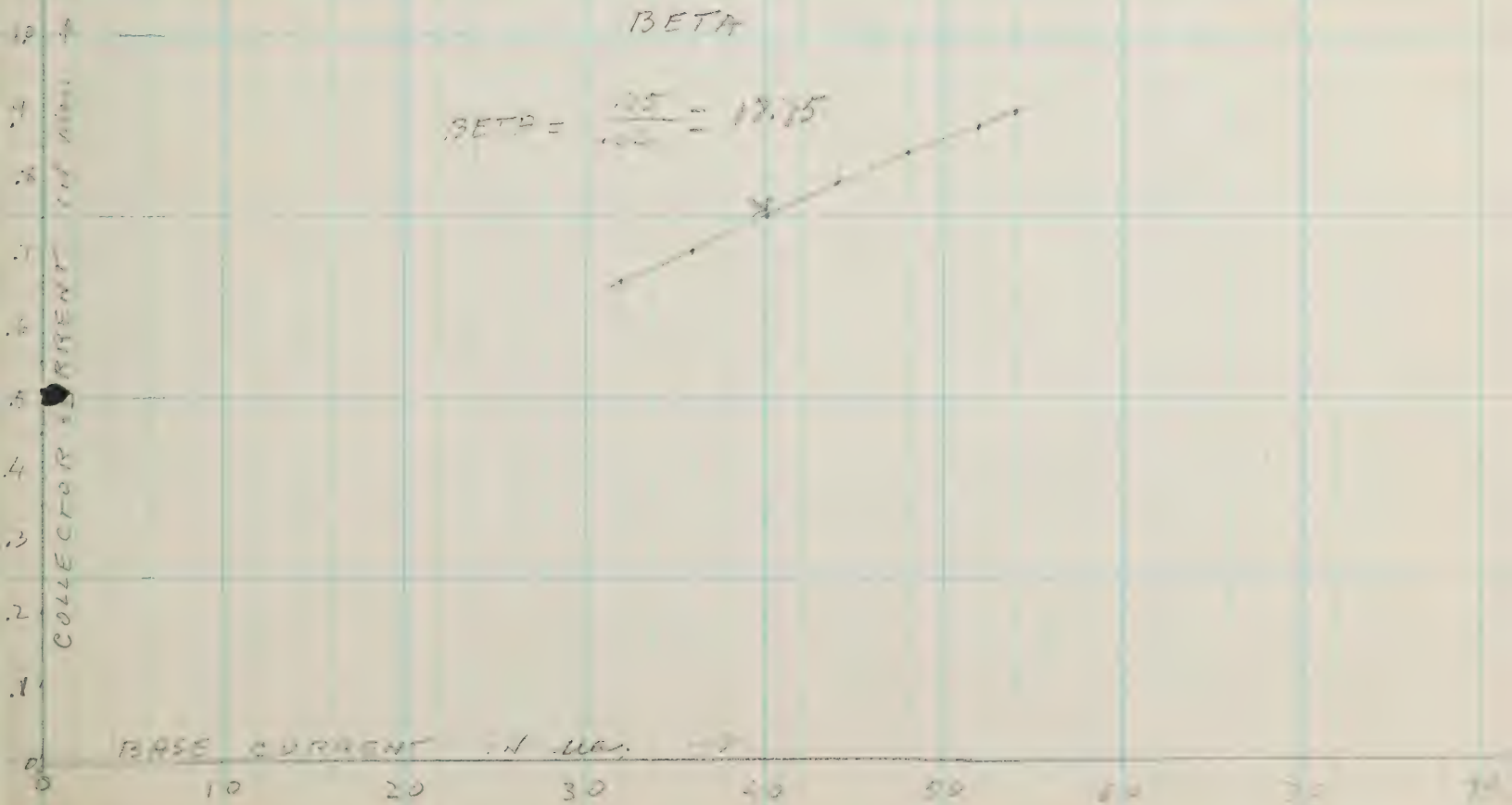


BETA
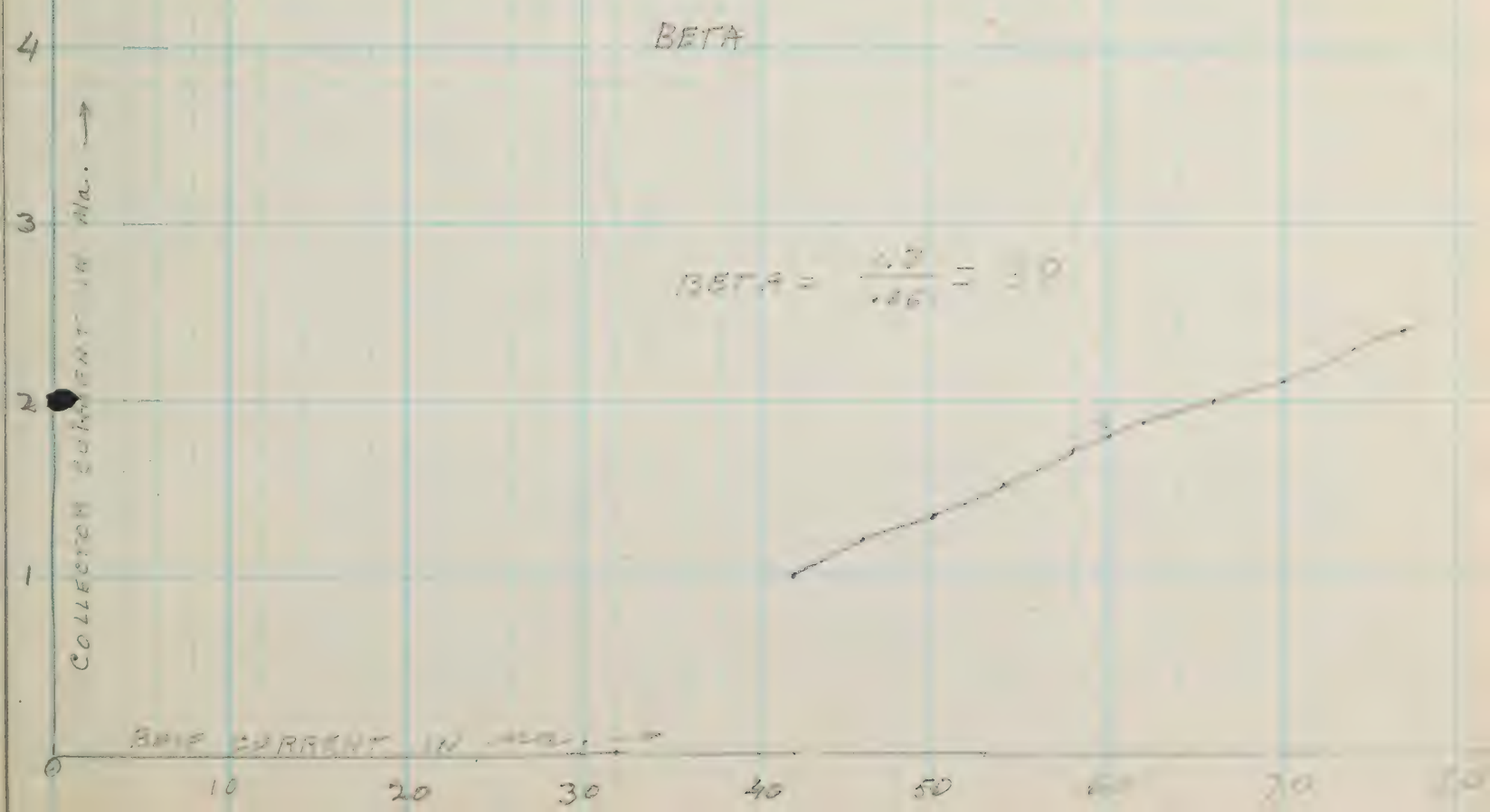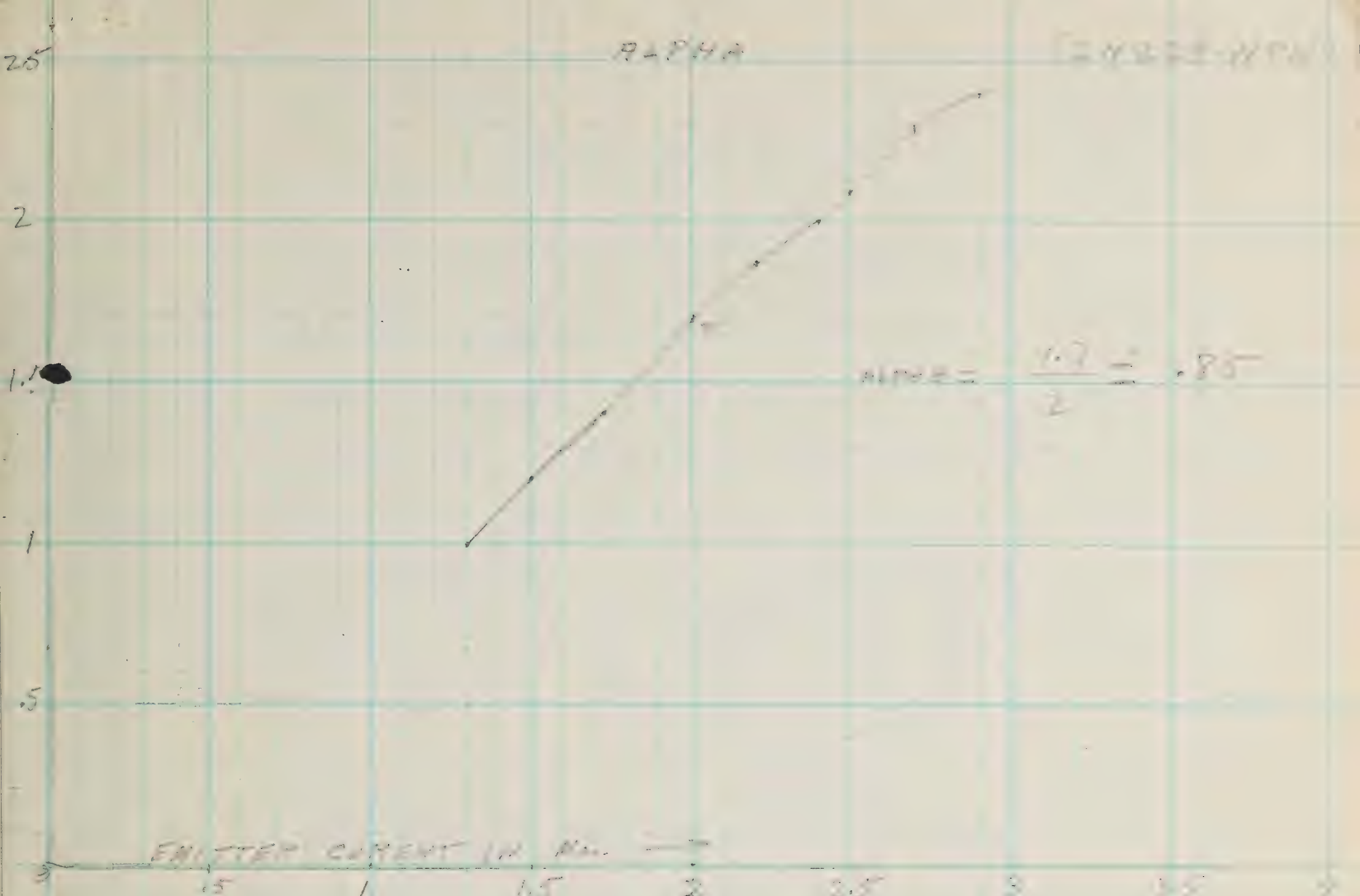
$$\text{BETA} = \frac{.75}{.04} = 17.75$$





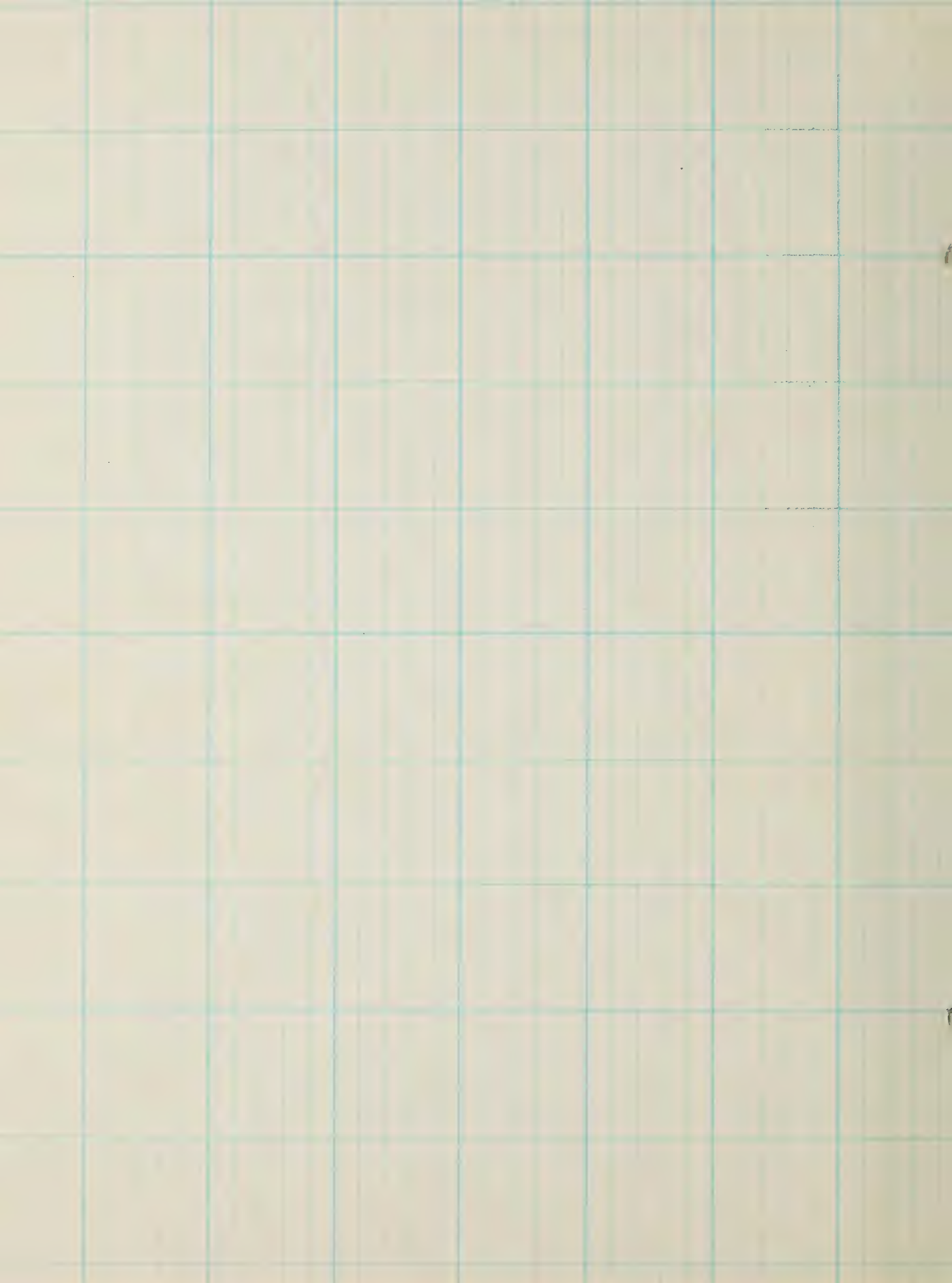

ELECTRONICS TECHNICIAN

JOB SHEET


Transistor Amplifier Characteristics

Objective: To determine the amplifying characteristics of a typical transistor amplifier.

Materials: Prepared transistor circuit board and components as illustrated.

Equipment: Oscilloscope, microammeter, ma. meter, and an audio signal generator.

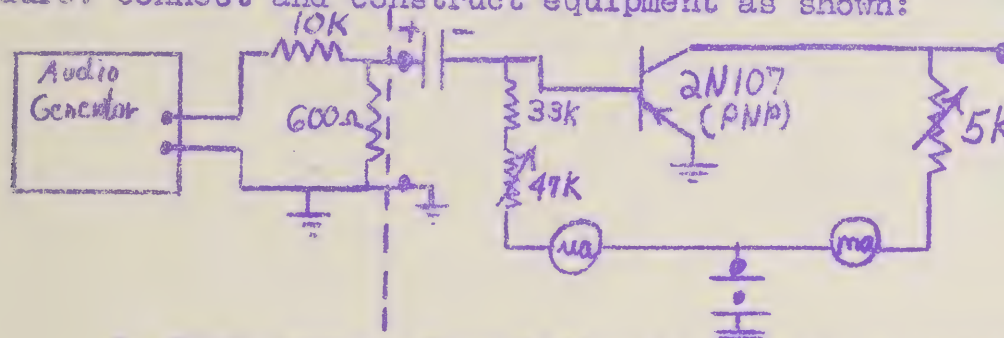Procedure: Connect and construct equipment as shown:



I. Plot curves of variation in I_c with a change in I_b for two collector loads--1K and 2K.

II. From reference data determine the input impedance of this transistor. With this information and the curves plotted determine the current and voltage gain for each load.

SHOW ALL WORK

Input impedance: 700 ohms. Voltage gain: $\frac{\Delta E_c}{\Delta E_b}$

Current gain: $\frac{\Delta I_c}{\Delta I_b}$

1 K. Load: Current gain: $\frac{.2 \text{ ma.}}{10 \text{ ua.}} = 20$

$$\Delta E_c = .0002 \times 1000 = .2 \text{ volts}$$

$$\Delta E_b = 10 \text{ ua.} \times 700 = .007 \text{ volts}$$

$$\text{Voltage gain: } \frac{.2}{.007} = 28.57$$

2 K. Load: Current gain: $\frac{.2 \text{ ma.}}{10 \text{ ua.}} = 20$

$$\Delta E_c = .0002 \times 2000 = .4 \text{ volts}$$



$$\Delta E_b = 10 \text{ ua.} \times 700 = .007 \text{ volts}$$

$$\text{Voltage gain: } \frac{.4}{.007} = 57.14$$

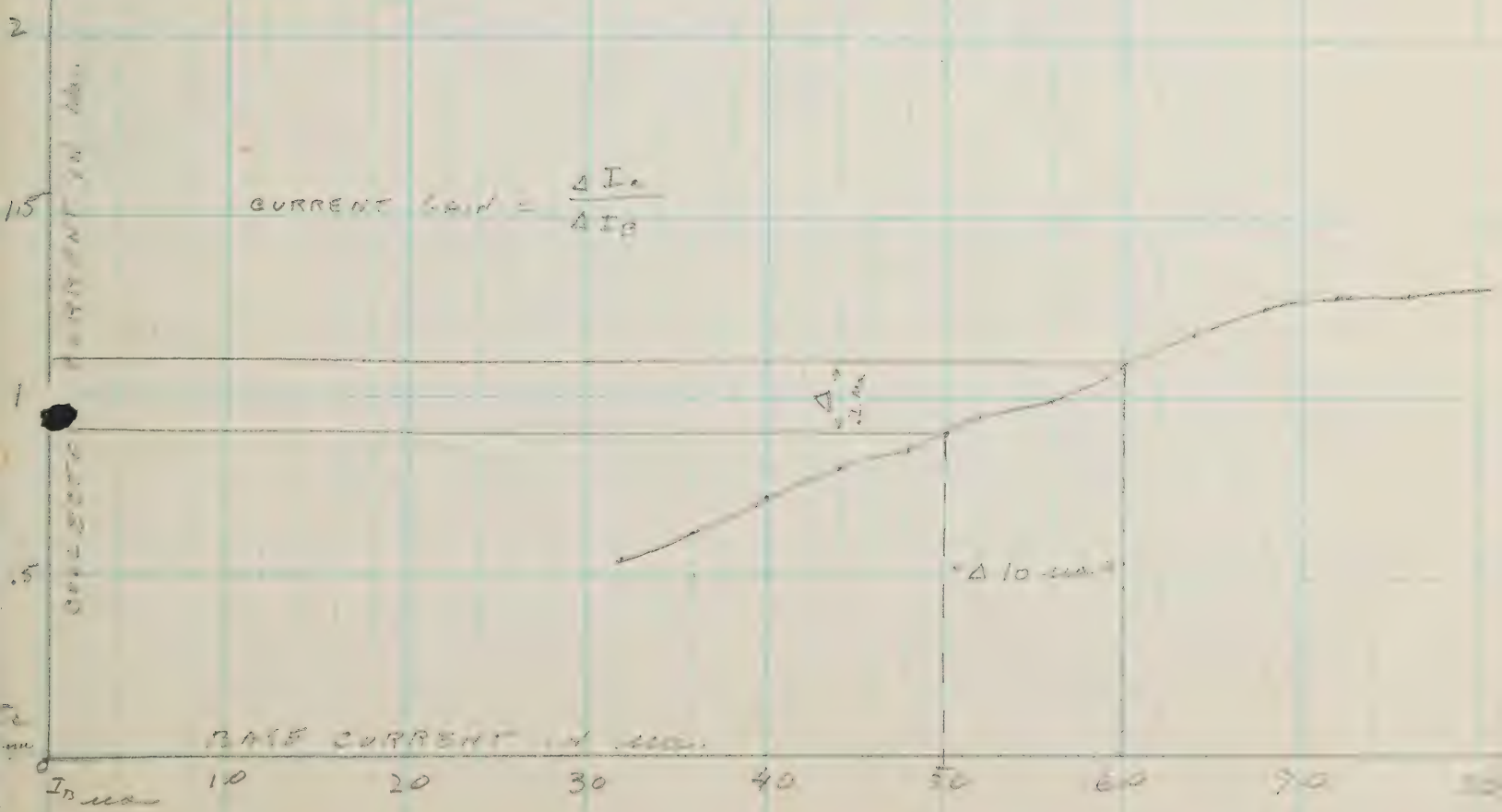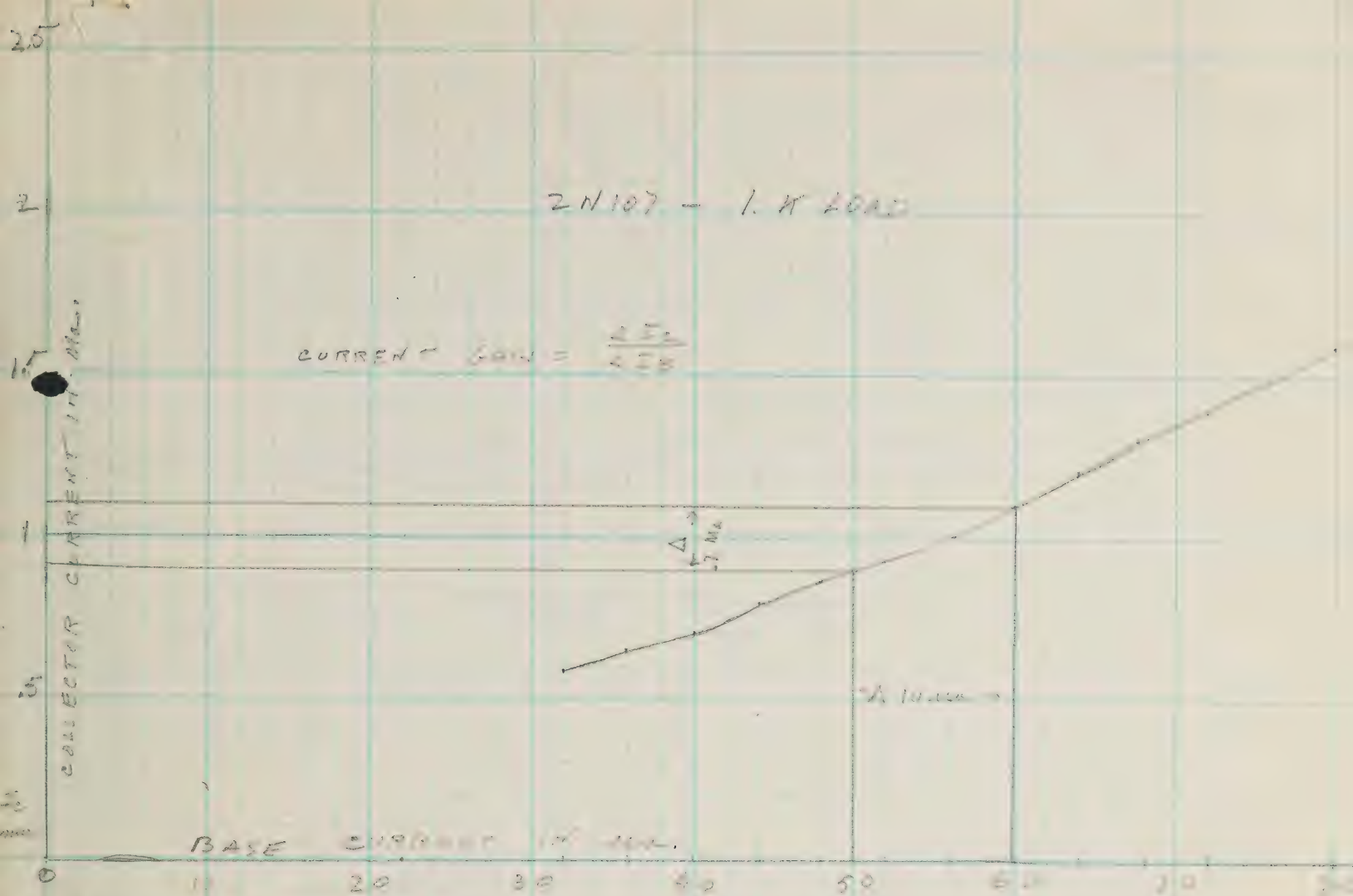III. Connect audio generator in series with the 10k ohm resistor and oscilloscope on output of amplifier. Adjust output of generator and bias for maximum undistorted output. Measure with oscilloscope input and output voltages. Compare this voltage gain with the calculated values in step # 2.

1 K. Load: Input----- .085 volts. Output--- 1.7 volts. Voltage gain 21.2

2 K. Load: Input----- .04 volts. Output--- 1.4 volts. Voltage gain 35



ELECTRONICS TECHNICIAN

JOB SHEET


Demodulation

Objective: To observe the characteristics of detectors and understand the principles of demodulation.

Materials: Crystal diode, 6C5 tube, and various resistors and capacitors as required to construct detectors.

Equipment: 455Kc RF amplifier, signal generator(RF with AM modulation), oscilloscope, and VTVM.

Procedure: Connect equipment as shown:

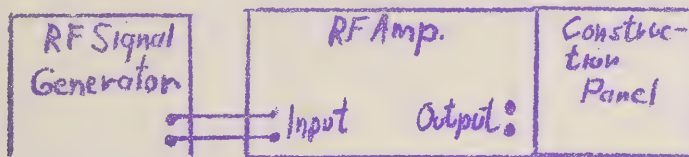

- I. Connect scope across output and set signal generator frequency for maximum output. Turn function switch on generator for AM modulation. Draw waveform of modulation envelope.
- II. On provided connection board of the RF amplifier, construct a crystal diode detector. Draw schematic of detector.
 - a. Place scope across diode load detector.
 - b. Draw waveforms for the following conditions:
 1. 100 mmfd RF by-pass.
 2. 500 mmfd " " "
 3. .01 mfd " " "
- III. Connect demodulator probe to input of scope. Observe results when placed across output of RF amplifier. What is the maximum peak to peak value of the AF component? What is the difference between a RF probe used for a VTVM and a probe for an oscilloscope? (VTVM assumed to be a DC voltmeter).
- IV. Connect 6C5 as a grid leak detector. Draw schematic and show values. Compare this detector with a diode for sensitivity and ability to handle signals without distortion. Note: to operate a 6C5 as a diode, tie plate and grid together.


Date: May 10 1957

ELECTRONIC TECHNICIAN

TECHNICAL REPORT


Title: Demodulation
Answers to Job Sheet

I.

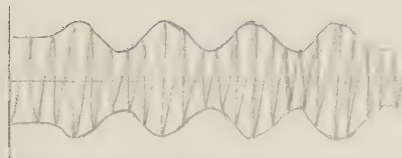

AM modulated RF carrier

II.

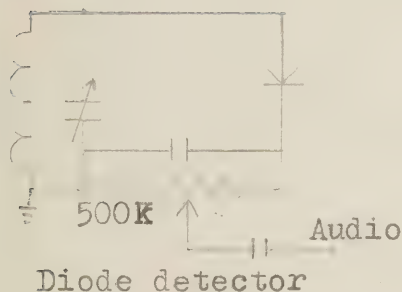

Audio wave with 100 mmfd. by-pass capacitor



Audio wave with 500 mmfd. by-pass capacitor



Audio wave with .01 mfd. by-pass capacitor

- III. a. The maximum peak to peak value of the AF component obtained with the detector probe is 1.7 volts.
- b. The difference between the scope and the DC VTVM RF probes is that the VTVM probe requires a filtering network so that the DC VTVM can read the voltage.

Los Trade Tech. Jr. College
Prof. R. H. Coffinger

Initiator: Agustin Lucas

Date: May 10 1957

ELECTRONIC TECHNICIAN


TECHNICAL REPORT

Demodulation (Cont.)

IV.



Grid Leak Detector.

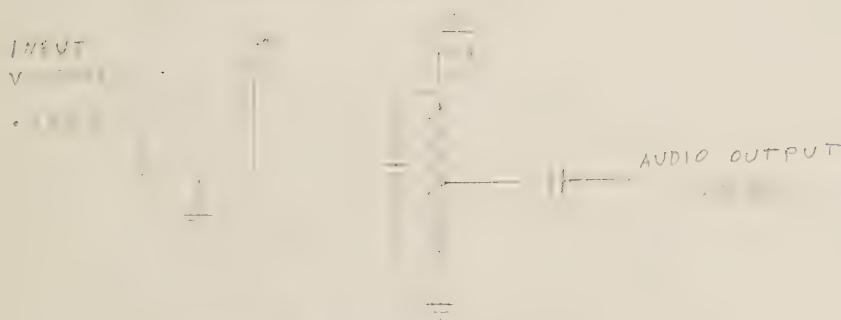

Diode Detector

The grid leak detector is more sensitive. It requires less input voltage and provides amplification.

Los Angeles Trade Tech. Jr. College
Instructor: R.H. Oeffinger

AGUSTIN LUCAS
MAY 9-57

ELECTRONICS TECHNICIAN

JOB SHEET


Harmonic Distortion

Objective: How to measure harmonic distortion.

Materials: Equivalent speaker load resistor.

Equipment: Audio amplifier, distortion meter, oscilloscope, audio generator, and AC voltmeter.

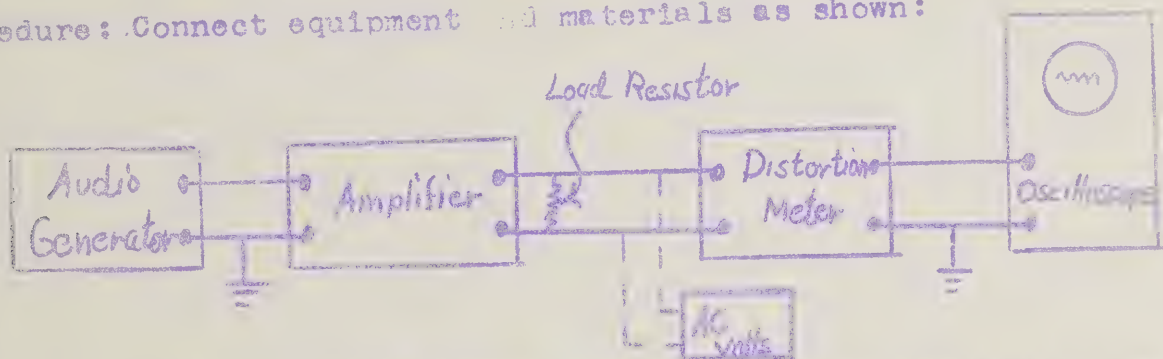Procedure: Connect equipment and materials as shown:



Determine the maximum input voltage to amplifier and test output of generator for this value at 1000 cycles.

Increase volume control until rated output of amplifier is reached. This can be determined from the voltage across the load resistor--power $\frac{V^2}{R}$ watts.

Remove voltmeter and proceed with distortion check after first reading and checking with instructor on the use and operation of the distortion meter.

Check and record % and type of distortion at and above and below rated output of amplifier.

At normal operation remove negative feedback and record results with respect to distortion, gain, and frequency response.


Date: May 8 1957

ELECTRONICS TECHNICIAN


TECHNICAL REPORT

Title: Harmonic Distortion

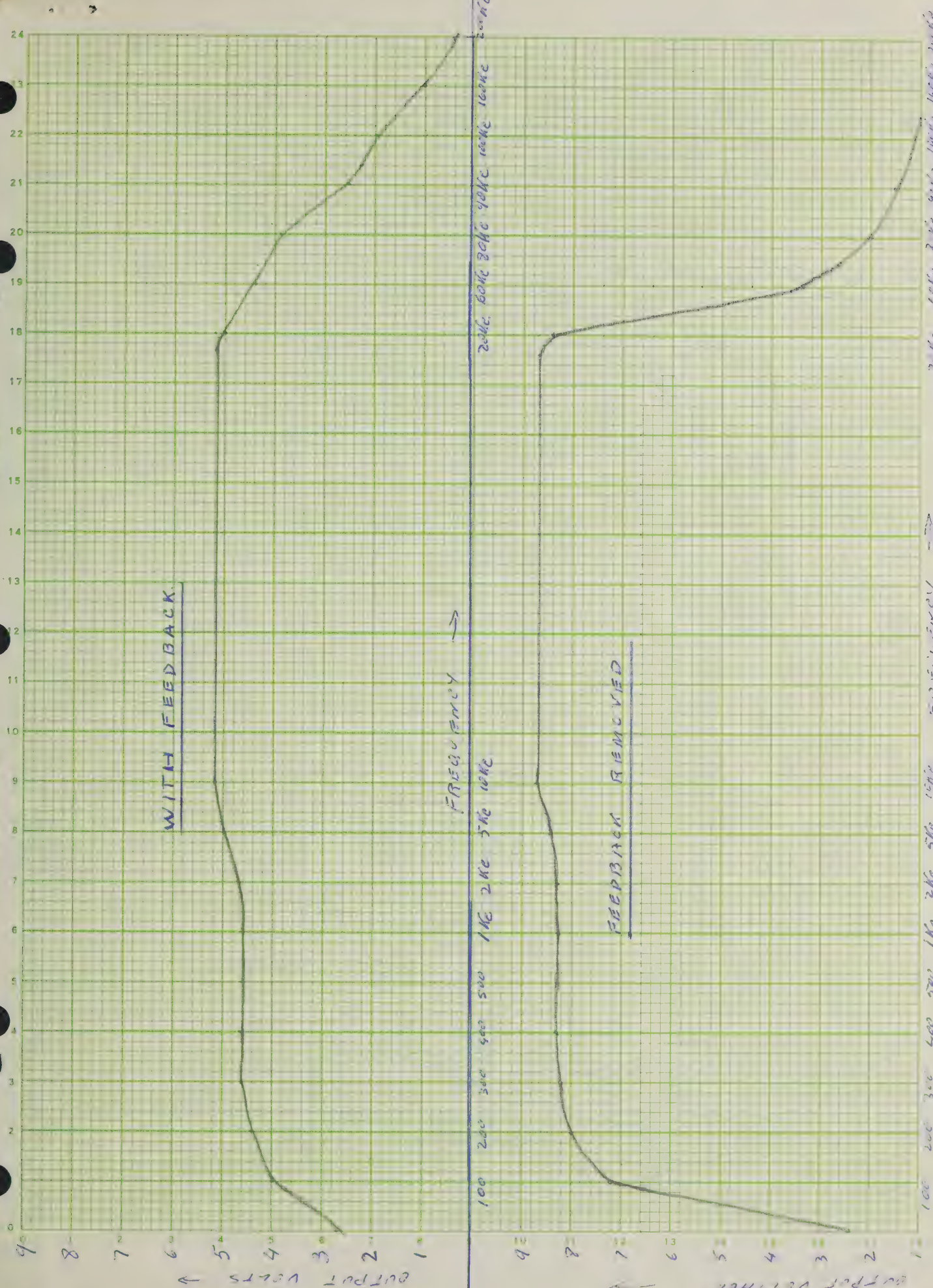1. Maximum input voltage to the amplifier: .8 volts
2. Rated output: 6 Watts. across a 10 ohm resistor.
output voltage: 7.75 volts. $= \frac{E^2}{R} = \frac{60}{10} = 6 \text{ Watts.}$
3. At rated output: 6 Watts, input---- .8 volts.
output---7.75 "
2nd. & 3rd. harmonic distortion ----- 9.3%
4. Below rated output: At 2 Watts, Input ----- .32 volts
Output -----4.47 "
2nd. & 3rd. harmonic distortion ----- 2.6%
5. Above rated output: At 7.1 Watts, Input ----- .9 volts
Output -----8.42 "
2nd. & 3rd. harmonic distortion ----- 12%
6. At normal operation: 2 Watts output with feedback.
Feedback removed: Input voltage ----- .32 volts
Output voltage-----8 volts
2nd. & 3rd. harmonic distortion -----12.5%
Output ----- 6.4 Watts
Gain: $10 \log \frac{6.4}{2} = 5.05 \text{ Db. gain without feedback.}$
7. Response curves shown on separate graph.



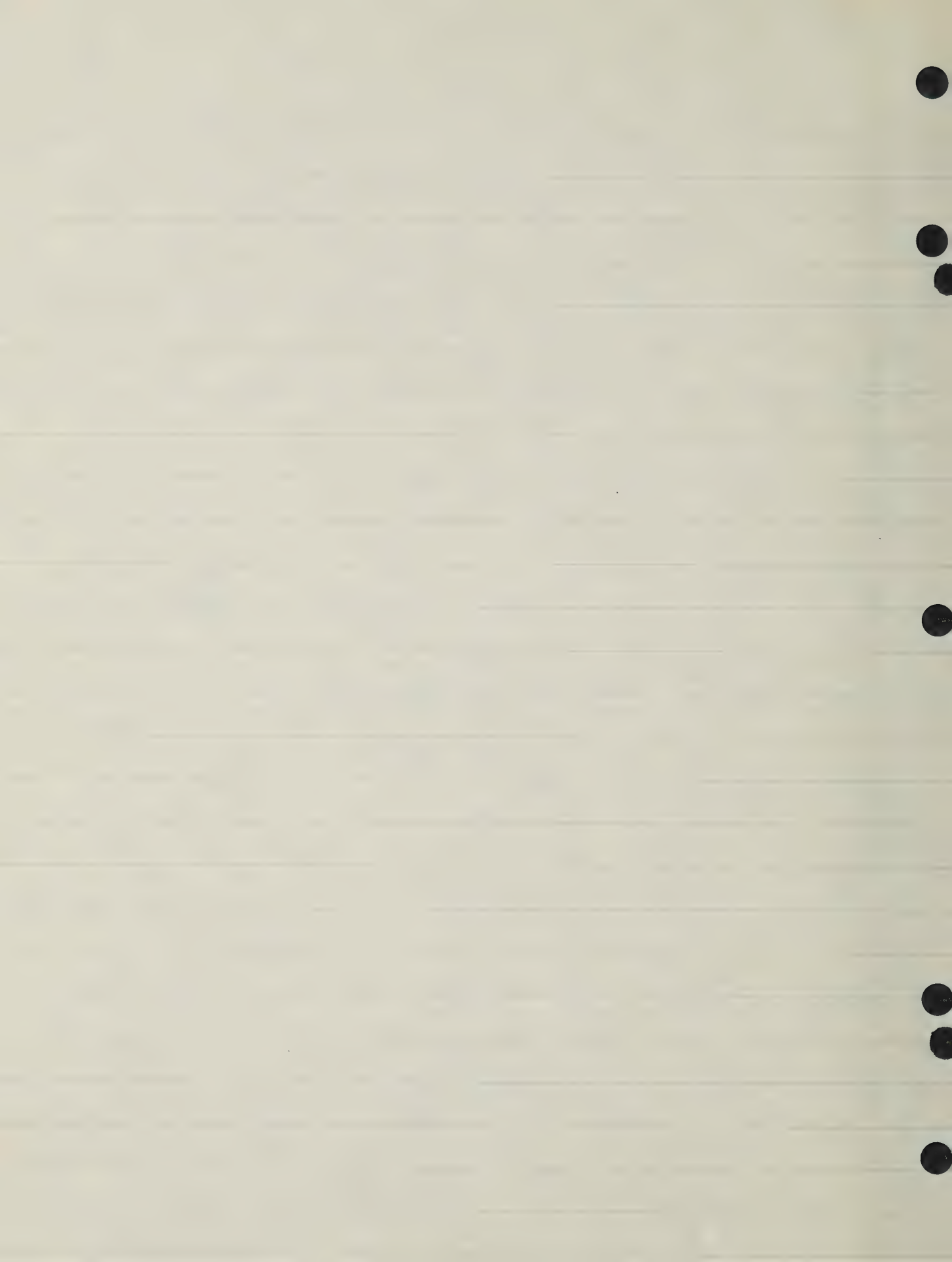1000 2000 3000 4000 5000 6000 7000 8000 9000 10000




Testing Transmission Lines and Antennas

Objective: How to test and measure the characteristics of transmission lines and antennas by the sweep generator method.

Materials: Prepared materials board and 50 feet of flat antenna lead-in.

Equipment: Sweep generator, marker generator, oscilloscope, and dipole antenna.

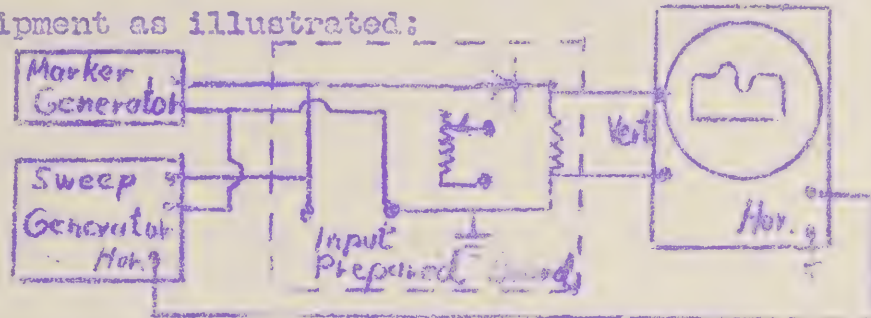Procedure: Connect equipment as illustrated:



- I. Connect one end of the twin lead to equipment and terminate the other end with the potentiometer. Set sweep generator for maximum sweep and output.

Adjust frequency control until a maximum and minimum voltage ratio can be observed on the oscilloscope. Adjust terminating potentiometer for minimum SWR. Measure the set value and record 310 OHMS.

1. Explain why this value is the characteristic impedance of the transmission line. MINIMUM SWR. MEANS, THAT NO ENERGY IS BEING RETURNED TO THE SOURCE. ALL OF IT IS CONSUMED BY THE LOAD. THEREFORE THE LINE IS MATCHED TO THE LOAD.
2. How can SWR be determined at the end of a line with the method used in this job sheet? BY MEASURING THE MAXIMUM AND MINIMUM PEAKS OF THE SW. AND USING THE FORMULA $SWR = \frac{E_{MAX}}{E_{MIN}}$.
- II. Connect antenna to equipment. Vary frequency of sweep generator. From SWRs observed determine the appx. frequency at which the antenna is out and the frequencies at which it is the most efficient. Use the marker generator to identify the frequencies. Record above results CENTER FR. 205 Mc. FR. RANGE 190 - 220 Mc.

3. Why does the antenna have more than one point of operation with respect to frequency? THE SECOND AND THIRD HARMONIC OF THE FR. FOR WHICH THE ANTENNA IS OUT CAN ALSO BE RECEIVED, BUT NOT AS EFFICIENTLY.

ELECTRONICS TECHNICIAN

JOB SHEET


Standing-Wave Characteristics

Objective: To understand the effect of standing-waves on transmission lines.

Materials: Line terminating resistance, variable stub, neon light, fluorescent light, and incandescent lamp.

Equipment: RF power source (200-300 mc) and Lecher line.

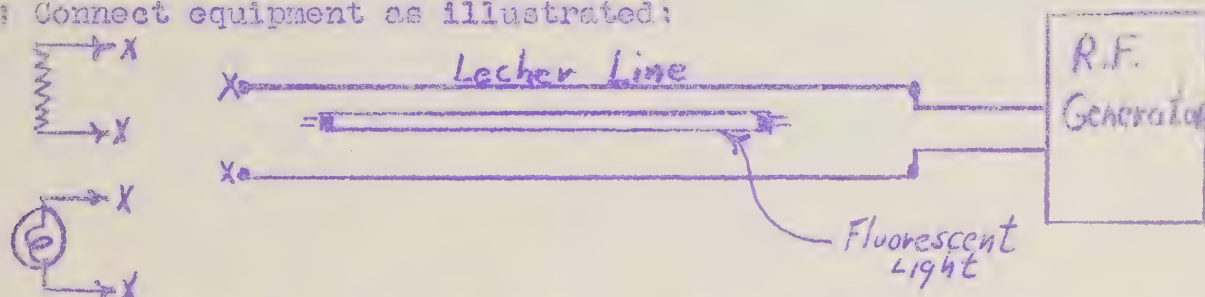Procedure: Connect equipment as illustrated:



- I. With power applied measure the distance between centers of the dark points on the fluorescent tube with the Lecher line open. Record from this the operating frequency and wavelength.

Move neon lamp along one wire and compare results with the fluorescent light.

1. What potential exists at end of transmission line?
2. What potential exists $\frac{1}{2}$ wavelength from end of line?

II. Short end of transmission line.

3. What happened to minimum points? Why?
4. Repeat questions 1 and 2.

- III. Calculate characteristic impedance of line from:
$$Z_0 = 276 \log_{10} \frac{b}{d}$$

b = distance between centers.
d = diameter of conductor.

Place this value at the end of the line and note condition of line.

5. Explain characteristic of voltage across transmission line terminated with its characteristic impedance.

- IV. Connect lamp across end of line. Move and adjust shorted stub near end of line for maximum light and minimum S.W.R.
6. Explain action of stub as an impedance matching device.

ELECTRONICS TECHNICIAN

TECHNICAL REPORT

Title: Standing-Wave Characteristics.

Answers to Job Sheet.

- I. Distance between dark points: 25 inches. The dark points represent the ends of a $\frac{1}{2}$ wavelength. One wavelength then is 50 inch.

$$\text{Fr.} = \frac{3 \times 10^8 \text{ meters}}{\text{Wavelength}}.$$

There are 39.4 inch. in one meter;

Therefore: $\frac{50}{39.4} = 1.27$ meters one wavelength;

Then; $\frac{3 \times 10^8}{1.27} = 2.36 \times 10^8 = 236 \text{ Mc.}$

The same results were observed with the fluorescent lamp and the neon lamp.

1. At the end of an open line exist a high potential.
2. $\frac{1}{4}$ wavelength back from the end of the line presents a low potential point.

- II. 3. When the line was shorted, the minimum voltage points moved forward $\frac{1}{4}$ wavelength. The characteristics of the line changed since at the end of a shorted line there is low impedance.

4. At the end of a shorted line exist low potential.
 $\frac{1}{4}$ wavelength back from the end presents a high potential point.

III. $Z_0 = 276 \log \frac{D}{a}$

D: Distance between wires in inches: 3"


a: Radius of wires in inches: .032"

$$Z_0 = 276 \log \frac{3}{.032} = 545 \text{ ohms.}$$

5. When a line is terminated with it's characteristic impedance, The voltage and current are in phase and their values are the same on any place in the line.

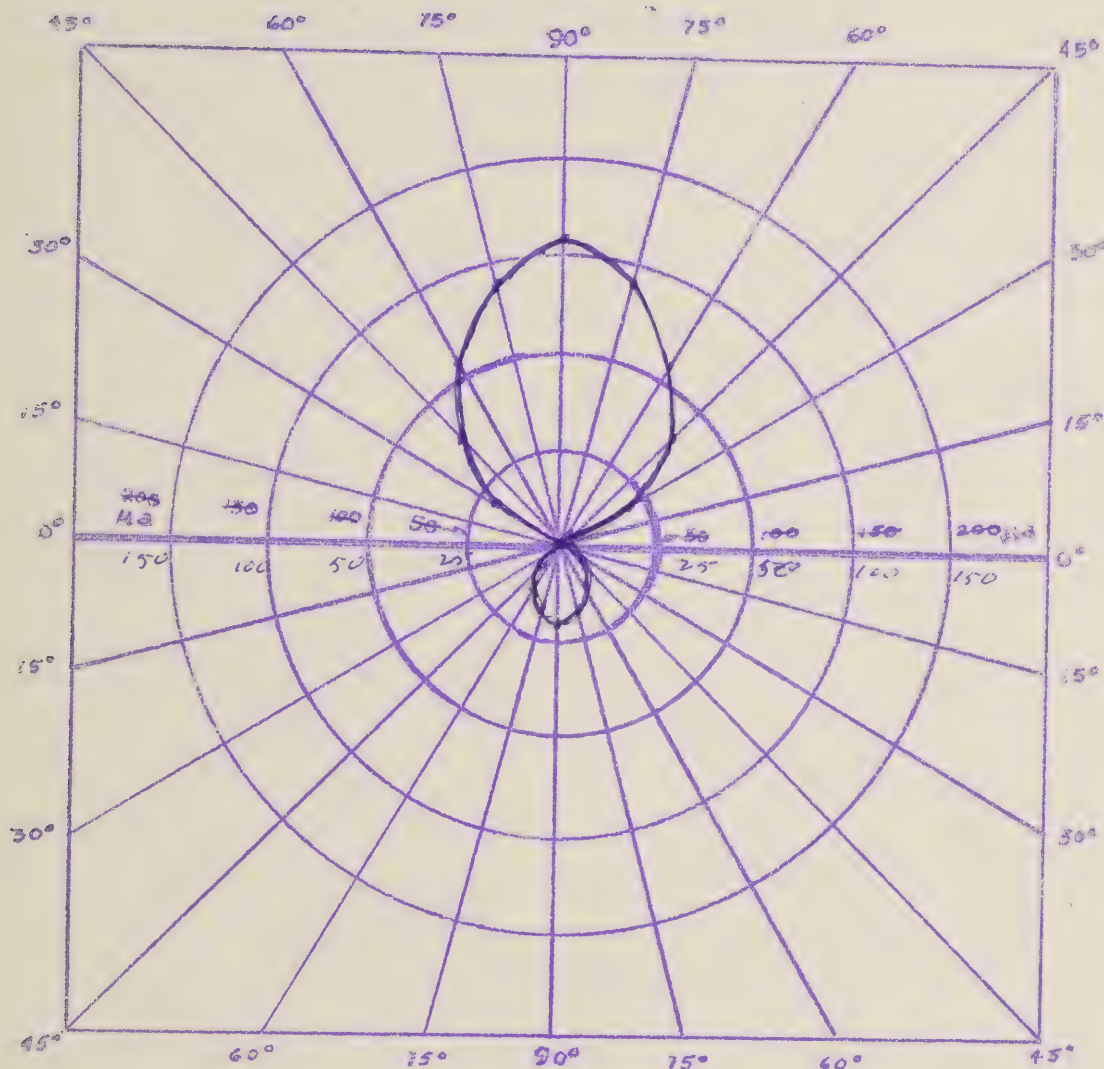- IV. 6. The lamp does not represent the matched load for the line. The shorted stub was less than a $\frac{1}{4}$ wavelength. A shorted stub less than a $\frac{1}{4}$ wavelength acts inductive. When a line is not terminated with it's characteristic impedance it acts either inductive or capacitive. Since the stub used was inductive, the cancelled reactance must be capacitive.

RADIATION PATTERN for Dipole with Reflector



Objective: To develop an understanding of polar graphs and the radiation pattern of a common dipole with a reflector.

Procedure: Connect signal level indicator to to transmission of fixed antenna. By signal level determine origin of transmitting antenna. From this reference plot a graph by rotating the antenna and observing the signal level.

What value is the front to back ratio?

$$\frac{\text{MAXIMUM FRONT } 110 \text{ } \mu\text{v}}{\text{BACK } 20 \text{ } \mu\text{v}} = \text{RATIO} = 5.5$$

Los Angeles Trade Tech. Jr. College
Instructor: R.H. Oeffinger

Agustin Lucas
May 28 1957

ELECTRONICS TECHNICIAN


JOB SHEET

Amplitude Modulation

Objective: How to measure the % of modulation.

Equipment: Oscilloscope, signal generator—RF and AF.

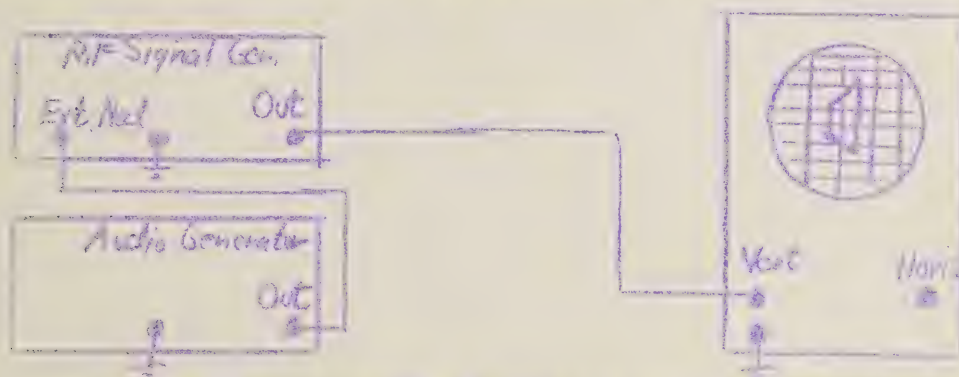Procedure: Connect equipment as shown to obtain trapezoidal pattern.



Draw the patterns showing zero, 50%, 60%, 100% and over modulation. Use the graph on the face of the scope and the following equation:

$$\% \text{modulation} = \frac{H_{\text{max.}} - H_{\text{min.}}}{H_{\text{max.}} + H_{\text{min.}}} \times 100$$

(use drawing form)

Summary Questions:

1. Name at least three types of modulation besides plate mod. Control Grid, Screen Grid and Cathode Modulation.
2. What determines the bandwidth in amplitude modulation? The range of fre. of the modulating signal. That is from the lowest modulating fre. with side-bands to the highest modulating fre. with side-bands.
3. Draw oscilloscope patterns for each case under procedure using the time base method.

24
23
22
21
20
19
18
17
16
15
14
13
12
11
10
9
8
7
6
5
4
3
2
1
0

1

1

2

3

4

5

6

7

8

9

10

11

12

13

14

15

16

17

18

5

5

$$MODU = \frac{5-5}{5+5} \times 100 = 0\%$$

$$MOD = \frac{5-1.75}{5+1.75} \times 100 = 48.2\%$$

3

5.5

5

$$MOD = \frac{5-.55}{5+.55} \times 100 = 80\%$$

4

0

5

$$MOD = \frac{5-0}{5+0} \times 100 = 100\%$$

ELECTRONICS TECHNICIAN


JOB SHEET

Hartley Oscillator

Objectives: How to test and adjust oscillators and
cause and requirements for oscillation.

Materials: Neon and pilot lamp, diode crystal, and hookup wire.

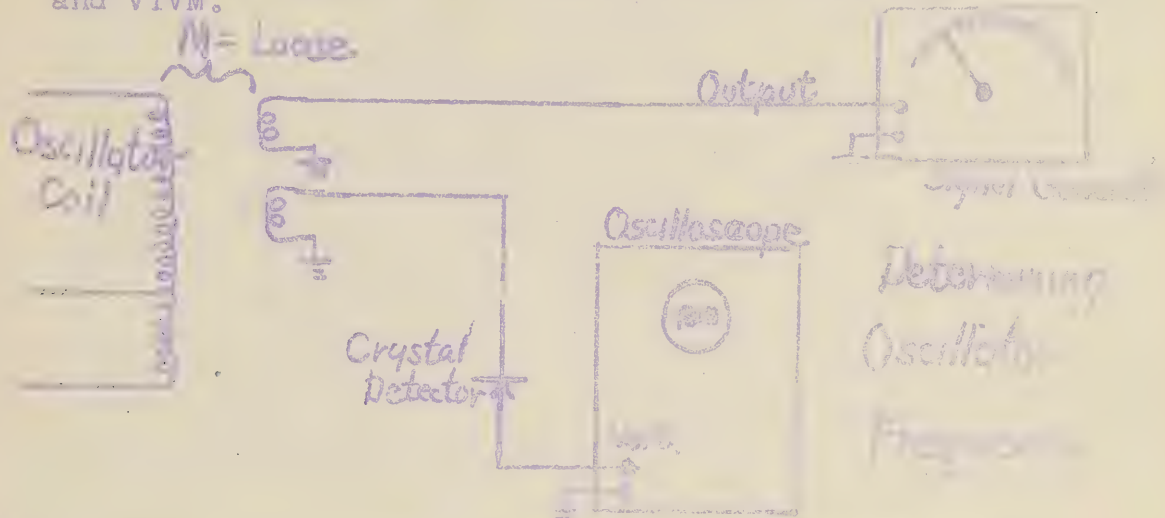Equipment: Oscillator instruction chassis, scope, signal generator
and VTVM.



Procedure: Examine oscillator and draw schematic (technical drawing)

Explain in detail its operation (technical drawing)

Construct a loading device and RF indicator.
Two loops of hookup wire that will slip over the
coil and solder the ends to the pilot lamp.
coil and record which position (plate or ~~grid~~) lights
up the lamp the brightest. Explain--- ~~GRID~~

The lamp lights up brightest on the bottom section, or plate
side of the coil. In this section there is more current, since
the feedback current plus the tank current are flowing
through that part of the coil.

1. Examine the RF potential and ground points.

The grid side of the tank has the highest RF potential.
The plate side has less RF.
The ground points have a very slight indication of RF.
The B plus no RF potential.

(1000)

Job Sheet--Hartley Oscillator

To determine frequency connect equipment as shown. This procedure will produce a zero beat at resonant frequency which can be observed on the oscilloscope.

Give frequency range of the oscillator.

From 2.7 Mc. to 4.9 Mc.

With the aid of the VTVM check for grid bias and record this value:

Maximum grid bias with no load: -13.6 v at 2.7 Mc.

" " " with load: -7.5 v. at 4.9 Mc.

Describe the effect of loading this type of oscillator:

As it can be seen by the drop on grid bias voltage above, when the circuit was loaded, the frequency shifted and the bias voltage dropped considerably. The drop of grid bias voltage indicates a loss of some of the oscillating voltage. This fact along with the fre. shift indicates that the circuit has been detuned. Therefore, when the circuit is loaded in the manner done on this job sheet, the energy consumed by the pilot lamp must come from the tank. In effect the Q of the circuit is lowered by the reflected impedance. This impedance is not a perfect resistance, since a reactance must also have been reflected to detune the tank.

Los Angeles Trade Tech. Jr. College
Instructor: R. H. Coffinger

Technician: Agustin Lucas

Date: May 28 1957

ELECTRONICS TECHNICIAN

TECHNICAL REPORT

Title: Hartley Oscillator

The Hartley is a self-excited oscillator. That is, oscillations begin spontaneously. No external source is required to trigger it.

Assuming that the cathode is heated for normal operation, but with no B plus applied to the plate, no current can flow. Now if by means of a switch, B plus is applied to the plate, there will be a surge of current through the tube since at that instant the bias is zero. Part of this current is fed to the grid tank circuit through the bottom section of the tank coil. This current will induce a voltage in the rest of the coil, which in turn will start the tank oscillating. The frequency of these oscillations will depend on the values of the capacitor and the coil.

As the tube current increased the grid began to draw current developing a negative voltage across the grid resistor.

In the meantime the tank oscillations keep increasing in strength due to the feed-back current. This oscillating voltage keeps adding and subtracting to the grid leak bias voltage until the negative peaks drive the grid to cut-off, stopping the tube current. At this point the bias is kept constant by the action of the bias capacitor.

The bias increases in the positive direction only when the positive peaks of the oscillations overcome the cut-off point. During this positive peaks, plate current flows for an instant, feeding back to the tank enough energy to sustain the oscillations.

